

Paper Id: **120102**Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--


**B.TECH**  
**(SEM I) THEORY EXAMINATION 2019-20**  
**BASIC ELECTRICAL ENGINEERING**

*Time: 3 Hours**Total Marks: 70***Note:** 1. Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 7 = 14**

- a. Three resistor  $2\Omega$ ,  $4\Omega$ ,  $5\Omega$  are connected in delta Determine its equivalent Star connection.
- b. Define Form Factor and Peak Factor.
- c.  $V_1 = 50 \sin 50 t$  and  $V_2 = 30 \sin (50 t - \pi/4)$ . Illustrate by phasor diagram.
- d. What is the major difference between PMMC type and dynamometer type of instruments?
- e. Compare star connection with delta in 3 phase system.
- f. Why dc series motor is never started on No load?
- g. Write different methods of starting single phase induction motor.

**SECTION B****2. Attempt any three of the following:****7 x 3 = 21**

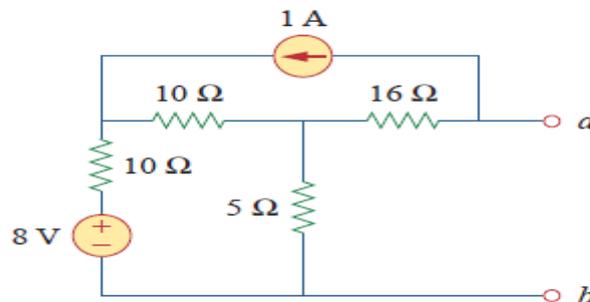- a. Obtain the Thevenin equivalent at terminals of the circuit given below-



- b. Explain with neat diagram, working principle of Moving Iron type electrical measuring instruments also write advantages and disadvantages.
- c. A sinusoidally varying alternating current of frequency 50 Hz has a maximum value of 10 amperes:
  - (i) Write down the equation for instantaneous value. (ii) Find the value of current after  $1/100$  second. (iii) Find the time to reach 7 amp for the first time and (iv) Find its average value
- d. Explain the two-wattmeter method for determination of power and power factor of three-phase load with suitable diagram.
- e. Explain principle of operation of three phase induction motor. Draw the torque-slip characteristics of a three phase induction motor.

Paper Id: 

120102
--------


Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--

## SECTION C

3. Attempt any *one* part of the following: 7 x 1 = 7

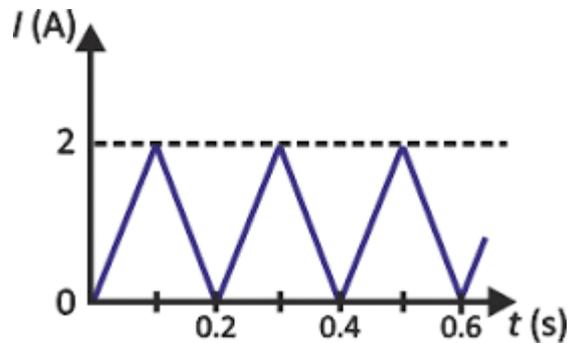- (a) Find the Average value and RMS value of the following wave.



- (b) A circuit consists of three parallel branches. The branch currents are represented by
- $i_1 = 10 \sin wt$
- ,
- $i_2 = 20 \sin (wt + 40^\circ)$
- ,
- $i_3 = 7.5 \sin (wt - 45^\circ)$
- . Find the resultant current and express it in the form
- $i = i_m \sin (wt + \phi)$
- .

4. Attempt any *one* part of the following: 7 x 1 = 7

- (a) Give the relationship between quality factor, resonant frequency and bandwidth for a series R-L-C Circuit.
- 
- (b) Why power factor improvement is required, explain any method to improve power factor.

5. Attempt any *one* part of the following: 7 x 1 = 7

- (a) Explain the principle of operation of attraction type of moving iron instruments. A moving coil instrument gives a full scale deflection of 30 mA when a potential difference of 70 mV is applied. Calculate the series resistance to measure 750V on Full scale.
- 
- (b) A 3-phase star connected balanced load is supplied 400 V, 50 Hz. The load takes a leading current of 1.732 A and power 20 KW. Calculate power factor of the load, resistance and inductance per phase.

6. Attempt any *one* part of the following: 7 x 1 = 7

- (a) List the various losses that occur in transformer. Derive the condition of maximum efficiency.
- 
- (b) Write analogy between Magnetic circuit and electric circuit.

7. Attempt any *one* part of the following: 7 x 1 = 7

- (a) Derive EMF equation of DC Machine; explain with the help of neat diagram the different types of DC motors.
- 
- (b) Explain working principle of synchronous motor and write its specific applications.