

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2019

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

SECOND SEMESTER EXAMINATION, 2005-2006

ELECTRICAL ENGINEERING

Time : 3 Hours

Total Marks : 100

- Note :**
- (i) Attempt **ALL** questions.
 - (ii) All questions carry equal marks.
 - (iii) In case of numerical problems assume data wherever not provided.
 - (iv) Be precise in your answer.

1. Attempt **any four** parts of the following : (5x4=20)

(a) The equation of an alternating current is

$$i = 42.42 \sin 628 t$$

Determine

- (i) its maximum value
 - (ii) frequency
 - (iii) rms value
 - (iv) average value
 - (v) form factor
- (b) Draw a phasor diagram showing the following voltages

$$V_1 = 100 \sin 500 t, \quad V_2 = 200 \sin (500 t + \pi/3)$$

$$V_3 = -50 \cos 500 t, \quad V_4 = 150 \sin (500 t - \pi/4)$$

Find RMS value of resultant voltage

()17099

- (c) A 120 V, 60 W lamp is to be operated on 220 V, 50 Hz supply mains. In order that lamp should operate on correct voltage. Calculate value of -
- non inductive resistance
 - pure inductance
- (d) A series ac circuit has a resistance of 15Ω and inductive reactance of 10Ω . Calculate the value of a capacitor which is connected across this series combination so that system has unity power factor. The frequency of ac supply is 50 Hz.
- (e) A series R-L-C circuit has $R = 10 \Omega$, $L = 0.1 \text{ H}$ and $C = 8 \mu\text{F}$. Determine
- resonant frequency
 - Q-factor of the circuit at resonance
 - the half power frequencies
- (f) Explain parallel resonance. Why is parallel resonance called the current resonance? Show the graphical representation of current in parallel resonance.

2. Attempt *any four* parts of the following : (5x4=20)

- (a) Using loop current method find the current I_1 and I_2 . Shown in Fig. 1.

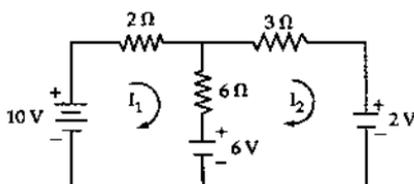


Fig. 1.

- (b) Use nodal analysis to find the currents in various resistors of the circuit shown (Fig. 2.0)

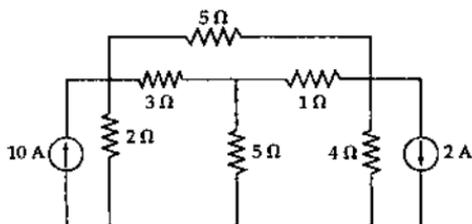


Fig. 2.0

- (c) Find Thevenin's equivalent circuit across A B Shown in Fig. 3.0

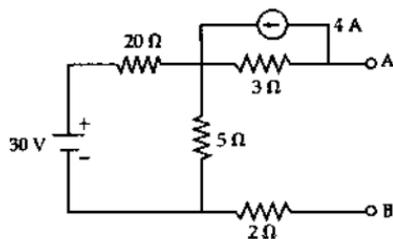


Fig. 3.0

- (d) Find the resistance between A B of the circuit shown in Fig. 4.0 use Y-Δ (star-delta) transformation.

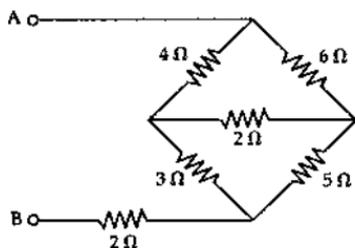


Fig. 4.0

- (e) A 50 A, 230 V meter on full load test makes 61 revolutions in 37 seconds. If the normal disc speed is 500 revolutions per kWh, find the percentage error.
- (f) Explain the working principle of induction type wattmeter with the help of diagram.

3. Attempt *any two* parts of the following : (10x2=20)

- (a) Derive expression for power in 3 phase star and delta connections. A balanced star connected load of $(\delta + j6)\Omega$ per phase is connected to a balanced 3-phase, 400 V supply. Find the line current, power factor and power.
- (b) Explain basic principle of operation of a single phase transformer. Where are they used ? Calculate the voltage regulation of a transformer in which ohmic drop is 1% and reactance drop 5% of the voltage at the following power factor (i) 0.8 lagging (ii) 0.8 leading.
- (c) Single phase transformer gave following test results : Rating 100 kVA, 11 kV/220V , 50 Hz
OC test : 220 V, 45 A, 2 kW
SC test : 500 V, 9.09 A, 3 kW
Determine equivalent circuit parameters referred to l.V. side.

4. Attempt *any four* parts of the following : (5x4=20)

- (a) Derive e.m.f. equation of a d.c. generator. What will be change in e.m.f. induced if flux is reduced by 20% and the speed is increased by 20%.
- (b) Why does the terminal voltage of d.c. shunt generator fall when it is loaded ? Explain with the help of load characteristics.
- (c) Describe one method to control the speed of D.C. shunt motor.
- (d) What are different losses in d.c. machines on what factors they depend.
- (e) Explain principle of operation of electromechanical energy conversion.
- (f) Explain V-curve and give applications of synchronous motor.

5. Attempt *any four* parts of the following : (5×4=20)

- (a) Why is problem of starting in single phase induction motor ? Describe one method to start it.
- (b) Explain Star-Delta starter used for starting 3 phase induction motor.
- (c) Define slip in 3-phase induction motor. What is its value at starting and at the synchronous speed. Draw torque-slip characteristics of 3-phase induction motor.
- (d) A 3-phase, 4-pole induction motor is supplied from 3-phase, 50 Hz ac supply. Calculate :
 - (i) the synchronous speed.
 - (ii) the rotor speed when slip is 4%.
 - (iii) the rotor frequency when rotor runs at 600 r.p.m.
- (e) Give applications of 3-phase induction motor and single phase induction motor. Why is 3-phase induction motor used for medium and large load and single phase induction motor for small load applications.
- (f) Explain principle of operation of three phase induction motor.

- o O o -