



Printed Pages : 7

TEC – 101 / TEC-201

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3033/3034

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B. Tech. (Sem. I & II)

SPECIAL CARRYOVER EXAMINATION, 2006-07

ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 100

- Notes :*
- (1) Attempt all questions.*
 - (2) Number of parts to be attempted from each question are indicated.*

1 Answer any **four** parts from the following : **4×5**

- (a) Comment on any **two** from the following statement :
 - (i) Electron and hole recombine and disappear.
 - (ii) An intrinsic semiconductor have equal number of electrons and holes.
 - (iii) A semiconductor behaves like an insulator at 0°k and becomes conductor at room temperature.
- (b) Draw the V-I characteristic of p-u junction diode. Write the current-voltage equation, specify all terms of equation. Discuss its temperature dependance.

- (c) Discuss the capacitive effect of p-n junction under reverse bias. What will happen to capacitance if the polarity of the applied voltage is changed explain ?
- (d) At what voltage the reverse current flowing through a germanium diode will reach 90% of its saturation value at room temperature 27°C ?
- (e) Define static and dynamic resistance of diode. How it can be obtained ?
- (f) Calculate V_0 and I_D for the circuit given in **fig. 1**.

 


Fig. 1

2 Attempt any **two** parts from the following : **2×10**

- (a) (i) Draw the circuit diagram of a full wave rectifier with π filter whose PIV = V_m .
- (ii) Define voltage regulation. Derive the expression for regulation and show that it is same in Half wave rectifier and full wave rectifier.
- (b) (i) What is the difference between avalanche breakdown and zener breakdown of a p-n junction ? Draw the circuit diagram of voltage regulator using zener diode.

- (ii) Calculate the V_{DC} , I_{DC} , $V_{r(rms)}$, I_{rms} through 1 kohm load connected to half wave rectifier circuit shown in fig. 2.


 


Fig. 2

- (c) (i) Prove that maximum d.c. output power occurs in half wave rectifier when $R_f = R_L$.
- (ii) Write short notes on any **two** of the following :
- (i) Voltage multiplier circuit using diodes.
 - (ii) Clipping circuits
 - (iii) Different type of filters used in rectifiers.
- 3** Attempt any **two** parts from the following : **2×10**
- (a) (i) Draw the output characteristic curve of n-p-n transistor in CE configuration level the parameters and indicate different regions of operation.

 - (ii) A germanium transistor used in an amplifier has a collector cut off current $I_{CO} = 10 \mu\text{A}$ at a temperature of 20°C and $h_{FE} = 50$, find collector current when.
- The Base current is 0.25 mA .
 - Assuming h_{FE} does not increase with temperature and temperature rises to 50°C .
- (b) (i) What do you understand by "Transistor biasing" ? Mention the important points to be considered for the selection of operating point.
- (ii) A Germanium transistor with $\beta = 49$ has the potential divider arrangement with $R_L = 1 \text{ kohm}$, $V_{CE} = 5 \text{ V}$, $I_C = 4.9 \text{ mA}$ and $V_{BE} = 0.2 \text{ V}$. The stability factor is desired to be 10. Obtain the values of biasing resistors R_1 , R_2 and R_E . Draw the circuit diagram also.
- (c) Draw the low frequency hybrid model of transistor amplifier in CE configuration given in **fig. 3** (c) and calculate input resistance, current gain and voltage gain of the amplifier. Given $h_{ie} = 1 \text{ k}$, $h_{re} = 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 100 \mu \text{ mho}$.



4 Answer any **four** parts from the following : 4×5

- (a) Explain the phenomenon of "Pinch off" in JFET.

An n channel silicon JFET has a donor concentration of $2 \times 10^{21}/\text{m}^3$ and a channel width of $4 \mu\text{m}$. If the dielectric constant of S_i is 12, find the pinch off voltage.

- (b) Why FET is called voltage controlled device ?
Draw the circuit diagram of JFET common drain amplifier and derive the expression for its voltage gain.

- (c) In a self bias n channel JFET, the operating point is to be set at $I_D = 1.5 \text{ mA}$ and $V_{DS} = 10 \text{ V}$. The JFET parameters are $I_{DSS} = 5 \text{ mA}$ and $V_P = -2\text{V}$. Find the value of R_S and R_D for given $V_{DD} = 20 \text{ V}$, draw the circuit diagram also.

- (d) Write the basic difference between enhancement and depletion MOSFET. Draw the structure of P-channel depletion MOSFET and explain working with drain and transfer characteristics.
- (e) Draw the structure of n channel JFET its drain and transfer characteristics. Indicate the different regions of operation in the drain characteristics. Why the name is "Field Effect Transistor" ?
- (f) Discuss different biasing methods of JFET.

5 Attempt any **four** parts from the following : **4×5**

(a) Convert the following as directed :

(i) $(62.7)_8 = (-----)_{16}$

(ii) $(0.342)_6 = (-----)_{10}$

(iii) $(10.10001)_2 = (-----)_8$

(iv) $(1 BE)_{16} = (-----)_8$

(v) $(547)_{10} = (BCD \text{ code})$

(b) Simplify one of the following Boolean expressions and implement the result as a logic diagram :

(i) $AB\bar{C}\bar{D} + A\bar{B}\bar{C}D + ABC\bar{D} + ABCD$

(ii) $AB + A\bar{B}C(\bar{B}C + C) + \bar{A}C$

(c) Reduce the following using K Map.

$$f(A, B, C, D) = \sum M (0, 1, 2, 11, 12, 14, 15) + d (3, 5, 6, 13)$$

- (d) Draw the pin diagram of 741 Op-Amp and mention the function of each pin. What are the characteristics of an ideal Op-Amp ? Why it is called operational amplifier ?
- (e) Calculate the maximum and minimum closed loop gain for the amplifier shown in **fig. 4** (e) assuming ideal Op-Amp.

 


Fig. 4

(f) State and prove DeMorgan's theorem.