

Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B. TECH.**  
**(SEM I) THEORY EXAMINATION 2020-21**  
**EMERGING DOMAIN IN ELECTRONICS ENGINEERING**

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

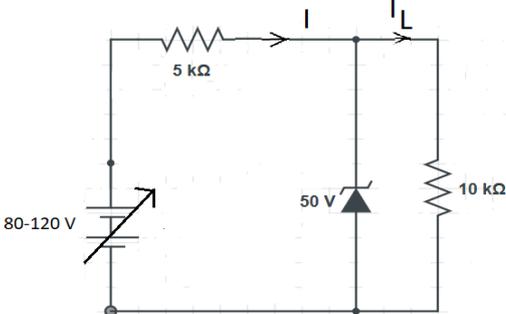
**SECTION A**

1. Attempt all questions in brief. 2 x 10 = 20

Q no.	Question	Marks	CO
a.	What do you mean by the term doping? Why it is required?	2	1
b.	List any two advantages of modulation.	2	3
c.	Evaluate: $(637)_9 = (?)_5$	2	2
d.	Draw the VI characteristics of an ideal diode in forward and reverse bias conditions.	2	2
e.	State two differences between microprocessor and microcontroller.	2	3
f.	Why bridge type full wave rectifier is preferred over center tapped full wave rectifier. State two reasons.	2	1
g.	State two differences between FET and BJT.	2	4
h.	Differentiate between avalanche and zener breakdown.	2	1
i.	Find 1's and 2's complement of : 1101001	2	2
j.	State the basic difference between Bluetooth and Wi-Fi technology.	2	2

**SECTION B**

2. Attempt any three of the following:

Q no.	Question	Marks	CO
a.	(i) With help of neat circuit diagrams, explain the working of a full wave bridge rectifier. (ii) Define the term ripple factor. What is the value of the ripple factor for a half wave rectifier and a full wave rectifier?	6+4	3
b.	(i) With help of a neat diagram, explain the working of a voltage doubler circuit. (ii) Write a short note on varactor diode.	6+4	3
c.	For the circuit shown below, determine the value of maximum and minimum zener diode current.  	10	4
d.	(i) What are liquid crystal displays? Explain their working with help of a neat diagram. (ii) Determine the output waveform of the following circuit,	3+7	4





Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

	(ii) $(110110.011)_2 = (?)_{16}$ (iii) $(231.36)_{10} = (?)_2$ (iv) $(11011.10)_2 = (?)_{10}$ (v) $(534)_8 = (?)_{10}$		
--	---	--	--

**6. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	(i) What do you mean by amplitude modulation? Explain with help of proper waveforms. (ii) AM radio transmitter radiates 6 KW power when modulation percentage is 70 %. Determine the carrier power.	5+5	4
b.	(i) Write a short note on satellite communication system. (ii) Differentiate between CDMA and GSM?	5+5	3

**7. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	(i) What are universal gates? Why are they called so? (ii) Implement XOR gate using NAND gate only.	5+5	2
b.	Determine the output for the following circuits:  (i) <div style="text-align: center;"> </div> (ii) <div style="text-align: center;"> </div>	5+5	4

XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX