

B.TECH.**THEORY EXAMINATION (SEM-II) 2016-17****BASIC ELECTRONICS****Time : 3 Hours****Max. Marks : 70****Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.****SECTION – A****1. Explain any seven of the following:****7 x 2 = 14**

- (a) Classify the materials with help of energy band.
- (b) Explain the principle of operation of LED.
- (c) Derive the relationship between α and β .
- (d) Why are FET called unipolar device?
- (e) Write down the constructional difference between Depletion type and Enhancement type MOSFET.
- (f) Derive the circuit of integrator using an ideal Op-Amp.
- (g) State the advantages of digital instruments over analog instruments.
- (h) Briefly discuss the need of modulation in communication engineering.

SECTION – B**2. Attempt any five of the following questions:****5 x 7 = 35**

- (a) Explain the V-I characteristic of p-n junction diode. How it is differ from Zener diode?
- (b) Draw the circuit and discuss the working of full wave bridge rectifier with suitable input -output waveforms. What is PIV of bridge rectifier?
- (c) Draw and explain the construction and working of p-channel depletion type MOSFET. Also draw the characteristics of p-channel depletion type MOSFET.
- (d) Calculate the output voltage for the circuit of Figure 1 with inputs of $V_1 = 40$ mV rms and $V_2 = 20$ mV rms.

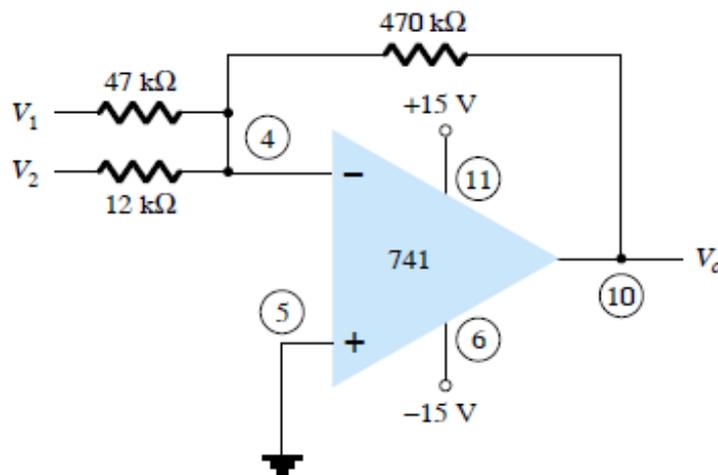


Figure 1

- (e) Given that $I_{CQ} = 2$ mA and $V_{CEQ} = 10$ V, determine R_1 and R_C for the network of Figure 2.

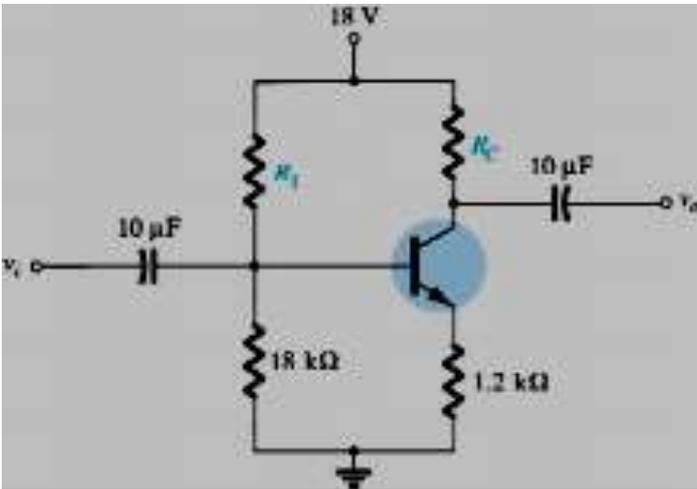


Figure 2

- (f) Draw and explain the block diagram of Ramp type digital voltmeter. Also draw related voltage to time conversion waveforms.
- (g) Derive the expression for AM modulated waveform. Also derive the expression for modulation index.
- (h) Describe the operation of CRT with neat block diagram. How unknown frequency is measured using CRO?

SECTION – C

Attempt any two of the following questions: 2 x 10.5 = 21

- 3. (a) Explain principle of operation and construction of Tunnel diode. Draw its V-I characteristic.
- (b) Design a clamper to perform the function indicated in Figure 3.

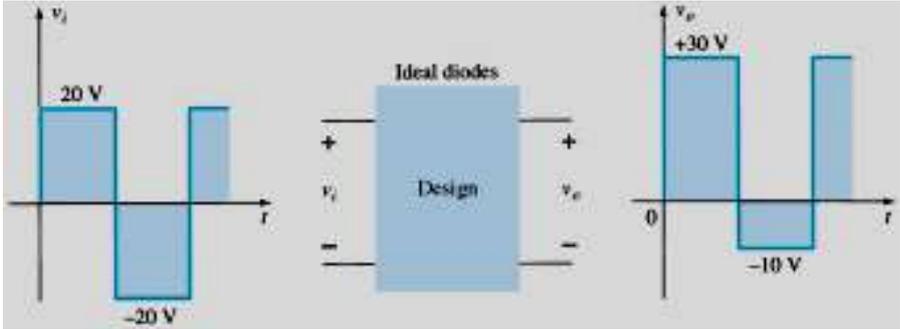


Figure 3

- 4. (a) Draw and explain the N-channel JFET and draw its transfer characteristics.
- (b) Draw and explain the differential amplifier. Define CMRR and slew rate in Op-Amp.
- 5. (a) Draw the CE n-p-n BJT characteristics. Also explain the self bias configuration in DC bias configuration.
- (b) Discuss the need of modulation in the communication engineering. Which types of modulations are used in television?