

Printed Pages: 02

Sub Code: EE-201

Paper Id: 120201

Roll No.

--	--	--	--	--	--	--	--	--	--

B TECH
(SEM II) THEORY EXAMINATION 2018-19
ELECTRICAL ENGINEERING

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If you require any missing data, choose suitably.

SECTION A

1. Attempt all questions in brief.

2 x 10 = 20


- What do you mean by active and passive elements?
- Explain the concept of source transformation with the help of an example
- Explain form factor and peak factor in a A.C. circuit.
- What is the significance of power factor?
- What do you mean by absolute instruments?
- What is the necessity of a three phase system?
- Why transformer cannot work on dc supply?
- Explain the concept of mutual induction.
- What is the physical significance of back e.m.f. in d.c. motor?
- Can induction motor runs at synchronous speed? Justify your answer.

SECTION B

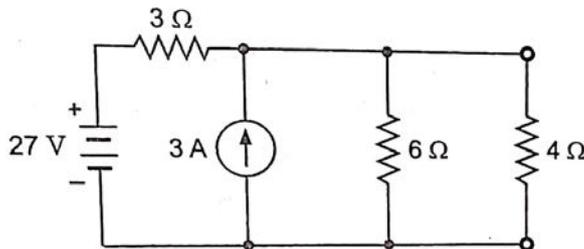2. Attempt any three of the following:

10 x 3 = 30

- Explain superposition theorem and find current in 4 ohm resistance of the given circuit.




- Explain resonance in a series R-L-C circuit and derive the relation for resonance frequency, impedance at resonance, and quality factor.
- Prove that in a three phase system, the sum of three phase power is equal to the sum of powers obtained by two wattmeters from two wattmeter method.
- Draw the layout of a power system using single line diagram explain in detail.
- What are the classifications of single phase induction motor based on the method of starting? Also explain why single phase induction motor is not self starting.

SECTION C

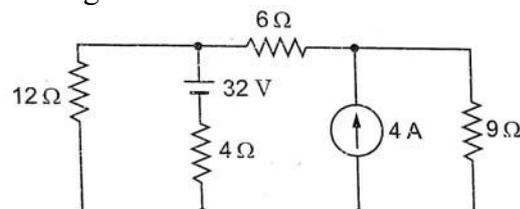3. Attempt any one part of the following:

10 x 1 = 10

- Explain and derive maximum power transfer theorem and find the efficiency in maximum power transfer theorem.
- In the given circuit find current in 6 ohm resistance using Thevenin theorem



4. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) Draw the phasor diagram of a pure inductive circuit and show that in a pure inductive circuit average power is always zero.
 - (b) A coil of resistance 100 ohm and inductance of 1 H is connect in series with a condenser of capacitance 200 μf across a 240 v , 50 Hz supply. Determine the following : (i) Impedance (ii) Current (iii) power factor (iv) Voltage across coil (v) voltage across capacitor.
5. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) Discuss the principle, construction, operation, advantage disadvantage and application of single phase dynamometer wattmeter.
 - (b) A balanced star connected load of $(10+j20)$ ohm/phase is connected to 3 phase 400 v supply . Find Line current, phase current, power factor, reactive power, active power and total volt amperes.
6. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) What are the difference and similarity between electric circuit and magnetic circuits?
 - (b) Explain different types of losses in a transformer and derive the relation for maximum efficiency.
7. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) Draw and discuss the characteristic of different types of D.C. motor and also give their applications.
 - (b) Explain the construction and working of 3 phase induction motor.