

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 2019**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

(SEM II) EVEN SEMESTER THEORY EXAMINATION, 2009-2010

**ELECTRICAL ENGINEERING**

Time : 3 Hours

Total Marks : 100

- Note:**
- (i) Attempt ALL questions.
  - (ii) All questions carry equal marks.
  - (iii) In case of numerical problems assume data wherever not provided.
  - (iv) Be precise in your answer.

1. Attempt any four parts of the following : (4x5=20)

- (a) An alternating current is represented by  $i = 400 \sin(157t + \pi/6)$  Determine :
  - (i) Average value of current
  - (ii) RMS value of current
  - (iii) Time period
  - (iv) Form Factor
  - (v) Phase angle
- (b) With the help of power triangle explain active and reactive powers. Prove that in a purely inductive circuit power absorbed is zero.
- (c) A series combination of R and C is in parallel with a  $20\Omega$  resistor across 50 Hz source results in a total current of 8A. Current through the  $20\Omega$  resistor is 5A and current in the R-C branch is 3A. Determine R and C.
- (d) A voltage wave  $e(t) = 141.4 \sin 120t$  produces a current  $i(t) = 14.14 \sin 120t + 7.07 \cos (120t + 30^\circ)$  in a circuit. Determine :
  - (i) the time expression of resultant current
  - (ii) the power factor of the system and the power delivered by the source.

- (e) A series combination of a capacitor C and resistor R is shunted by an inductive coil having resistance R and inductance L and the combination is connected to an ac source. Show that the impedance of the circuit will be independent of frequency if  $R = \sqrt{\frac{L}{C}}$ .
- (f) Deduce analogy on three points between magnetic circuit and electric circuit. What are the two major points of difference between them?

2. Attempt **any four** parts of the following :

(4x5=20)

- (a) In the network shown in Fig. 1.1 determine the direction and magnitude of current flow in the ammeter A having a resistance of  $10\Omega$ .

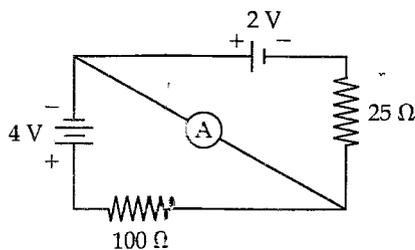


Fig. 1.1

- (b) Determine Norton's equivalent across AB in Fig.1.2.

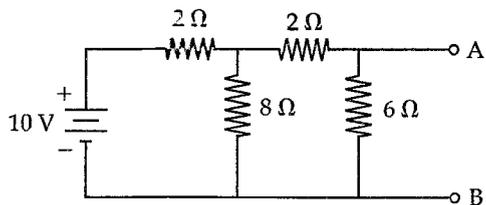


Fig. 1.2

- (c) State and explain maximum power transfer theorem. Find the value of R which will absorb maximum power in Fig. 1.3.

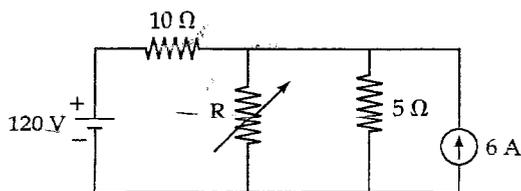


Fig. 1.3

- (d) Deduce the expression for converting a star connected resistances into an equivalent delta.
- (e) Describe the constructional details of a single phase induction types energy meter with the help of a circuit diagram. Give its principle operations and use.
- (f) A moving coil instrument gives a full scale deflection of 10m A when the potential differences across its terminals is 100 mV. Calculate the series resistance to measure 1000V on full scale.

3. Attempt any two parts of the following : (2x10=20)

- (a) Compare star and delta systems of connection in 3 phase a.c. circuits. Justify that total power in the 3-phase, 3-wire star connected load circuit is the algebraic sum of two wattmeters. A 3-phase 400V motor load has a power factor of 0.75(lag). Two wattmeters connected to measure the power, reads the total input to be 26 kW. Find the reading of each instrument.
- (b) Define voltage regulation of a single phase transformer. How it is determined? Calculate the regulation of a transformer in which ohmic drop is 1% and reactance drop 5% of the voltage at the following power factors (i) 0.8 lagging (ii) 0.8 leading.
- (c) Following are the test results for the 4 kVA, 200V/400V, 50Hz single phase transformer

OC test : 200V, 0.8A, 70 W

SC test : 17.5V, 9A, 50 W

Calculate the parameters of equivalent circuit and its efficiency at full load.

4. Attempt any two parts of the following : (2x10 =20)

- (a) Explain the role of back emf in DC motor. A 200V dc series motor runs at 500 rpm when taking a current of 25A. The resistance of the armature is  $0.5\Omega$  and that of the field is  $0.3\Omega$ . If the current remains constant, calculate the resistance necessary to reduce the speed to 250 rpm.
- (b) Draw and explain :
- (i) Operating characteristics of D.C. shunt generator.
- (ii) Speed-torque characteristic of D.C. motor.
- (iii) V curve of Synchronous motor.
- (c) Explain the methods of speed control of D.C. motors. Give the application of the D.C. series motor, D.C. shunt motor and synchronous motor.

5. Attempt **any two** parts of the following :

(2x10=20)

(a) Prove that for 3-phase Induction motor.

$$P_g : \text{rotor ohmic loss} : P_m = 1 : S : (1-S).$$

Where  $P_g$  = Airgap power

$P_m$  = Mechanical power

The power input to a 500 V, 50Hz, 6 pole, 3-phase squirrel cage induction motor running at 975 rpm is 40 kW. The stator losses are 1 kW and the friction and windage losses are 2 kW. Calculate (i) slip (ii) rotor copper loss (iii) motor efficiency.

(b) Draw torque slip characteristics of 3-phase Induction motor. Explain what will happen if rotor resistance is increased? Give the application of 3-phase induction motor.

(c) Justify using double revolving field theory that net starting torque in single phase induction motor is zero. Explain various methods of starting single phase Induction motors.

- o O o -