

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3034 Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

SECOND SEMESTER EXAMINATION, 2005-2006

**ELECTRONIC ENGINEERING**

Time : 3 Hours

Total Marks : 100

- Note :** (i) Attempt ALL questions.  
(ii) All questions carry equal marks.  
(iii) In case of numerical problems assume data wherever not provided.  
(iv) Be precise in your answer.

1. Attempt *any four* parts of the following : (5x4=20)

- (a) Distinguish between intrinsic and extrinsic semiconductors. What properties of a semiconductor are determined from Hall effect experiment ? Explain briefly.
- (b) Describe the condition established by forward and reverse bias condition on a p-n junction diode and how the resulting current is affected ?
- (c) What is static and dynamic resistance in the forward biasing of the diode ? Explain with suitable diagram.
- (d) Draw a circuit diagram which uses a breakdown diode to regulate the output voltage across a load and explain the working.

- (e) How does the diffusion capacitance  $C_D$  vary with dc diode current ? Explain.
- (f) What do you mean by Zener and a Avalanche breakdown in the barrier layer of a semiconductor ?

2. Attempt *any four* parts of the following : (5x4=20)

- (a) Explain the following terms in context with a semiconductor diode.
- (i) Potential Barrier  
(ii) Depletion layer  
(iii) Breakdown voltage  
(iv) Peak inverse voltage  
(v) Knee voltage
- (b) For the given zener diode network shown in figure 2 (b) determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $I_R$ .

 


figure 2 (b)

- (c) A 220V, 50 Hz ac. voltage is applied to the primary of 4 : 1 step-down transformer, which is used in a bridge rectifier, having a load resistance of 1 kΩ. Assuming the diodes to be an ideal, determine the following :
- (i) D.C. output voltage  
(ii) DC. Power delivered to load  
(iii) PIV of each diode  
(iv) Output frequency

- (d) Draw the output waveform for the following circuit for the given input waveform [Ref to figure 2 (d)].

 


figure 2 (d)

- (e) Draw the voltage double circuit and the working of the circuit.  
 (f) Draw a neat diagram of a full wave bridge/rectifier circuit. Explain its working in details, clearly making the direction of flow of currents for positive and negative cycles.

3. Attempt *any four* parts of the following : (5x4=20)

- (a) For the given network shown in figure 3 (a) determine the  $I_C$ ,  $V_{CE}$ ,  $V_B$  and  $V_C$ .

 


figure 3 (a)

- (b) Draw the circuit diagram of transistor in the CE configuration. Sketch the output characteristics and indicate the active, saturation and cut off region.

- (c) A junction transistor has the following h-parameters  $h_{ie} = 2k$ ,  $h_{re} = 1.6 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 50 \mu A/V$ . Determine the current gain, voltage gain, input resistance and output resistance of CE amplifier if the load resistance is  $12 k\Omega$  and source resistance is  $500 \Omega$ .

- (d) Draw the hybrid equivalent circuit for common basic configuration and find the expression of current gain, voltage gain and input impedance.

- (e) Draw the d.c. load line and locate the operating point for the fixed biasing transistor circuit shown in figure 3 (e). What will be its stability factor.  $V_{BE} = 0.7V$ .

 


figure 3 (e)


- (f) Why a capacitive coupling is used to connect a signal source to an amplifier? For a capacitively coupled load, is the dc load larger or smaller than ac load? Explain.

4. Attempt *any two* parts of the following : (10x2=20)

- (a) What is the significant difference between the construction of an enhancement type MOSFET and depletion type MOSFET? Explain with suitable diagram.

 - (b) Determine the following for the given network shown in figure 4(b).

$I_{DQ}, V_{GSQ}, V_D, V_S, V_{DS}, V_{DG}$



- (c) What are the advantages of the FET over a conventional bipolar junction transistor? Define pinch-off voltage, amplification factor and drain resistance of FET. Explain with the help of circuit diagram, how an FET is used as a voltage dependent resistor.

5. Attempt *any two* parts of the following : (10x2=20)

- (a) (i) Convert the following function in to canonical form

(1)  $AB + \overline{BCD} + \overline{AD}$

(2)  $(A + \overline{B})(\overline{C} + \overline{D})(\overline{B} + \overline{C})$

- (ii) Convert the following numbers

(1)  $(4021.25)_{10} = ( )_2$

(2)  $(A6F.CD)_{16} = ( )_8$

- (iii) Solve the following :

(1)  $(A6C.DF)_{16}$       (2)  $(7001)_8$

+  $(IDE.9A)_{16}$       -  $(5763)_8$

- (iv) Minimize the give boolean function with the help of Boolean Algebra rules

$$f(A, B, C, D) = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}CD + \overline{A}B\overline{C}D + \overline{A}BCD + A\overline{B}\overline{C}D + A\overline{B}CD + AB\overline{C}D + ABCD + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D} + ABCD$$

- (b) (i) Minimize the given Boolean function using k-map

$$f(A, B, C, D) = \sum m(3, 4, 5, 7, 9, 13, 14, 15) + d(0, 2, 8)$$

Implement the minimized function only using NAND gates.

- (ii) Prove that the NAND and NOR gate is a universal gate.

- (c) (i) Explain the terms in op-Amp.

(1) Input off set current

(2) Input off set voltage

(3) Slew Rate

(4) CMRR

- (ii) Draw the circuit diagram of op-Amp as summer and subtractor and find out the expression for output.

- o o o -