

- (c) Determine V_L , I_L , I_Z and I_R for the circuit R_L is 470 ohms.

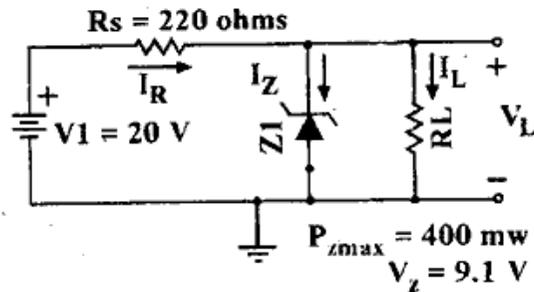


Fig. 3

- (d) For the clamping circuit shown in fig. 4 sketch for V_O .

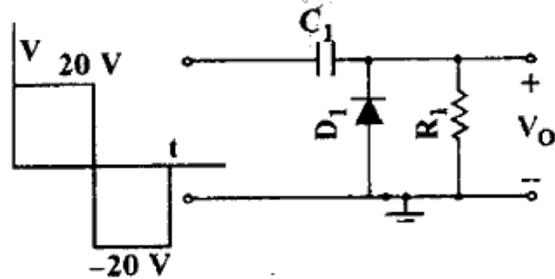


Fig. 4

- (e) Draw the circuit diagram of a bridge rectifier. Discuss the operation and find dc and rms output voltage.
 (f) With the help of the circuit diagram explain the working of a voltage doubler.

3 Attempt any **two** parts of the following : 10×2

- (a) For a voltage divider biasing circuit shown in fig. 5. Find I_C , V_{CE} , I_B , V_E and V_B .

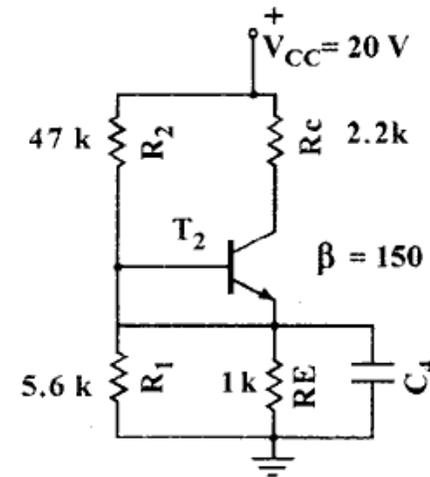


Fig. 5

- (b) For the circuit shown in fig. 6. Find A_v , A_i , Z_o and Z_i . (h) parameters are $h_{ie} = 1k$, $h_{re} = 0$, $h_{fe} = 50$, $h_{oe} = 0$.

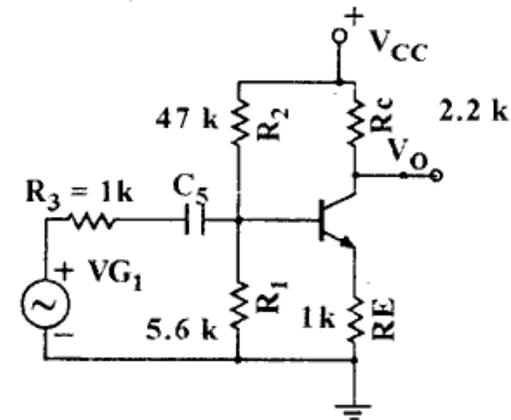


Fig. 6

- (c) Derive the expression for input impedance and voltage gain for a CE and shown in fig. 7 using simplified (approximate) equivalent circuit i.e. $h_{re} = h_{oe} = 0$.

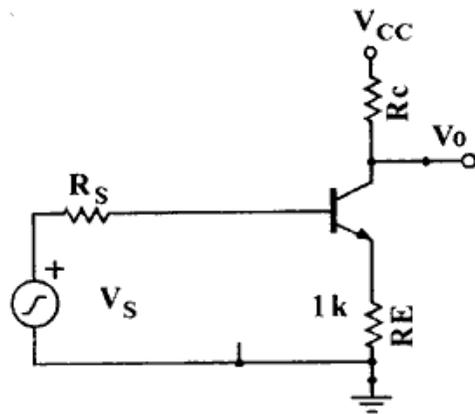


Fig. 7

4 Attempt any **two** parts of the following : 10×2

- (a) Define trans conductance (g_m) output resistance (r_p) and gain of a FET. How these parameters are determined graphically.
- (b) For common source FET amplifier with source resistance is R_s . Derive the expression for voltage gain input impedance and output impedance.
- (c) For a circuit shown in fig. 8. Calculate V_o , Z_i and Z_o . Input is $V_i = 0.2$ V (rms.)
 $I_{DSS} = 9$ ma $V_p = -4.5$ V.

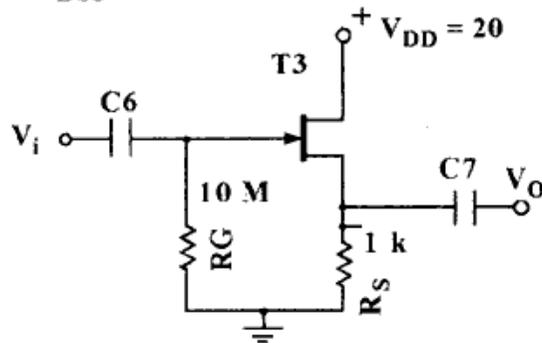


Fig. 8

5 Attempt any **two** parts of the following : 10×2

- (a) (i) Define CMRR of a differential amplifier.
- (ii) For the circuit shown in fig. 9. Find out voltage, V_o .

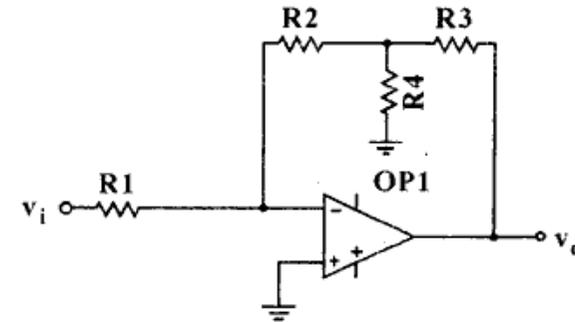


Fig. 9

- (b) (i) Convert the following numbers :
 - (1) $2D6_{16} = ()_2$
 - (2) $011010110_2 = ()_{16}$
- (ii) Convert the following function in to canonical forms :
 $Y = AB + AC + AD + BCD$
- (iii) Complete the following operations :
 - (1) $8_{16} + F_{16} = ()_{16}$
 - (2) $0001\ 0100 + 0011\ 1001 = ()_2$
 $0100\ 1111 - 0000101 = ()_2$



- (iv) Minimize the following function using Boolean algebra.

$$Y = \bar{A}BCD + ABC\bar{D} + AB\bar{C}D + ABCD + ABC\bar{D} + A\bar{B}CD + \bar{A}BCD + \bar{A}BC\bar{D}$$

- (c) (i) Draw the circuits of inverting amplifier, non-inverting amplifier and difference amplifier using Op-Amp. Derive the expression for output voltage.
- (ii) Draw the circuit of integrator and differentiator using Op-Amp, derive the expression for output.