

Printed Pages : 4

EEC201/ECE201

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3302

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.**(SEMESTER-II) THEORY EXAMINATION, 2011-12****ELECTRONICS ENGINEERING****Time : 3 Hours]****[Total Marks : 100****Note :** Answer **all** the Sections.**Section – A**1. Attempt **all** parts of this question :**10 × 2 = 20**

- (a) Distinguish between avalanche and zener breakdown.
- (b) For p type semiconductor dopants from 3rd group are typically employed. Can we use dopants from 2nd group ? Give reason.
- (c) Determine I_E , α and β of common base transistor circuit given $I_C = 7$ mA, $I_B = 0.1$ mA.
- (d) The thickness of base is typically smaller than emitter and base. Why ?
- (e) What is the basic difference between JFET and MOSFET ?
- (f) What do you mean by term slew rate in opamp ?
- (g) Convert 120_{10} to equivalent hexadecimal.
- (h) What do you mean by canonical form of a Boolean expression ?
- (i) How is voltage measured using CRO ?
- (j) Describe input characteristics of a digital voltmeter.

3302

1

P.T.O.

Section – B

2. Attempt any **three** parts of this question :

3 × 10 = 30

- (a) (i) Explain the formation of potential barrier across a p-n junction.
- (ii) Explain the function of the circuit of Fig. 1 and draw the output waveform.

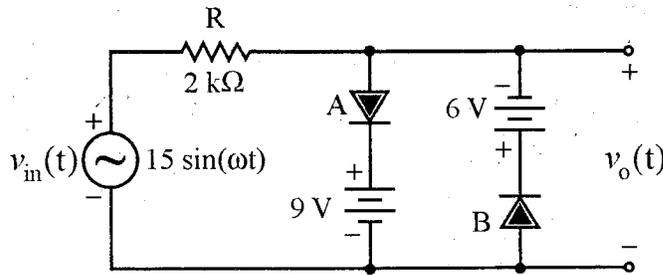


Fig. 1

- (b) (i) What is base width modulation ? How it affects the output characteristics of a transistor in CB and CE configuration ?
- (ii) The transistor in Fig. 2 has values of $h_{FE} = 100$. Determine the Q-point values of I_C and V_{CE} at both of these temperatures.

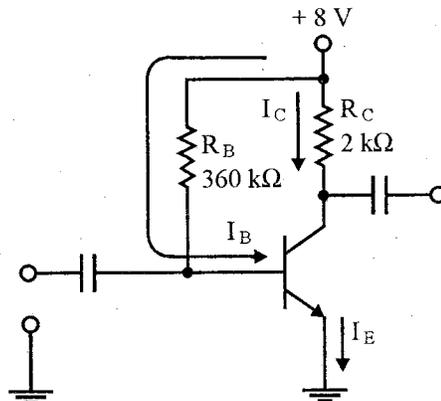


Fig. 2

- (c) (i) Describe different biasing schemes used in JFET amplifiers. State their advantages.
- (ii) Given $I_{DSS} = 9 \text{ mA}$ and $V_p = -3.5 \text{ V}$, determine I_D when $V_{GS} = 0 \text{ V}$ and $V_{GS} = -2 \text{ V}$.
- (d) (i) Represent the unsigned numbers 84 and 56 in BCD and then show the steps necessary to form their sum.
- (ii) Express $(10110.0101)_2$ in decimal.
- (e) (i). Explain how would you measure phase of signal from CRO.
- (ii) Describe the operating of CRO with neat block diagram.

Section – C

Attempt any **two** parts of each question :

5 × 10 = 50

3. (a) Determine V_o for the network for the input indicated.

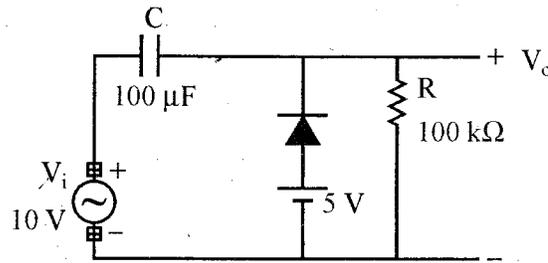


Fig. 3

- (b) Explain the working of centre tap full wave rectifier. What is the value of peak inverse voltage ?
- (c) Discuss the application of zener diode as shunt regulator.
4. (a) Draw hybrid equivalent of CE configuration and obtain expressions for A_i and A_v .
- (b) Why is transistor biasing required ? Describe different schemes of transistor biasing in CE n-p-n transistor circuit. State their advantages.
- (c) Determine R_i and R_o for the circuit of Fig. 4. Use the following parameters :

$h_{fe} = 110, h_{ie} = 1.6 \text{ k}\Omega, h_{re} = 0.0002$ and $h_{oe} = 20 \mu\text{A/V}, R_C = 4.7 \text{ k}\Omega, R_B = 470 \text{ k}\Omega$.

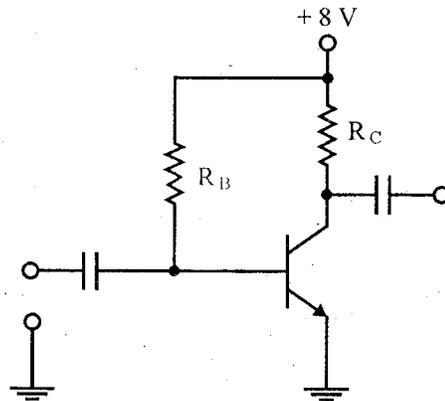


Fig. 4

5. (a) Explain the construction of depletion type NMOSFET and explain its output characteristics.
- (b) Draw the circuit diagram of an integrator using opamp and explain its working.
- (c) Describe ideal and practical opamp parameters.

6. (a) Implement an OR gate using NAND gates.
- (b) Simplify the following function with help of K map :
- $$F(A, B, C, D) = \sum(3, 5, 9, 11, 15) + d(2, 4, 6, 10)$$
- (c) Discuss the commutative and distributive postulates of Boolean algebra with example.
7. (a) Draw block diagram of digital multimeter and explain its working.
- (b) Discuss different controls of CRO.
- (c) What is function of time base circuit in CRO ? How will you measure the frequency of sinusoidal signal with help of CRO ?