

Printed Pages: 04

Sub Code: EEC 201

Paper Id: 131202Roll No.


B.Tech
(SEM II) THEORY EXAMINATION 2017-18
ELECTRONICS ENGINEERING

Time: 3 Hours**Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**


- a) Define the terms intrinsic concentration and energy band gap of a semiconductor material.
- b) Differentiate between avalanche and zener mechanisms related to zener breakdown.
- c) Establish the relationship between I_{CBO} and I_{CEO} .
- d) Define the drain to source saturation current of JFET
- e) Enlist the characteristics of an ideal operational amplifier (op-amp)
- f) Draw the circuit of a subtractor using op-amp and explain its working.
- g) Explain the concept of universal gates in Boolean algebra.
- h) What are logic gates? Explain the various types of logic gates with the help of logic symbols.
- i) What do you understand by Virtual ground in an op-amp?
- j) What are Lissajous figures? Why they are used?

SECTION B**2. Attempt any three of the following: 10 x 3 = 30**

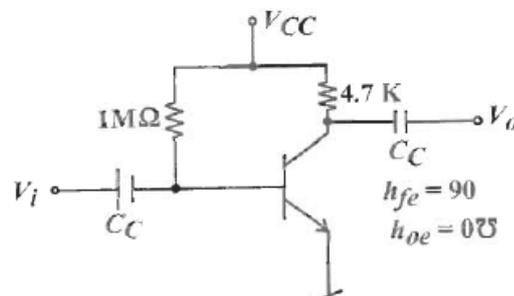- a) Define voltage regulation for a rectifier. What are ideal and practical values of voltage regulation for a rectifier? Calculate the voltage regulation for a full wave rectifier.
- b) Determine V_{CC} for the following circuit if the Voltage gain $A_v = -200$.



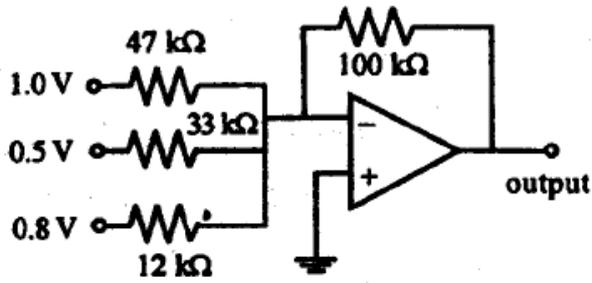- c) Write a short note Op-Amp as adders. Determine the output voltage for the given figure.




- d) What do you understand by number system? Describe the methods for converting an integer number in decimal number system to all other number systems. Use suitable examples.
- e) Explain the working and characteristic curve of Ramp type digital voltmeter with the help of a neat diagram.


SECTION C

3. Attempt any *one* part of the following: 10 x 1 = 10

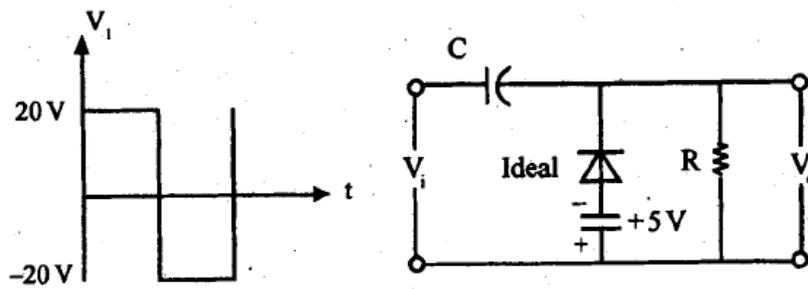(a) Sketch V_o of the following network as shown in Figure.




b) Determine the DC load voltage and ripple voltage for the circuit as shown in figure.

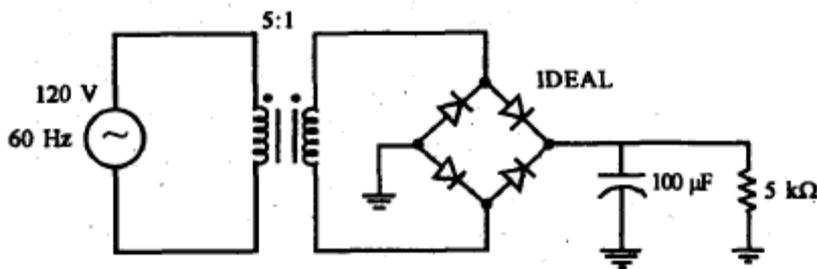


4. Attempt any *one* part of the following: 10 x 1 = 10

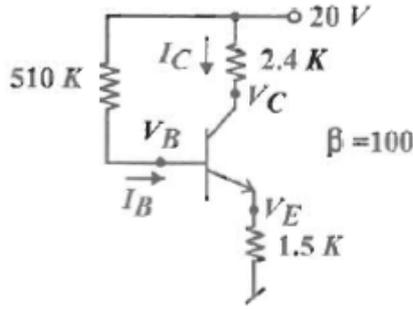(a) Determine I_C , V_E , V_B , V_C and I_B for the following circuit.




(b) A common collector amplifier has a potential divider bias using $V_{CC} = 10V$, $R_E = 4.3k\Omega$, $R_1 = R_2 = 10k\Omega$. Determine the voltage Gain for the following circuit.

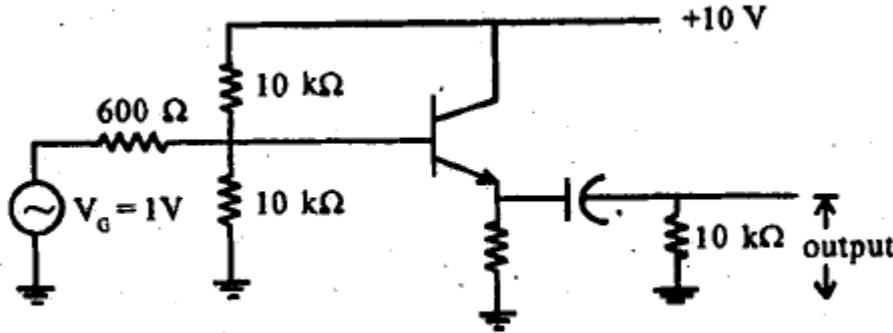

5. Attempt any *one* part of the following: 10 x 1 = 10

(a) Distinguish between enhancement type and depletion type MOSFETs. Draw the cross-section of N-channel enhancement type MOSFET. Explain and draw the transfer characteristics.

(b) Determine V_{GS} , I_D , V_{DS} , V_D , V_G and V_S for the following circuit

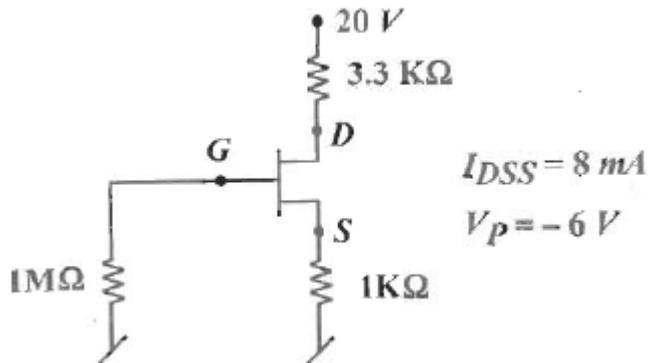

6. Attempt any *one* part of the following: 10 x 1 = 10

(a) (i) Write the various postulates for the Boolean algebra.
 (ii) Convert the following function in to canonical form and express the function as sum of minterms.

$$F(A, B, C, D) = (A'B'D + A'B'C + ADC)$$

(b) (i) Simplify the following Boolean expression using k-map:

$$f(a, b, c, d) = \sum m(5, 6, 7, 10, 14, 15) + d(9, 11)$$

- (ii) Simplify the following expression and implement with minimum NAND gate circuit.

$$f(A, B, C) = \overline{A}BC + A\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

7. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Explain the working of a digital multimeter with the help of a properly labeled block diagram. State some applications of digital multimeter
- (b) Describe the procedure for measuring the phase and frequency of an input signal using CRO?