

B. TECH.
(SEM II) THEORY EXAMINATION 2018-19
ELECTRONICS ENGINEERING

Time: 3 Hours

Total Marks: 100

Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.

2×10 = 20

- a. How depletion layer is formed in a PN junction?
- b. Calculate PIV of half wave and full wave rectifier.
- c. Calculate the collector and emitter current levels of a BJT with $\alpha=0.99$ and $I_B=20\mu A$.
- d. Why CE configuration is widely used in Amplifier circuits?
- e. Determine the value of g_m for a JFET when $I_{DSS}=8mA$, $V_P= -6V$ and biased at $V_{GS}=V_P/4$.
- f. Enlist the practical characteristics of OPAMP.
- g. Convert 101 into equivalent binary and octal.
- h. Why delay line is used in CRO?
- i. Compare analog and digital instruments.

SECTION B

2. Attempt any three of the following:

10 x 3 = 30

- a. (i) Draw and explain the working of Bridge rectifier with input and output waveforms.
- (ii) Draw the output waveform for the circuit shown in fig (1).

 


Fig (1)

- b. (i) Draw the common emitter (CE) circuit of a transistor. Sketch its input and output characteristics curve. Indicate its various region of operation.
- (ii) A junction transistor has the following h-parameter $h_{ie} = 2k\Omega$, $h_{re} = 1.6 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 50\mu A/V$. Determine Current Gain, Voltage Gain, Input Resistance, Output Resistance of the CE amplifier, if load resistance is $12 K\Omega$.
- c. (i) Draw and explain construction and working of n- channel JFET and also plot the drain and transfer characteristics curves.
- (ii). Calculate the output voltage V_0 for the circuit of fig (2). Given that $R_1 = 11 K\Omega$, $R_2 = 22 K\Omega$, $R_3 = 33 K\Omega$, $R_f = 132 K\Omega$, and $V_{in} = 20\mu V$.

 


Fig (2)

- d. (i) Convert the following numbers as indicated $(360)_8 = (\dots\dots\dots)_{16}$, $(10011.1101)_2 = (\dots\dots\dots)_8$ and $(222.62)_{10} = (\dots\dots\dots)_{16}$.
- (iii) Simplify the logic expression using Boolean algebra

$$f(A, B, C, D) = A \bar{B} \bar{C} D + \bar{A} \bar{B} D + BC \bar{D} + \bar{A} B + B \bar{C}$$
- e. (i) Draw the block diagram of Digital Volt Meter (DVM). Also explain the function of each block.
- (ii) Explain, how the signal pattern displayed over the CRO screen?

SECTION C

3. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Distinguish between Avalanche and Zener breakdown mechanism. Calculate I_R , I_Z , I_L and V_L for the network shown in fig (3) if $R_L=470 \Omega$.

 


Fig (3)

- (b) What is multiplier circuit? Draw the output waveform V_0 for the fig (4).

 



Fig (4)

4. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Draw the circuit for potential divider biasing with following parameters $R_1=8.1K\Omega$, $R_2=2.2K\Omega$, $R_C=2.7K\Omega$, $R_E=1.8K\Omega$, $\beta=120$, $V_{CC}=20V$. Also determine I_B , I_C , V_{CE} , V_E , V_C , V_B , and V_{BC} .
- (b) Compare CE, CB and CC configuration of a BJT.

5. Attempt any *one* part of the following: 10 x 1 = 10

 - (a) Sketch the structure of an n-channel depletion mode MOSFET. Explain the drain and transfer characteristics. And also explain how depletion type MOSFET works as enhancement type MOSFET.
- (b) Write short notes on Non inverting and Subtractor OPAMP. Find V_0 for the network shown in fig (5).



6. Attempt any *one* part of the following: 10 x 1 = 10
- (a) Reduce the function $f(A, B, C, D) = \sum m(1,3,7,11,15) + \sum d(0,2,4)$ using k-map.
 - (b) Briefly explain, why NAND and NOR gates are known as universal gates?
7. Attempt any *one* part of the following: 10 x 1 = 10
- (a) Draw the block diagram of Digital Multi Meter (DMM). Explain the function of each block.
 - (b) Draw the block diagram of CRO. Also explain the function of each block.