

Printed Pages : 4



NAG-301/AG-301

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 992301/993301

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) (ODD SEM.) THEORY
EXAMINATION, 2014-15

BASIC ELECTRONICS AND INSTRUMENTATION

Time : 3 Hours]

[Total Marks : 100

Note : Attempt question from all sections as per instruction.**SECTION - A**

1 Attempt all part of the questions. All parts **10×2=20**
carry equal marks :

- (a) Define the zenar and avalanche breakdown in p-n junction.
- (b) What the meant by depletion layer in p-n junction?
- (c) What is the effect of temperature on conductivity of a semiconductor?
- (d) What are called universal gates? Why are they called so?
- (e) Does a hole in a semiconductor contribute to a flow of current? If yes, how and if no, how?

992301/993301]

1

[Contd...

- (f) What the need for biasing a transistor?
- (g) Define positive logic and negative logic in logic design.
- (f) State the advantage of a digital instrumentations over a analog instruments.
- (h) Explain, why BJT are called bipolar devices and FET are called unipolar device?
- (i) What is the duality in Boolean algebra?

SECTION -B

2 Attempt any three questions. All question **10×3=30**
carry equal marks :

- (a) Explain the potential divider biasing circuit.
- (b) Draw the circuit diagram of transistor in CE configuration and sketch in output characteristics.
- (c) What are the advantage of the FET over a BJT ? Define pinch off voltage and drain voltage and drain resistance FET.
- (d) Explain the construction and characteristics of JFET.
- (e) Draw and explain V-I characteristics of P-N junction diode.

SECTION - C

- 3** (a) Write the characteristics of an ideal op-amp. How it is used as an integrator and summer? **10×1=10**

OR

- (b) Explain the basic construction, operation and characteristics of MOSFET.
- 4** (a) Explain the working of positive clipper and negative clamper circuit. **10×1=10**

OR

- (b) Explain the working of Half wave and Full wave rectifier. What are the advantage of full wave rectifier?
- 5** (a) Explain how frequency and phase can be measure using a CRO. And also describe the application of CRO. **10×1=10**

OR

- (b) Draw and explain input/output characteristics of CB configuration of BJT.
- 6** (a) What do you understand by don't care condition is it an advantage or disadvantage to include them in a map, explain with reasons? **10×1=10**

OR

- (b) Simplify the function using k-map
 $F(A,B,C,D) = \sum m(3,4,5,7,9,13,14,15) + \sum d(0,1,8,10)$.
 Implement the output using gates.

- 7 (a) Draw the block diagram of digital multimeter. Explain the operation of each block. **10×1=10**

OR

- (b) Draw the circuit of op-amp as a subtractor and find out the expression of output.
