

Printed pages:
Paper Id: 3025

Sub Code: EEC 309

Roll No.

--	--	--	--	--	--	--	--	--	--

B.TECH
(SEM III) THEORY EXAMINATION 2017-18
ANALOG AND DIGITAL ELECTRONICS

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief. 2 x 10 = 20

- a) Explain the operation of Schottky diode.
- b) What is photo diode? How it is different from a light emitting diode?
- c) Write the properties of negative feedback.
- d) Explain Amplifier transfer function.
- e) Describe the basic principle of an oscillator circuit.
- f) What are Crystal oscillators?
- g) Differentiate between a latch and flip-flop.
- h) Define Mod-N Counters. What does 'N' signify?
- i) Compare the features of RAM and ROM. List different types of RAM/ROM.
- j) Explain the function of Schmitt trigger.

SECTION B

2. Attempt any three of the following: 10 x 3 = 30

- a) Explain how a transistor can be used as a switch. What modification in the doping levels of various regions is required?
- b) Explain the basic principle of feedback amplifiers. Explain the circuits for series-series, series-shunt, shunt-series and shunt-shunt feedback amplifiers.
- c) Explain the principle of a sinusoidal oscillator. Describe the advantages of a crystal oscillator.
- d) Explain the basic principle of shift registers. Describe the functioning of a Universal Shift register as PIPO, SISO.
- e) Discuss the various types of Analog to Digital convertors and Digital to Analog Convertors.

SECTION C

3. Attempt any two parts of the following: 5 x 2 = 10

- a) What is a Varactor diode? Draw and describe its characteristics.
- b) Explain the construction of a tunnel diode. Explain tunneling effect?
- c) Explain the construction and principle of operation of LED. Give the applications of LED.

4. Attempt any one part of the following: 10 x 1 = 10

- a) Explain the low frequency response of common emitter configuration. Explain the functions of coupling and bypass capacitors.
- b) Explain the difference between negative feedback and positive feedback. Describe the advantages of negative feedback. Mention applications of the positive feedback.

- 5. Attempt any *two* parts of the following: **5 x 2 = 10****
- a) What are tuned oscillators? Explain the differences between Collpit and Hartley oscillators.
 - b) What is a phase shift oscillator? Derive the expression for the phase shift provided by an RC phase shift oscillator.
 - c) Explain the working of a Wein Bridge oscillator. Calculate the oscillator frequency and loop gain.
- 6. Attempt any *one* part of the following: **10 x 1 = 10****
- a) Implement a 16:1 MUX using 2:1 Multiplexers.
 - b) Explain the difference between ring counter and Johnson counter with a suitable diagram. Also draw the waveforms for the output of a Johnson counter.
- 7. Attempt any *one* part of the following: **10 x 1 = 10****
- a) (i) Differentiate between Astable, Monostable and Bistable multivibrators.
(ii) Describe the features and applications of Timer IC- 555.
 - b) Define voltage regulation. Distinguish between the series, shunt and switching voltage regulators. Which of this configuration has the best voltage regulation? Justify your answer.