

Printed pages: 02

Sub Code: REC309

Paper Id: 3 0 8 2

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech

**(SEM III) THEORY EXAMINATION 2017-18
ANALOG & DIGITAL ELECTRONICS**

Time: 3 Hours

Total Marks: 70

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A**1. Attempt all questions in brief. 2 x 7 = 14**

- a. What is SCR draw its characteristic?
- b. Why germanium is not used for the construction of photo diodes?
- c. What is a cascade amplifier?
- d. What are the drawbacks of negative feedback?
- e. Encode the decimal numbers 43 and 295 into BCD code.
- f. For the logic operation $f = A\bar{B}D + \bar{A}BC + B\bar{C}\bar{D}$ obtain the standard POS equation.
- g. What is the difference between EPROM and EEPROM?

SECTION B**2. Attempt any three of the following: 7 x 3 = 21**

- a. Explain basic structure of LED, its operation. Also calculate the LED voltage drop and current.
- b. Explain Common collector amplifier and find its input resistance, voltage and current gain.
- c. Discuss the effect of negative feedback of voltage gain , stability , distortion, bandwidth, output and input impedance of an amplifier in series shunt configuration.
- d. Realize a JK flip flop using NAND and NOR gate. Also give their truth table and wave forms.
- e. Explain universal shift registers in detail with the help of proper diagrams.

SECTION C**3. Attempt any one part of the following: 7 x 1 = 7**

- (a) Explain tunnel diode and phenomenon of tunneling. Also give the equivalent circuit, characteristic of tunnel diode and application.
- (b) Explain construction and working of Schottky diode. Draw its characteristic and write merits and demerits and applications.

4. Attempt any one part of the following: 7 x 1 = 7

- (a) What do mean by multistage amplifier? And derive the relation for the product of gain bandwidth.
- (b) Explain common emitter configuration as an amplifier and derive the relations for frequency response.

5. Attempt any one part of the following: 7 x 1 = 7

- (a) Sketch the circuit of Wien bridge. Derive the expression for frequency of oscillation. Does the oscillation take place with sustained oscillation?

- (b) What is a clap oscillator and its frequency of oscillation?
Determine the frequency of oscillations of a clap oscillator if the component values are as follows.
 $C_1 = 100\text{pf}$, $C_2 = 1.2\text{ nf}$, $C_3 = 12\text{pf}$ and $L_3 = 8\mu\text{H}$.

6. Attempt any one part of the following: 7 x 1 = 7

- (a) Design a half adder using multiplexer.
(b) Explain multiplexer and demultiplexer. Design a 32:1 multiplexer using two 16:1 multiplexer.

7. Attempt any one part of the following: 7 x 1 = 7

- (a) Differentiate between synchronous and asynchronous digital sequential circuit and design MOD-5 counter.
(b) Give the classification of semiconductor memory and explain the function of PLA in detail.