

B.TECH
(SEM-III) THEORY EXAMINATION 2019-20
ANALOG AND DIGITAL ELECTRONICS

Time: 3 Hours

Total Marks: 70


Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. **Attempt all questions in brief.** 7 x 2 = 14
- What is LED?
 - What is combinational circuit and sequential circuit?
 - How oscillators generate sustained oscillation?
 - What is the effect of capacitors in low frequency response?
 - What is volatile memory?
 - What is the basic difference between latch and flipflop?
 - Explain universal shift register.

SECTION B

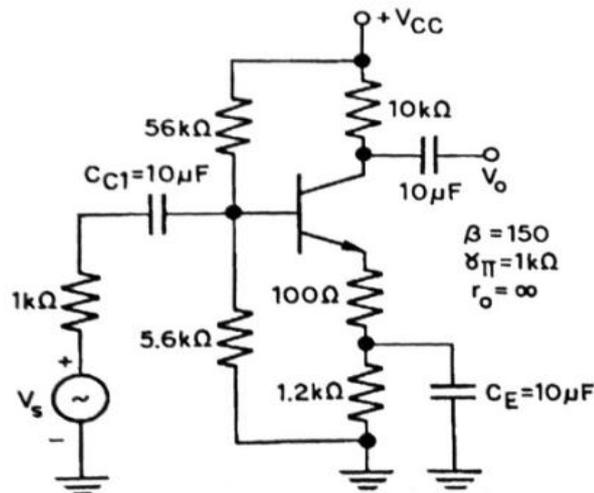2. **Attempt any three of the following:** 7 x 3 = 21
- Explain Tunnel diode. Draw its constructional details and characteristic curve.
 - For the BJT amplifier circuit shown in figure determine:
 - The lower half frequency due to coupling capacitor (i) C_{c1} (ii) C_E
 - The overall lower cut off frequency of the amplifier circuit



- Explain Wein bridge oscillator and also derive its frequency of oscillation.
- Implement the following Boolean function using SOP and draw the logic gates
 $F(A, B, C,) = \pi M(2,4,5,6)$
- With the neat logical diagram and timing diagram, explain the operation of 3 bit binary ripple up/down counter constructed using JK Flip flop

Paper Id:

130304

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

SECTION C3. **Attempt any one part of the following:** **7 x 1 = 7**

- (a) Explain power device SCR with its characteristics and applications. Compare it with Transistor.
- (b) What is a Schottky diode? Explain its characteristic and applications.

4. **Attempt any one part of the following:** **7 x 1 = 7**

- (a) Explain voltage series and current shunt feedback with the help of circuit and block diagram and derive the relation for gain and input/output impedance with and without feedback.
- (b) Explain Hartley oscillator and also determine its frequency of oscillation.

5. **Attempt any one parts of the following:** **7 x 1 = 7**

- (a) Explain multistage amplifier for RC coupled indicating its gain.
- (b) Discuss the high frequency equivalent circuit of FET and hence derive gain bandwidth product for any one configuration.

6. **Attempt any one parts of the following:** **7 x 1 = 7**

- (a) Convert SR Flip Flop to JK Flip flop? Draw the transition table in support of your answer.
- (b) What are Multiplexer? Design a 8 to 1 MUX using two 4 to 1 MUX.

7. **Attempt any one parts of the following:** **7 x 1 = 7**

- (a) Explain ROM with the help of block diagram? Compare RAM with ROM.
- (b) Design a combinational circuit using PAL for following Boolean Expression
 $X(A,B,C,D) = \sum(7,8,9,10,11,12,13,14,15)$
 $Z(A,B,C,D) = \sum(1,2,8,12,13)$