

**B.TECH**  
**(SEM-III) THEORY EXAMINATION 2019-20**  
**DIGITAL DESIGN**

**Time: 3 Hours****Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**

- a. What is the best Example of Digital system?
- b. Define Pair, Quad, and Octet?
- c. What are the basic Logic gates?
- d. Define Fan-in and Fan-out?
- e. What are the fundamental properties of Boolean algebra?
- f. Define Setup time?
- g. What is meant by K-Map or Karnaugh Map?
- h. What is a Multiplexer?
- i. Convert the Binary Code 111001 into octal and hexadecimal code.
- j. Perform the BCD addition of 126 and 105.

**SECTION B****2. Attempt any three of the following: 10x3=30**

- a. Explain the full adder circuit using logic diagram and Truth Table.
- b. Explain different logic gates families in digital circuits. Write a short note on Universal Gate.
- c. Solve the following Boolean functions by using K-Map : F  
 $(w,x,y,z) = \Sigma(0,1,4,5,6,8,9,10,12,13,14)$
- d. What is asynchronous counter? How would you design asynchronous counter?
- e. What are sequential logic circuits? Draw the logic diagram of JK Flip Flop.

**SECTION C****3. Attempt any one part of the following: 10x1=10**

- a. With the help of logic diagram, explain the 4 bit universal shift register using D flip-flops and 4:1 MUX.
- b. Write the truth table of the SR, JK, D & T flip-flops.

**4. Attempt any one part of the following: 10x1=10**

- a. Design a Mod 6 synchronous counter using D flip-flop and T flip-flop.
- b. Explain Mealy and Moore model of a clocked synchronous sequential network.

**5. Attempt any one part of the following: 10x1=10**

- a. Construct a state diagram for synchronous decade UP/DOWN counter. The mode control; 'M' decides the pattern of counting operation. When M=0 Counter counts UP and when M=1, counter counts DOWN. When counter reaches terminal count Y=1 (for UP count) and Z=1 (for DOWN count). Label the state diagram in M/YZ mode.
- b. Define state, present state, state diagram and state table.

**6. Attempt any one part of the following: 10x1=10**

- a. Implement 4 bit magnitude comparator.
- b. Simplify following logic function and realize using NOR gates.  
 $f(w,x,y,z) = \pi M(1,2,3,7,10,11) + d(0,15)$   
 $f(w,x,y,z) = \pi M(3,4,5,6,7,10,11,15)$

**7. Attempt any one part of the following: 10x1=10**

- a. Design a carry look ahead 4-bit parallel adder. Show that the time for addition is independent of the length of operands.
- b. Construct 16:1 MUX using 4:1 and 2:1 multiplexers and hence analyze using truth table.