

B TECH
(SEM-III) THEORY EXAMINATION 2018-19
DIGITAL LOGIC DESIGN

Time: 3 Hours**Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**1. Attempt all questions in brief. 2 x 10 = 20**

- a) What are the merits of hamming codes?
- b) Find the 'x' base of $(211)_x = (152)_8$?
- c) Distinguish Encoder and Decoder?
- d) What are the applications of Multiplexer?
- e) What is the programmable table of PLA?
- f) Why is a shift register restrictive?
- g) How is the capacity of a PLA specified?
- h) How many flip flop will be complemented in an 8-bit ripple counter to reach the next count after the following count 10110111?
- i) What is race around condition in JK flip-flop?
- j) What is race condition in asynchronous sequential Circuits?

SECTION B**2. Attempt any three of the following: 10 x 3 = 30**

- a) Reduce the Boolean expression-
 - (i) $ABC[AB + \overline{C}(BC + AC)]$
 - (ii) $\overline{A}BC + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$
- b) Design a logic circuit to generate even parity bit?
- c) Explain ROM and discuss their advantage and disadvantage?
- d) Write the design steps of synchronous counter?
- e) Discuss the analysis procedure of asynchronous sequential Circuits?

SECTION C**3. Attempt any one part of the following: 10 x 1 = 10**

- a) Minimize & implement the following multiple output function in SOP using K-map

$$f = \sum m(0, 2, 3, 4, 7, 9, 15) + d(6, 8, 11)$$
- b) Obtain the set of prime implicants for the Boolean expression

$$f = \sum m(0, 1, 6, 7, 8, 9, 13, 14, 15)$$
 using tabular method.

4. Attempt any one part of the following: 10 x 1 = 10

- a) Write the program table to implement a BCD to excess-3 code?
- b) Discuss the comparison among PROM, PLA and PAL?

5. Attempt any *one* part of the following:

10 x 1 = 10

- a) Implement a full adder using 3-line to 8line decoder?
- b) What is Hazards? Discuss its types and hazard free realization?

6. Attempt any *one* part of the following:

10 x 1 = 10

- a) Convert an SR flip flop into (i) T-flip flop (ii) JK flip flop?
- b) Discuss the application of Shift register?

7. Attempt any *one* part of the following:

10 x 1 = 10

- a) Find a circuit that has no Static hazards and implements the Boolean function
F (A, B, C, D) = (0, 2, 6, 7, 8, 10, 12)
- b) The Boolean functions for the inputs of an SR latch are

$$S = \overline{x_1} \overline{x_2} x_3 + x_2 x_2 x_3$$

$$R = \overline{x_2} x_1 + x_2 \overline{x_3}$$

Obtain the circuit diagram, using a minimum number of NAND gates?