

B TECH
(SEM-III) THEORY EXAMINATION 2019-20
DIGITAL LOGIC DESIGN

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**

- a. What is a Logic gate?
- b. What is meant by a bit, pair, and quad?
- c. What are the advantages and disadvantages of the K-Map Method?
- d. What are the differences between Combinational Circuits and Sequential Circuits?
- e. What are the applications of the octal number system?
- f. Define Hold time?
- g. What is Full-Adder?
- h. Implement the Boolean function $F = x'yz' + z$ using NOR gates only.
- i. Perform the BCD addition of 256 and 85.
- j. Convert the Gray Code 111001 into binary code.

SECTION B**2. Attempt any three of the following: 10x3=30**

- a. Define Multiplexer. Give the example of 4×1 multiplexer. Draw its truth table.
- b. Using active high output 3:8 line decoder, implement the following functions
 $f_1(A,B,C,D) = \sum m(0,1,2,5,7,11,15)$
 $f_2(A,B,C,D) = \prod m(1,3,4,11,13,14)$
- c. Design a carry look ahead 4-bit parallel adder. Show that the time for addition is independent of the length of operands
- d. Using Quine McCluskey method & PI reduction table, determine the minimal SOP expression for the following using decimal notation
 $f = \sum m(1,4,7,9,12,14) + \sum d(2,13)$
- e. Draw a circuit diagram of a CMOS inverter. Draw its transfer Characteristics and explain its operation.

SECTION C**3. Attempt any one part of the following: 10x1=10**

- a. Design a synchronous counter using JK flip-flops to count the sequence 0,1,2,4,5,6,0,1,2 use static diagram and state table
- b. Write the truth table of the SR, JK, D & T flip-flops.

4. Attempt any one part of the following: 10x1=10

- a. Design a combinational circuit that accepts a three bit number and generates an output binary number equal to the square of the input number.
- b. Design a BCD counter with JK flip flops.

5. Attempt any one part of the following: 10x1=10

- a. Simplify following logic function and realize using NOR gates.
 $f(w,x,y,z) = \pi M(1,2,3,7,10,11) + d(0,15)$
 $f(w,x,y,z) = \pi M(3,4,5,6,7,10,11,15)$
- b. Draw the basic circuit fo the DTL NAND gate. Explain the operation.

6. Attempt any one part of the following: 10x1=10

- a. Design a BCD to excess-3 code converter using ROM
- b. Convert the decimal number 246.8 to base 3, base 5 and base 7.

7. Attempt any one part of the following: 10x1=10

- a. Draw the basic flip flop circuit with NAND gates. Explain its operation.
- b. What is state reduction? Explain with a suitable example.