



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2023-24
DIGITAL SYSTEM DESIGN

TIME: 3HRS

M.MARKS: 70

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 7 = 14**

Q no.	Question	Marks
a.	What is the purpose of binary arithmetic in digital logic design?	2
b.	Explain the concept of signed magnitude representation.	2
c.	Explain the operation of a multiplexer.	2
d.	How does a full adder differ from a half adder?	2
e.	What are the basic building blocks of sequential logic circuits?	2
f.	What is fan-out in logic families?	2
g.	What are the key specifications of a DAC?	2

SECTION B**2. Attempt any three of the following:****7 x 3 = 21**

a.	Convert the following. Hexadecimal equivalent of the decimal number 256 Decimal equivalent of (123) ₉ 378.9310 to octal Convert A3BH and 2F3H into binary.	7
b.	Design a full adder by constructing the truth table and simplify the output equations.	
c.	Describe the operation of various flip-flops, including S-R, JK, D, and T flip-flops.	7
d.	Draw a circuit diagram of a CMOS inverter. Draw its transfer characteristics and explain its operation.	7
e.	Explain switched capacitor and give its applications.	7

SECTION C**3. Attempt any one part of the following:****7 x 1 = 7**

a.	Use Karnaugh maps to simplify the Boolean function: $F(A, B, C, D) = \sum(1, 2, 4, 6, 9, 10, 11, 12, 13, 14, 15)$.	7
b.	State and Prove Demorgan's theorem.	7

4. Attempt any one part of the following:**7 x 1 = 7**

a.	Implement a full adder using NAND gates.	7
b.	Design 2-bit magnitude comparator.	7

5. Attempt any one part of the following:**7 x 1 = 7**

a.	Compare and contrast Mealy and Moore machines and discuss their applications in digital systems design.	7
b.	Explain positive edge triggered D-flip-flop with the help of circuit diagram and waveforms.	7

6. Attempt any one part of the following:**7 x 1 = 7**

a.	Explain the characteristics and specifications of TTL NAND gates, including noise margin, propagation delay, fan-in, and fan-out.	7
b.	Describe the concept of programmable logic devices (PLDs) and explain how they are used for logic implementation in digital systems.	7

7. Attempt any one part of the following:**7 x 1 = 7**

a.	Explain the principle of operation of an R2R ladder DAC.	7
b.	Describe the principle of operation of a successive approximation ADC.	7