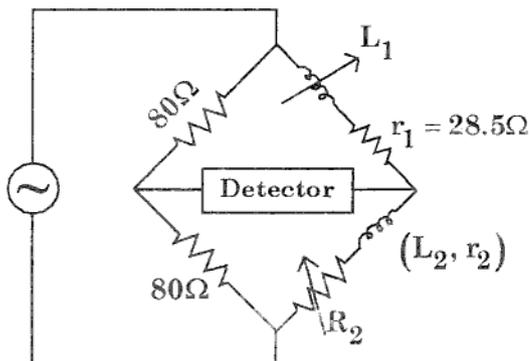


Explain how this instrument can be used for measurement of

- (i) Current upto 1 A
- (ii) Voltage upto 5 V.
- (e) Differentiate between the primary and secondary transducer.
- (f) Describe the method for measurement of temperature with use of RTD and Thermistor.

2 Attempt any **four** of the following : 5×4=20

- (a) Describe the working of a low voltage Schering bridge.
- (b) Explain briefly electronic multimeter.
- (c) Explain vector impedance-meter with the help of block diagram.
- (d) In a bridge shown in **figure** below the balance was obtained with $L_1 = 52.6 \text{ mH}$ and $R_2 = 1.68 \Omega$. Find the resistance and inductance of coil.



- (e) A circuit having an effective capacitance of 160 PF is tuned to a frequency of 1.2 MHz. In this circuit the current falls to 70.2% of its resonant value when the frequency of an e.m.f. of constant magnitude injected in series with the circuit deviates from the resonant frequency by 6 kHz. Calculate the Q factor and effective resistance of the circuit.
- (f) Discuss the circuit for measurement of power at radio frequencies.

3 Attempt any **two** parts of the following : $10 \times 2 = 20$

- (a) Describe the working of an integrating type digital voltmeter. A D/A converter has 6 bits and a reference voltage of 10 V. Calculate the minimum value of R such that the maximum value of output current does not exceed 10 mA. Find also the smallest quantized value of output current.
- (b) Explain the theory and working of LCDs. Describe the advantage of LEDs.
- (c) Draw the circuit of a digital frequency meter. Explain the difference between $3\frac{1}{2}$ digits and 4 digits displays.

4 Attempt any **two** parts of the following : $10 \times 2 = 20$

- (a) Describe the following for CRO circuit :
- (i) Blanking circuit
 - (ii) Z axis modulation
 - (iii) Astigmatism control
 - (iv) Time base generator.

- (b) (i) Derive the expression for vertical deflection of an electron beam in a CRT and sensitivity of CRT.
- (ii) Draw the Lessajous patterns for same voltage put frequency $f_x = \frac{7}{2} f_y$ inputs are connected to y and x plates of the oscilloscope respectively.
- (c) (i) An oscillation has an input capacitance 50 PF and resistance of $2\text{ M}\Omega$ and the voltage divider ratio of 10. What are the parameters of a high impedance probe?
- (ii) Write a short note on storage oscilloscope.

5 Attempt any **four** parts of the following : **5×4=20**

- (a) Discuss the function of wave analyzer.
- (b) Discuss the different types of analog instruments based on measurements.
- (c) Explain in brief spectrum analyzer.
- (d) Explain the working of function generator.
- (e) Write a short note on the working of Harmonic distortion meter.
- (f) Define the terms :
- (i) Accuracy
- (ii) Resolution
- (iii) Linearity
- (iv) Static sensitivity.