



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2023-24
NETWORK ANALYSIS AND SYNTHESIS

TIME: 3HRS

M.MARKS: 70

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.



2 x 7 = 14

Q no.	Question	Marks	CO
a.	What is node analysis, and how is it different from mesh analysis?	2	1
b.	Explain the significance of reactance in network analysis.	2	1
c.	State the superposition theorem.	2	2
d.	Define reciprocity theorem.	2	2
e.	Define singularity functions.	2	3
f.	Explain the concept of poles and zeros in network functions.	2	4
g.	What are the characteristics of band-reject filters?	2	5

SECTION B

2. Attempt any three of the following:

7 x 3 = 21

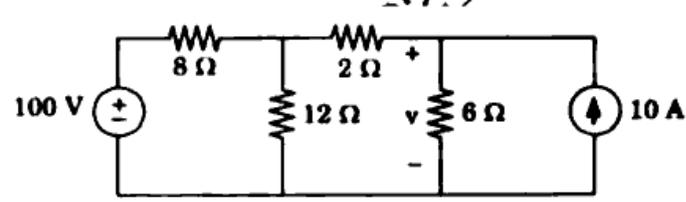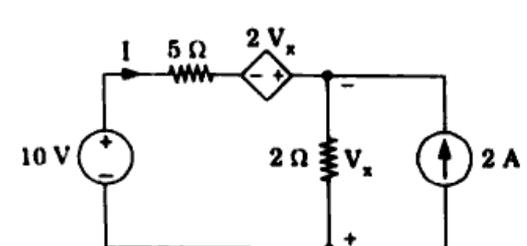Q no.	Question	Marks	CO
a.	For the circuit shown in Fig., determine the voltage using nodal analysis. 	7	1
b.	Calculate the current I shown in Fig. by using superposition theorem. 	7	2
c.	Explain step response of series RC circuit.	7	3
d.	Describe the concept of symmetry in two-port networks. Discuss how symmetry affects the port parameters and overall behavior of the network.	7	4
e.	State and prove convolution theorem.	7	5

SECTION C

3. Attempt any one part of the following:

7 x 1 = 7

Q no.	Question	Marks	CO
a.	Write the mesh current equations in the circuit shown in Fig., and determine the currents.	7	1




Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2023-24
NETWORK ANALYSIS AND SYNTHESIS

TIME: 3HRS

M.MARKS: 70

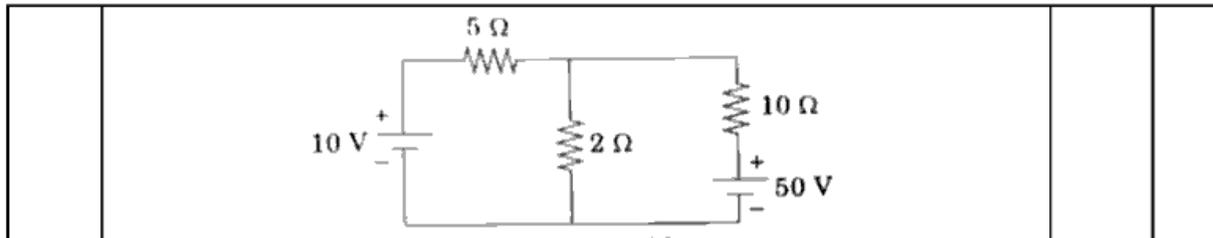


b. What do you mean by "duality of graph of the network"? Also mention its utilities and drawbacks. 7 1

4. Attempt any one part of the following: 7 x 1 = 7

Q no.	Question	Marks	CO
-------	----------	-------	----

a. State reciprocity theorem in AC network. 7 2

b. Find the Norton equivalent circuit of the circuit in Fig. at terminals a-b 7 2

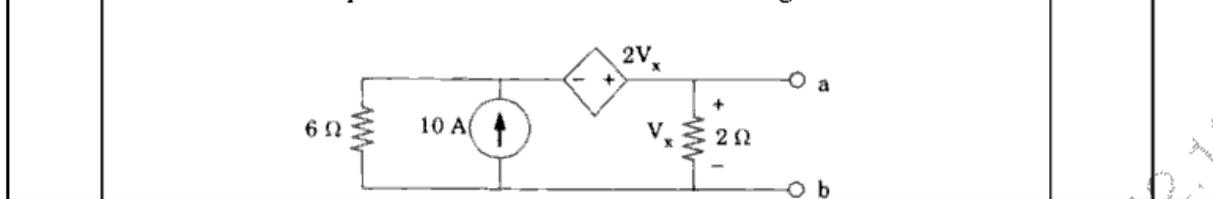

5. Attempt any one part of the following: 7 x 1 = 7

Q no.	Question	Marks	CO
-------	----------	-------	----

a. Write the Laplace transforms of:
i. Unit impulse
ii. Unit step
iii. Unit ramp and
iv. Parabolic functions. 7 3


b. What is inverse Laplace transform? Calculate inverse Laplace Transform of $e^{-5s} U(s)$. 7 3

6. Attempt any one part of the following: 7 x 1 = 7

Q no.	Question	Marks	CO
-------	----------	-------	----

a. Explain the concept of cascading two-port networks. Discuss any limitations or issues that may arise when cascading networks. 7 4

b. Determine the y and z parameters for a two-port network. 7 4

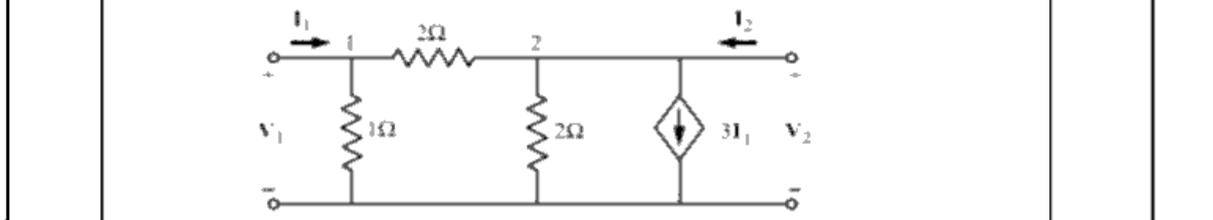

7. Attempt any one part of the following: 7 x 1 = 7

Q no.	Question	Marks	CO
-------	----------	-------	----

a. Explain quality factor. Also give relationship between bandwidth and quality factor of the circuit. 7 5

b. Derive an expression for parallel resonance and mention its salient features. 7 5