

B TECH
(SEM-III) THEORY EXAMINATION 2019-20
NETWORK ANALYSIS & SYNTHESIS

Time -3 Hour

Total Marks: 100

Note: Attempt all Section. If require any missing data: then choose suitably.

SECTION A

1 . Attempt all questions in brief

2x10= 20

- (a) State Thevenin theorem
- (b) What are the limitations of initial value theorem?
- (c) Write is the properties of RL functions.
- (d) Write applications name of 741IC used in network analysis.
- (e) Write is the necessary and sufficient condition for positive real function
- (f) Define open circuit parameters.
- (g) What do you mean by transfer impedance function?.
- (h) Explain the gate function used in network analysis.
- (i) State about zeros of transmission.
- (j) Check whether the given polynomial $P(s) = s^4 + s^3 + 4s^2 + 2s + 3$ is Hurwitz or not.


SECTION B

2. Attempt any three of the following

10x3= 30

- (a) What is mean by complex frequency? Explain all basic standard signal used in network analysis.
- (b) State and explain the different types of network used in network analysis.
- (c) Realize the following RLdriving point impedance function in
 - (a) Cauer first form
 - (b) Cauer second form
$$Z(s) = (s+4)(s+6)/(s+3)(s+5)$$

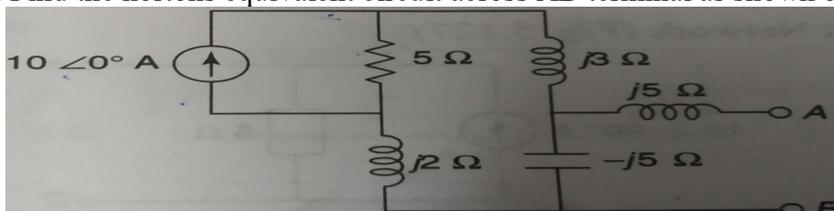(d) Find the nortons equivalent circuit across AB terminal as shown below



- (e) Prove any two properties of laplace transform and determine inverse laplace transform of the following function using convolution integral $F(s) = F_1(s) \cdot F_2(s) = 1/(s+c)(s+b)$.

SECTION C

3. Attempt any one parts of the following

10x1=10

(a) Calculate the current through $j3$ branch using Thevenin theorem in fig 2.

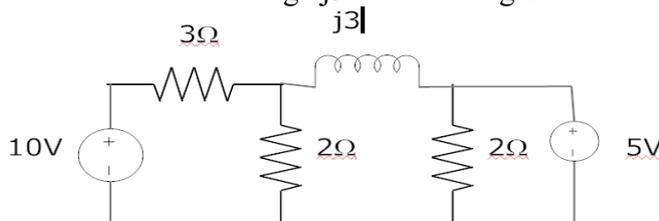


Fig 2

- (b) (i) Explain the Negative Impedance Converter in detail.
- (ii) Prove the Initial value theorem in complex frequency domain.

4. Attempt any one parts of the following 10x1=10

- (a) Explain the Series connection using Z parameters and parallel connection using y parameters and also prove for overall parameters using two model of two port network.
- (b) Write the all properties of positive real function and transfer function.

5. Attempt any one parts of the following 10x1=10

- (a) Determine the voltage transfer function $V_2(s) / V_1(s)$ for the network shown in fig 3.

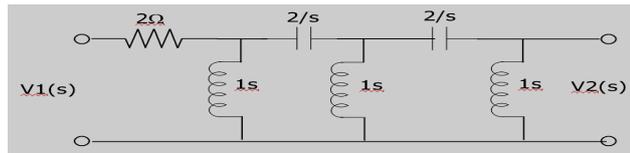


Fig 3

- (b) Synthesis the following function using 1 ohms termination
 $Z_{21}(s) = 2 / (s^3 + 3s^2 + 4s + 2)$

6. Attempt any one parts of the following 10x1=10

- (a) (i) Determine the Z parameters of circuit shown in figure 4.

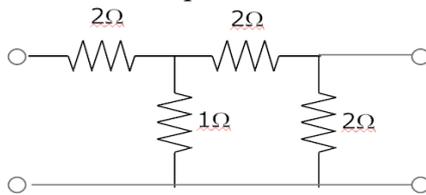


Fig 4

- (ii) Convert y parameters in terms of ABCD parameters.

- (b) (i) What is mean by active filter? Explain them using proper characteristics..
- (ii) Determine whether the function $Z(s) = (4s^2 + 3s + 3) / (4s^2 + 4s + 16)$ is positive real or not.

7. Attempt any one parts of the following 10x1=10

- (a) Using the foster (I) and foster (II) to synthesize the function:

$$Z(s) = 2(s^2 + 1)(s^2 + 9) / s(s^2 + 4)$$

- (b) Realize the following RL driving point impedance function in

- (i) Foster II form

- (ii) Cauer first form

$$Z(s) = (s + 1)(s + 3) / (s + 2)(s + 4)$$