

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3071

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

(SEM. III) ODD SEMESTER THEORY EXAMINATION  
2010-11

**PULSE AND DIGITAL ELECTRONICS***Time : 3 Hours**Total Marks : 100***Note :-** Attempt all questions. All questions carry equal marks.1. Attempt any **two** parts of the following : (10×2=20)

(a) Draw the circuit diagram of NMOS NOR gate and explain its operation. Why power dissipation in an NMOS NAND gate is lower than that of NMOS NOR gate ? Explain.

(b) Simplify the given function using tabular method  
 $F(A, B, C, D, E, F, G) = \Sigma(20, 28, 38, 39, 52, 60, 102, 103, 127)$ .  
Also implement the simplified function using basic gates.

(c) Simplify the given function using Karnaugh Map :

$$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 7)$$

$$d(5, 8, 10, 11, 15).$$

Also implement the simplified function using univesal gates only.

2. Attempt any **four** parts of the following : (5×4=20)

(a) Subtract 68 from 61 using BCD. Show all the steps.

(b) Design Full Subtractor. Also show truth table and circuit diagram.

(c) Design a 3-bit magnitude comparator.

(d) Design a full adder using 8 : 1 multiplexer.

(e) Implement the following function using PLA :

$$F_1(A, B, C) = \Sigma(0, 1, 6, 7)$$

$$F_2(A, B, C) = \Sigma(1, 2, 4, 6).$$

(f) A combinational circuit is defined by the following Boolean functions. Design circuit with a decoder and external gates :

$$Y_1 = \overline{A} \overline{B} \overline{C} + AC$$

$$Y_2 = A \overline{B} C + \overline{A} C.$$

3. Attempt any **four** parts of the following : (5×4=20)

(a) What is the difference between a latch and a flip-flop ? How basic latch operation is performed by NOT gates ?

(b) Convert D - flip-flop to T flip-flop.

(c) Design universal shift register.

(d) Design a Mod-5 synchronous counter.

(e) Design a four-stage Johnson Counter.

(f) Draw waveforms to illustrate how a serial binary number 1011 is loaded into a shift register.

4. Attempt any **four** parts of the following : (5×4=20)

(a) With the help of figure explain the operation of a bipolar SRAM cell and MOS SRAM cell.

(b) Explain basic semiconductor memory organization with the help of figure.

(c) Explain the working of dual slope ADC.

(d) Explain the operation of basic sample and hold circuit. Also state the advantages and applications of sample and hold circuits.

(e) What is attenuator ? Explain the under and over compensation in attenuators.

(f) Derive and draw the response of low pass RC circuit to step and sinusoidal waveforms.

5. Attempt any **four** parts of the following : (5×4=20)

(a) With reference to a PLL, define :

(i) Capture range

(ii) Lock range

(iii) Pull in time.

(b) For a noninverting regenerative comparator shown in Fig.1, calculate tripping voltages. Assume  $V_{sat} = \pm 12V$

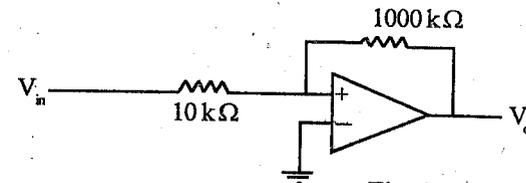


Fig. 1

- (c) Design a monostable for a pulse width of 10 ms by using IC 555.
- (d) Explain the working of IC 555 as an astable multivibrator with neat diagram.
- (e) Design an adjustable voltage regulator using IC 7805 to give variable output voltage from +5 V to +8 V with  $I_L = 1$  A.
- (f) Draw the diagram of series and shunt regulators and explain the working.