

B.TECH.**THIRD SEMESTER EXAMINATION, 2002-2003****SOLID STATE DEVICES & CIRCUITS**

Time : 3 Hours


Total Marks : 100

- Note :** (1) Attempt ALL the questions.
(2) All questions carry equal marks.
(3) Assume missing data suitably.

1. Attempt any FOUR from the following :— (5×4)

- (a) Draw the circuit diagram of a full-wave rectifier. Derive the expression for —
- (i) the d.c. load voltage;
 - (ii) the d.c. load current;
 - (iii) the d.c. diode voltage; and
 - (iv) the r.m.s. load current.
- (b) What will be the peak inverse voltage in a bridge rectifier with and without capacitor filter ? Explain why mainly capacitor is employed as filter. What will be the effect if large value capacitor is used as filter in a rectifier circuit ?
- (c) Draw the circuit of transistor in C.E. configuration. Sketch the output characteristic curves. Indicate the cut off, active and saturation regions and explain.
- (d) Is $|V_{BEsat}|$ greater or less than $|V_{CEsat}|$? Explain.
- (e) Draw the Ebers-Moll model for a $p-n-p$ transistor and explain.

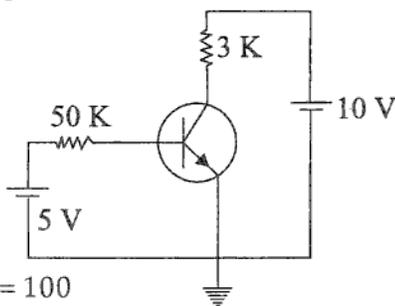
- (f) Find the region in which the Q point of following transistor circuit will lie :—



$$\begin{aligned} h_{FE} &= 100 \\ V_{CESat} &= 0.2 \text{ V} \\ V_{BESat} &= 0.8 \text{ V} \\ V_{BEactive} &= 0.7 \text{ V} \end{aligned}$$

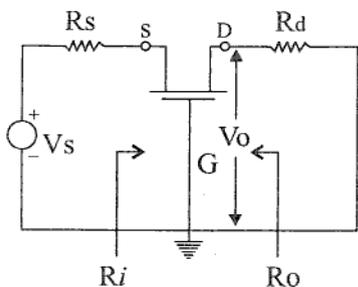2. Attempt any FOUR from the following :— (5×4)

- Define the pinch off voltage V_p , trans-conductance g_m , drain resistance r_d and amplification factor μ . Find relationship among μ , g_m and r_d .
- Compare the Bipolar Junction transistor and Junction Field effect transistor. Draw the circuit of a MOFET NOT circuit and explain its working.
- Draw the circuit diagram of a common source amplifier. Derive the expression for voltage gain at low frequencies. What is the maximum value of voltage gain A_v ?
- For the following circuit, find the expressions for
 - voltage gain,
 - input impedance,
 - output impedance :—




The power supplies are not shown. Neglect capacitances.

- (e) Draw the common source drain characteristic of a n-channel field effect transistor and explain the shape of curve.
- (f) Show that the transconductance g_m of a JFET is related to drain current I_{DS} by

$$g_m = \frac{2}{|V_P|} \sqrt{I_{DSS} I_{DS}}$$

3. Attempt any TWO from the following :— (10×2)

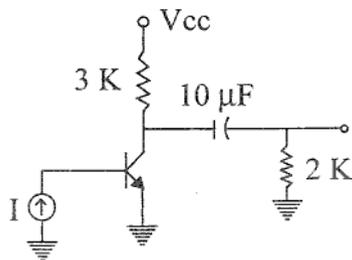- (a) Why is multistaging done at all ? List the advantages and disadvantages of multistaging. Draw the circuit diagram of a two stage R-C coupled amplifier and explain its operation. What will happen if both bypass capacitors are open circuited simultaneously?
- (b) How are the power amplifiers classified ? Explain each type. What are advantages of push-pull system ? Draw the circuit diagram of a class B push-pull amplifier and explain its working.
- (c) For a transistor CE stage, as shown in the following figure with $\frac{1}{h_{oe}} \equiv \infty$,



calculate the percentage tilt in the output, if input current I is a 100 Hz square wave. What is the lowest frequency square wave that will suffer less than 1% tilt ?

4. Attempt any TWO from the following :— (10×2)

(a) Draw the small signal hybrid π model at high frequency. Explain all the components of your model. Prove that $h_{fe} = g_m r_{b'e}$.

(b) Define f_β and f_τ . Derive the expressions for both f_β and f_τ and hence find the mathematical relation between f_β and f_τ .

(c) (i) Write short note on Cascode Amplifier.
 (ii) What do you mean by Tuned Amplifier? Draw the circuit diagram of a tuned amplifier and explain its working. What are the applications of tuned amplifier ?


5. Attempt any TWO of the following :— (10×2)

(a) What are the different characteristics of Amplifier that are modified with negative feedback ? Define desensitivity D and discuss the effect of large value of D .

(b) What are the Barkhausen conditions

required for sustained sinusoidal oscillation ? Sketch the circuit of a Wien bridge Oscillator. Derive the expressions for frequency of oscillations. Does the oscillation take place with balanced bridge ?

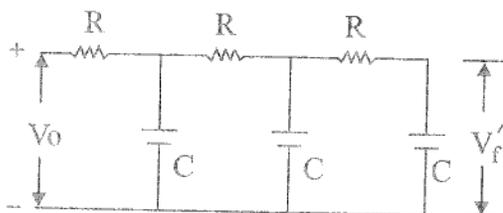- (c) For the following feedback network, find :—
- (i) the transfer function,
 - (ii) input impedance,
 - (iii) the frequency of oscillation and minimum amplifier voltage gain, if this network is used in a phase shift oscillator. (Assume no loading to take place),



•