

B. TECH.

THIRD SEMESTER EXAMINATION, 2003-2004
SOLID STATE DEVICES & CIRCUITS


Time : 3 Hours

Total Marks : 100

Note : Attempt ALL questions.

1. Attempt any FOUR of the following :— (5×4=20)

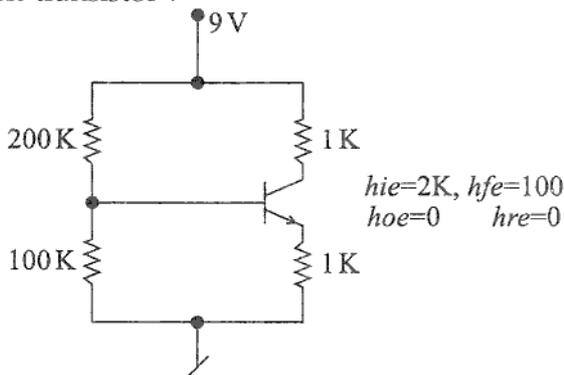
- (a) In the output of a fullwave rectifier, $L-C$ filter is connected with $C = 1000\mu\text{F}$, 16 V and $L=10$ mH. The resultant power supply is 6 V, 500 mA. Find the value of bleeder resistance.
- (b) Define the following diode ratings :—
- (i) PIV
 - (ii) I_{dc}
 - (iii) Repetitive peak current
 - (iv) Non-repetitive peak current
 - (v) Reverse recovery time
- (c) Why is potential divider biasing preferred over all other biasing circuits ?
- (d) Find I_C and V_{CE} for the following figure of silicon transistor :—



- (e) Explain Ebers-moll model of a transistor.
- (f) Explain all the different possible regions of operations of a transistor.
2. Answer any FOUR of the following :— (5×4=20)
- (a) Can a depletion type MOSFET operate in enhancement mod ? If yes, why and how, and if no, why ?
- (b) Describe, in detail, how a JFET is biased.
- (c) If $V_p = -4V$ and $I_{DSS} = 4\text{ mA}$ plot g_m versus I_{DSS} for a JFET.
- (d) How is an FET used as voltage variable resistance ? Explain.
- (e) Deduce the voltage gain of a common-source JFET amplifier.
- (f) Compare two devices JFET and MOSFET.
3. Answer any TWO of the following :— (10×2=20)
- (a) Draw a Darlington emitter follower. Explain why the input impedance is higher than that of a single-stage emitter follower. Add a bootstrap in biasing so that the biasing circuit does not reduce the input impedance drastically.
- (b) (i) Explain why even harmonics are not present in a push-pull amplifier.
- (ii) Give two additional advantages of this circuit over that of a single transistor amplifier.
- (c) Explain the effect of coupling and bypass capacitor in transistorised multistage RC-coupled amplifier. Draw its Gain-frequency plot.

4. Answer any TWO of the following :— (10×2=20)

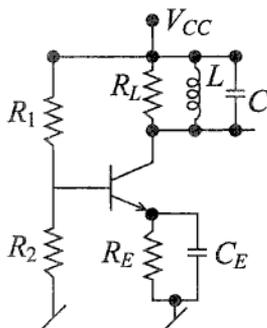
- (a) Draw and explain complete hybrid- π model of a Bipolar Junction Transistor.
- (b) What do you understand by CASCODE amplifier? Explain, in detail, with circuit and expression.
- (c) Find gain-bandwidth product of the following circuit :—



Assume and state simplifying conditions.

5. Answer any TWO of the following :— (10×2=20)

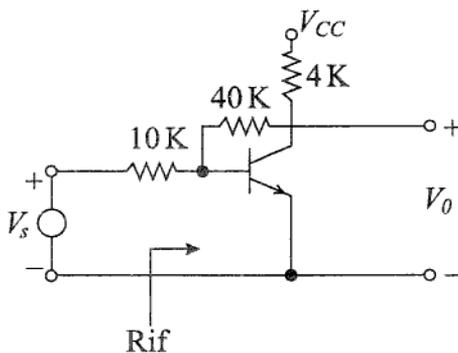- (a) For the circuit shown below, the transistor $h_{fe} = 50$, $h_{ie} = 1.1 K$ and $h_{oe} = h_{re} = 0$. Find (i) A_{vf} (ii) R_{if} .



-
- (b) Write notes on the following :—
- (i) Classification of Feedback
 - (ii) Barkhausen Criterion
- (c) (i) Deduce the condition of oscillation and frequency of oscillation of Wienbridge oscillator.
- (ii) How is the amplitude of this oscillator stabilized ? Explain.
-