



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3003

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) EXAMINATION, 2007-08

SWITCHING THEORY AND LOGIC DESIGN

Time : 3 Hours]

[Total Marks : 50

Note : Attempt all questions.

1 Attempt any **two** of the following : 5×2=10

(a) (i) Prove :

$$X \cdot Y + \bar{X} \cdot Z + Y \cdot Z = X \cdot Y + \bar{X} \cdot Z$$

(ii) Using Karnaugh map, find minimal sum of product expression for

$$f(A, B, C) = \sum(0, 1, 2, 4)$$

(b) Consider a logic expression :

$$F = \bar{W} \cdot Y + \bar{X} \cdot \bar{Y} + W \cdot X \cdot Z$$

Find all static hazards in the two level AND-OR or OR-AND circuit realization of above function.

(c) Design a hazard free circuit to realize the logic function of Q.1 (b)

- 2 Attempt any **two** parts of the following : $7 \times 2 = 14$
<http://www.uptuonline.com>
- (a) Each of the following arithmetic operations is correct in at least one number system. Determine one possible radix for each operation.
- (i) $1234 + 5432 = 6666$
- (ii) $41 / 3 = 3$
- (b) Suppose a $4n$ -bit number B is represented by an n -digit hexadecimal number H . Prove that the two's complement of B is represented by 16's complement of H .
- (c) Design a 3-bit carry look ahead adder. Compare it with ripple adder.

- 3 Attempt any **two** parts of the following : $6.5 \times 2 = 13$
- (a) Design a synchronous mod-5 counter using J-K flip-flops.
- (b) What is the problem of 1s and 0s catching in master slave JK flip-flop ? How is it solved in triggered J-K flip-flop ?
- (c) Write the excitation equations, transition table and output table for following clocked synchronous state machine :

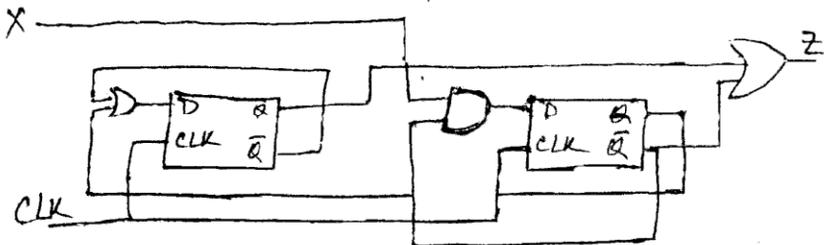


Fig. 1

Attempt any **two** parts of the following : $6.5 \times 2 = 13$

- (a) Represent the number $(+48.5)_{10}$ as a floating point binary number with 32 bits. The normalized fraction mantissa has 20 bits plus sign and the exponent has 10 bits plus sign. <http://www.uptuonline.com>
- (b) Define parity groups for a distance-3 hamming code with 11 information bits.
- (c) Draw the circuit of a positive edge-triggered D flip-flop with preset and clear using NAND gates. Derive its excitation equations and construct a transition table. <http://www.onlineQP.com>