

(Following Paper ID and Roll No. to be filled in your Answer Book)

Paper ID: 131304

Roll No.

B. Tech.

(SEM. III) THEORY EXAMINATION, 2015-16

SWITCHING THEORY & LOGIC DESIGN

[Time: 3 hours]

[Total Marks: 100]

Section-A

1. Attempt all parts. All parts carry equal marks. Write answer of each part in short. (10×2=20)
 - (a) Write the difference between Decoder and Demultiplexer.
 - (b) Perform the subtraction using 2's complement 46-23
 - (c) Realize an EX-OR gate using NAND gates only.
 - (d) How many address lines and data I/O lines are required for a 16K X 12 memory?
 - (e) Simplify the following Boolean expression to a minimum number of literals:

$$(x'y'+z')'+z+xy+wz$$
 - (f) Differentiate between Asynchronous and Synchronous Sequential Circuits.

- (g) What are the required no. of flip flops in a MOD-16 Asynchronous Counter, MOD-16 Synchronous Counter, MOD-16 Ring Counter, MOD-16 Johnson Counter?
- (h) Design a Half Adder using Multiplexer.
- (i) Convert the decimal number 32.75 in Octal, Binary, Hexadecimal, Gray.
- (j) Draw Master Slave Flip-Flop.

Section-B

Attempt any five questions from this section. (10×5=50)

2. Design a 4-bit magnitude comparator using one bit comparator modules.
3. Prepare hamming Code for the message "01001001010" assuming even parity. Also explain error detection and correction capabilities at the receiver by assuming an error in any of the received bits.
4. Using a decoder and external gates, design the combinational circuit defined by the following three boolean functions:

$$F_1 = x'yz' + xz$$

$$F_2 = xy'z' + x'y$$

$$F_3 = x'y'z' + xy$$

5. Design a 3-bit binary to Gray Code converter using PLA.
6. Draw and explain 4-bit Universal shift register.
7. Describe the hazards in digital Circuits. How are these removed?
8. What do you understand by state reduction? Reduce the following state diagram.

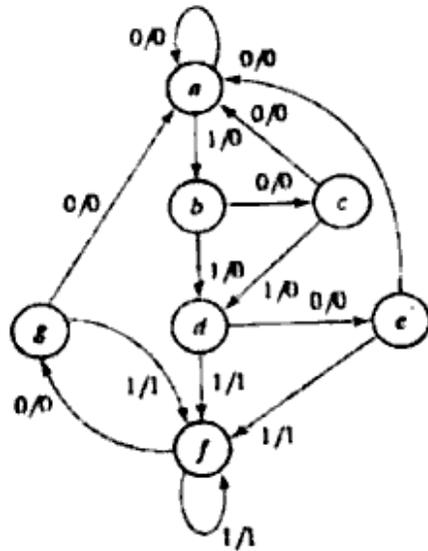


Figure 1

9. Derive the State Table and State Diagram for the sequential Circuit shown in figure 2:

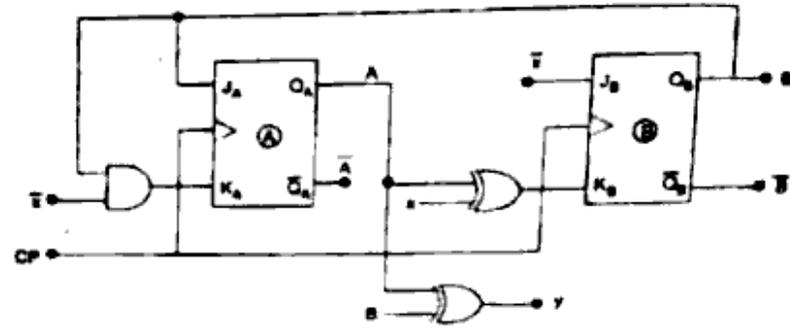


Figure 2

uptuonline.com

Section-C

Attempt any two questions from this section. (15 = 2=30)

10. Minimize the following using Quine McCluskey method:

$$F (W, X, Y, Z) = \sum (0, 3, 5, 6, 7, 10, 12, 13) + \sum d (2, 9, 15)$$
11. (a) Design a 3-bit Asynchronous UP-Down Counter using T-Flip-Flop.
 (b) Design a Full Adder using two Half Adders.

- 12 Design the clocked sequential circuit for the following state diagram using JK Flip-Flops.

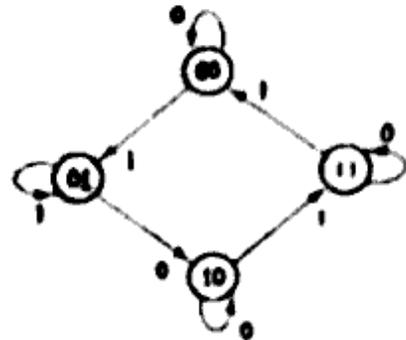


Figure 3

uptuonline.com