

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3072

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

THIRD SEMESTER EXAMINATION, 2006-07

SWITCHING THEORY

Time : 3 Hours

Total Marks : 100

- Note :**
- (i) Attempt *ALL* questions.
 - (ii) All questions carry equal marks.
 - (iii) In case of numerical problems assume data wherever not provided.
 - (iv) Be precise in your answer.

1. Attempt *any four* parts of the following : (5×4=20)

- (a) Convert the base-7 number $(3\ 5\ 6\ 1\ 4)_7$ to base-12.
- (b) Simplify the following Boolean expression which represent the output of a logical decision circuit :
$$f(A, B, C, D) = (AB + C + D)(\bar{C} + D)(\bar{C} + D + E)$$
- (c) Perform the following arithmetic operations in BCD numbers :
 - (i) $954 + 463$
 - (ii) $893 - 647$

- (d) Minimize the following function by Tabular method :

$$f(w, x, y, z) = \sum m(1, 4, 8, 9, 13, 14, 15) + d(2, 3, 11, 12)$$

- (e) Determine minimal sum of product form for the following multiple output system (using K-map or Tabular method) :

$$f(A, B, C, D, E) = \sum m(0, 1, 2, 3, 6, 7, 14, 15, 17, 19, 31)$$

- (f) Write notes on Hamming code.

2. Attempt *any four* parts of the following : (5x4=20)

- (a) What are the different types of parallel adders ? Explain carry save and carry look-ahead adders.

- (b) Using four-input multiplexers, implement the following functions :

(i) $f(A, B, C) = \sum m(0, 2, 3, 5, 7)$ control variables A and B.

(ii) $f(A, B, C) = \sum m(1, 3, 4, 6, 7)$ control variables B and C.

- (c) Design a code converter that converts a decimal digit from the 8 - 4 - 2 - 1 code.

- (d) How will you use ROM as decoder ? Justify your answer.

- (e) Design a two digit BCD adder with the help of 4-bit binary adders.

- (f) Explain the following :
- (i) Amplitude comparator
 - (ii) PLA

3. Attempt *any two* parts of the following : (10x2=20)

- (a) Describe the following in brief :
- (i) Excitation table and next state equation of FFs.
 - (ii) Design of sequential circuits using flow-chart.
- (b) Design a synchronous counter using J-K flip-flops for the following input sequences :

A	B	C
0	0	0
1	0	1
1	1	0
1	1	1
0	1	1
0	1	0
0	0	0

this repeats

- (c) Answer the following :
- (i) What are the steps for the analysis of asynchronous sequential circuit ?
 - (ii) Define ASM action blocks.
 - (iii) How do you convert the state diagram to ASM chart ?

4. Attempt *any two* parts of the following : (10x2=20)

- (a) What is meant by open collector output of TTL gate ? What is its utility ? Draw the circuit showing open collector output and pull-up resistor. Explain its operation.

What are the applications of open collector output ?

- (b) What are the advantages of BiCMOS logic circuits ? Draw the circuits of BiCMOS NAND and NOR gates. Explain their operations.

Draw a circuit diagram to interface CMOS to TTL.

- (c) Answer the following :

(i) Write merits/demerits of different logic families.

(ii) Explain the parameters used to characterize logic families.

(iii) How will you determine NAND gate delay in the laboratory ?

5. Attempt *any two* parts of the following : (10x2=20)

- (a) Plot K-map of the following functions :

(i) $f(A, B, C, D) = \Sigma m(0, 2, 4, 5, 6, 8, 9, 11, 12, 14, 15)$ and

(ii) $f(A, B, C, D) = \Sigma m(3, 4, 5, 6, 11, 12, 13, 14, 15)$

Determine hazard free implementation in both above cases, using :

(1) NAND gates

(2) NOR gates

It can be assumed that gate having a maximum Fan-in of three.

- (b) Develop a fault detection table for the circuit shown in figure 5 (b).

 


Figure 5 (b)

- (c) Write short notes on the following :
- Formation of memory banks
 - Static and dynamic memories

- o O o -