

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3072

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) ODD SEMESTER THEORY EXAMINATION

2010-11

SWITCHING THEORY*Time : 3 Hours**Total Marks : 100***Note :** Attempt **all** the questions. All questions carry equal marks.

1. Attempt any **four** parts of the following : **(5×4=20)**
 - (a) Convert binary 11010111.110 to decimal, octal and hexadecimal.
 - (b) Subtract 61 from 68 using BCD. Also show all the necessary steps.
 - (c) Using Tabular method and algebraic solution of P.I. table, obtain minimal realization of a function shown below :

$$F(A, B, C, D, E) = \Sigma m(13, 15, 17, 18, 19, 20, 21, 23, 25, 27, 29, 31) + \Sigma d(1, 2, 12, 24).$$
 - (d) How does parity help in error-detection ? Explain.
 - (e) Using boolean postulates, prove DeMorgan's theorem.
 - (f) What are universal gates ? Why they called so ? Explain with example.

2. Attempt any **four** parts of the following : **(5×4=20)**
 - (a) Design a full subtractor.
 - (b) Design a 4-bit magnitude comparator.
 - (c) Design a binary to Gray code converter.

- (d) Design a full adder with a decoder and two OR-gates.
 (e) A ROM is to be used to implement the boolean functions :

$$F_1(A, B, C, D) = ABCD + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$F_2(A, B, C, D) = (A + B) + (\bar{A} + \bar{B} + C)$$

$$F_3(A, B, C, D) = \Sigma m(13, 15) + \Sigma d(3, 5)$$

What is the minimum size of the ROM required ?

- (f) Implement the following functions using PLA :

$$F_1 = \bar{A}\bar{B} + AC$$

$$F_2 = AC + BC$$

3. Attempt any two parts of the following : (10×2=20)

- (a) (I) Convert a D-FF to a T-FF.
 (II) Draw a neat diagram of master slave JK FF. Explain how race around condition is avoided using master-slave JK flip-flop.
 (b) (I) Design a universal shift register.
 (II) Draw the ASM chart for a binary multiplier.
 (c) Design a JK flip-flop asynchronous sequential circuit that has two inputs and single output. The circuit is required to give an output equal to 1 if and only if the same input variable changes two or more times consecutively.

4. Attempt any four parts of the following : (5×4=20)

- (a) Explain the AC noise margin and DC noise margin.
 (b) What is CMOS ? Why its use in digital circuit is advantageous ?
 (c) Why FAN OUT of ECL is higher and propagation delay is lower ?

- (d) Explain the interfacing of CMOS to TTL logic gate.
 (e) With the help of circuit diagram explain CMOS inverter.
 (f) What is three state logic ? Draw the circuit diagram of three state NAND gate and explain its operation.

5. Attempt any four parts of the following : (5×4=20)

- (a) Define Hazard and find the hazard free realization of the combinational circuit :

$$Y = \bar{A}\bar{B} + BD$$

- (b) Discuss the fault table method for fault detection in digital circuit.
 (c) Given two 2K × 8 ROM ICs and two 2K × 8 RAM ICs. Obtain a memory system of 8K × 8 bits.
 (d) With the help of diagram, explain the operation of a bipolar SRAM cell.
 (e) Explain how a multiplexer can be used as ROM ?
 (f) Explain the basic structure of a EPROM cell ? Why they are so popular ?