

Printed Pages: 02

Sub Code: NEC409A

Paper Id:

131427

Roll No.

--	--	--	--	--	--	--	--	--	--

**(SEM. IV) THEORY EXAMINATION 2017-18
ANALOG AND DIGITAL ELECTRONICS****Time: 3 Hours****Total Marks: 100**

- Note:** 1. Attempt all Sections.
2. Assume any missing data.

SECTION A

- 1. Attempt all questions in brief. 2 x10 = 20**
- a. What are the different materials used for the manufacturing of LED?
 - b. Explain V-I characteristics of tunnel diode.
 - c. What is the necessity of frequency response analysis?
 - d. What are the advantages of introducing negative feedback?
 - e. State the Barkhausen criterion for an oscillator.
 - f. Define piezoelectric effect.
 - g. Compare combinational and sequential logic circuits.
 - h. What is the difference between Decoder and Demultiplexer.
 - i. Write short note on Schmitt trigger with diagram?
 - j. Explain PROM in brief.

SECTION B

- 2. Attempt any three of the following: 10 x 3 = 30**
- a. Explain the principle and working of light emitting diode (LED) with V-I characteristics. An LED is connected across a voltage source of +10 V through a series resistance of 820 Ω . Calculate the LED current. Assume the voltage drop across an LED of 15 V.
 - b. Distinguish between current feedback and voltage feedback with appropriate circuit /block diagram.
 - c. Explain Hartly oscillator and derive the equation for oscillation?
 - d. Explain the operation of master slave flip flop and show how the race around condition is eliminated.
 - e. Explain the organization of RAM with the help of neat diagram. Also describe the switching regulators.

SECTION C

- 3. Attempt any one parts of the following: 10 x 1 = 10**
- a. What is photodiode? Draw typical I-V characteristic curves at two illumination levels and explain how does it work as a photo resistor?
 - b. With the help of output characteristics explain how a transistor is used as a switch.
- 4. Attempt any one parts of the following: 10 x 1 = 10**
- a) Draw and explain high frequency equivalent circuit of the typical RC coupled common emitter amplifier.

- b) Describe the properties of series-shunt and shunt-shunt feedback amplifier. List five characteristics of an amplifier which are modified by negative feedback.

5. Attempt any one parts of the following: 10 x 1 = 10

- a) Draw a neat diagram of phase shift oscillator using BJT. Derive an expression for its frequency of oscillation.
- b) Explain the properties of a quartz crystal which are responsible for its use in an oscillator.

6. Attempt any one parts of the following: 10 x 1 = 10

- a) Draw and explain the 4-bit SISO, SIPO, PISO and PIPO shift register with its waveforms.
- b) Design a 3-bit synchronous counter using D-flip flop.

7. Attempt any one parts of the following: 10 x 1 = 10

- a) Explain A/D convertor using voltage to frequency convertor. Describe any one method of A/D convertor.
- b) What are the voltage regulators? Discuss the working of shunt and series Op-Amp based voltage regulators.