

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0321

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. IV) THEORY EXAMINATION 2010-11

ELECTRONIC CIRCUITS

Time : 3 Hours

Total Marks : 100

Note :- (1) Attempt *all* questions.

(2) All questions carry equal marks.

1. Attempt any **FOUR** parts of the following :— (4×5)
 - (a) Draw the circuit of difference amplifier using OP-AMP and apply superposition to determine the common mode gain expression.
 - (b) Draw the circuit diagram of inverting weighted summer calculate the output voltage for the same.
 - (c) Derive the expression for closed loop gain of non-inverting configuration of OP-AMP. What are its characteristics ? Discuss the effect of finite open loop gain.
 - (d) (i) Using non-inverting input draw the practical circuits of
 - (i) VCVS
 - (ii) CCVS
 - (ii) An OP-AMP having 106dB gain at dc and a single pole frequency response with $f_1 = 2$ MHz is used to design a non-inverting amplifier with nominal dc gain of 100.

Find the 3dB frequency of the closed loop gain.

(e) Define :—

- (i) Slew rate
- (ii) Half power bandwidth.

An OP-AMP has a rated output voltage of $\pm 10V$ and slew rate of $1 V/\mu S$. What is the Half power bandwidth if an input sinusoid with frequency $f = 5 f_M$ is applied to a unity gain follower constructed using this OP-AMP. What is the maximum possible amplitude that can be accommodated at output without incurring SR distortion ?

(f) What is "Input Bias current" of an OP-AMP ? How its effect can be reduced by connecting a resistance in the non-inverting terminal explain with mathematical expression.

2. Attempt any TWO parts of the following :— (2×10)

(a) (i) Name the different biasing methods of MOSFET. Describe in detail the biasing using a constant current source. Implement this biasing for the application of current mirror.

(ii) A MOSFET is to operate at $I_D = 0.1 \text{ mA}$ and to have $g_m = 1 \text{ mA/V}$ if $K'_n = 50 \mu A/V^2$. Find the required W/L ratio and overdrive voltage.

(b) Explain the working of common source amplifier with a resistance connected in source lead. Draw its small signal equivalent circuit neglecting r_o and deduce the expression for overall voltage gain.

- (c) (i) Design the circuit given in Fig. 1 to obtain a current I_D of $80 \mu\text{A}$. Find the value required for R and find the dc voltage V_D . Let the NMOS transistor have $V_t = 0.6 \text{ V}$, $\mu_n \cdot C_{ox} = 2000 \mu\text{A}/\text{V}^2$, $L = 0.8 \mu\text{m}$ and $W = 4 \mu\text{m}$. Assume $\lambda = 0$.

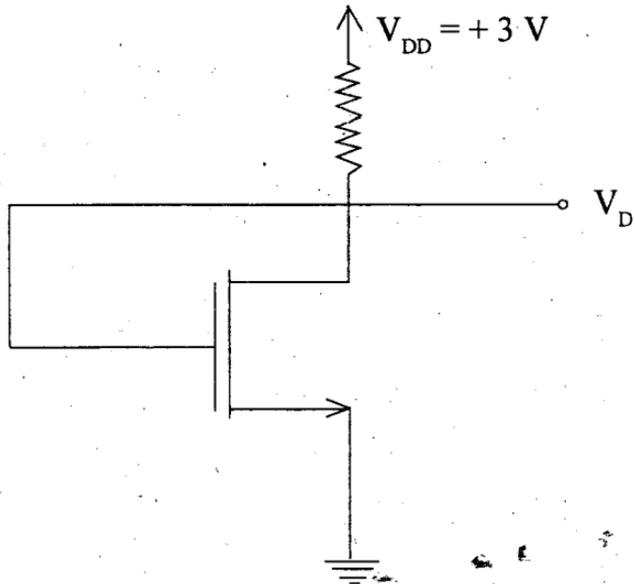


Fig. 1

- (ii) Re-design the circuit given in Fig. 1 to double the value of I_D without changing V_D . Give and values of W/L and R .
3. Attempt any **TWO** parts of the following :— (2×10)
- (a) Draw the circuit diagram of CE amplifier. Replacing the transistor with its hybrid Π model deduce the expression for its voltage gain.
- (b) (i) Discuss the various internal capacitances in detail for BJT.

- (ii) Draw the high frequency hybrid Π model of BJT.
Derive the expression given below :

$$f_T = \frac{g_m}{2\pi (C_{\Pi} + C_{\mu})}$$

- (c) Write the steps through which small signal equivalent circuit model can be used in the analysis of transistor amplifier.

Analyze the transistor amplifier given in Fig. 2 to determine its voltage gain. Assume $\beta = 100$.

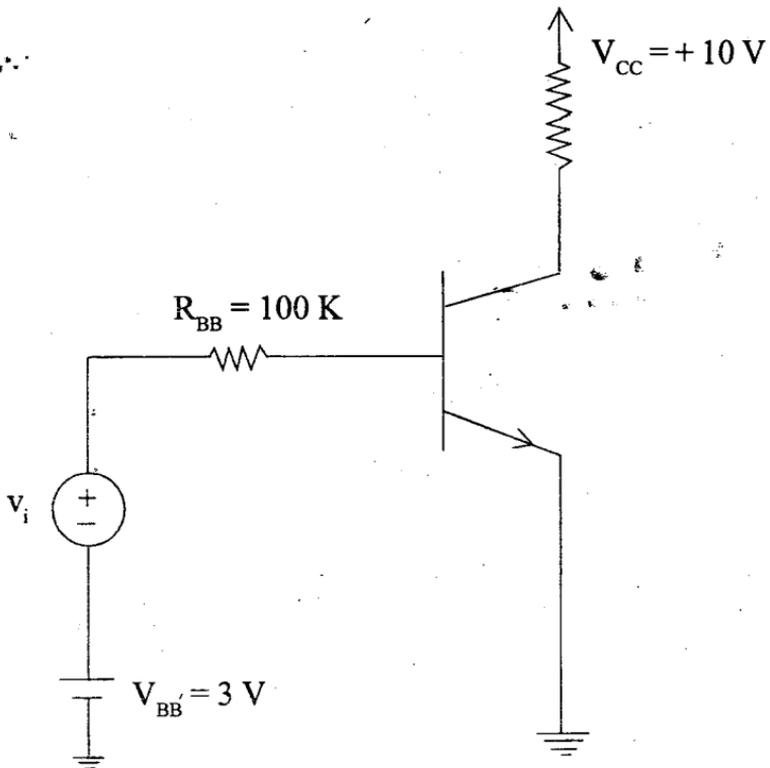


Fig. 2

4. Attempt any **TWO** parts of the following :— (2×10)
- (a) Write the features of differential amplifier. Draw the circuit of MOS differential pair configuration and describe its common mode operation for the determination of over drive voltage.
- (b) For a MOS amplifier with differential input, prove that $g_m = \frac{I}{V_{OV}}$ where symbols have their usual meaning.
- (c) (i) Explain the advantages of an active load. Draw a circuit of MOS differential amplifier with active load.
- (ii) An N MOS balanced output differential amplifier is operated at a bias tail current of 0.5 mA and has a $\frac{W}{L}$ ratio of 50, $\mu_n C_{ox} = 250 \mu A/V^2$ and $R_D = 4 \text{ k}\Omega$. Find g_m and A_d assume $\lambda = 0$.
5. Answer any **FOUR** parts of the following :— (4×5)
- (a) Mention the advantages of negative feedback and discuss its effect on :
- (i) Frequency response and bandwidth expression.
- (ii) Non-linear distortion.
- (b) Explain the working of trans-conductance amplifier using BJT and derive the expression for closed loop trans-conductance.

- (c) For the MOS source follower shown in Fig. 3, calculate the value of A_{vP} , R_{iP} , R_{oP} and β .

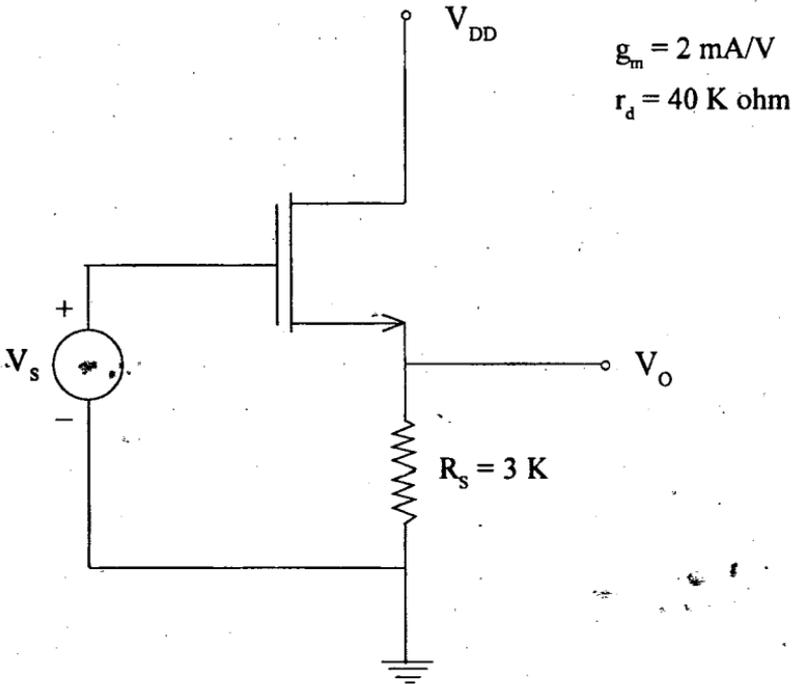


Fig. 3

- (d) Write the disadvantages of RC phase shift oscillator. Draw the circuit diagram of RC phase shift oscillator and derive the expression for frequency.

- (e) Draw the circuit of colpitts oscillator using MOSFET devices and show that tank circuit capacitors are in the ratio given as

$$\frac{C_2}{C_1} = g_m R.$$

- (f) What is piezoelectric crystal ? Derive the expression of the ratio of frequency in series and parallel resonance in a piezoelectric crystal.