

Printed Pages: 02

Sub Code: NEC402

Paper Id: 131422

Roll No.

--	--	--	--	--	--	--	--	--	--

B TECH
(SEM. IV) THEORY EXAMINATION 2017-18
ELECTRONIC CIRCUITS

Time: 3 Hours**Total Marks: 100**

- Note:** 1. Attempt all Sections.
2. Assume any missing data.

SECTION A

- 1. Attempt all questions in brief. 2 x 10 = 20**
- A differential amplifier has inputs $V_1 = 10\text{mV}$ and $V_2 = 9\text{mV}$. It has a differential mode gain of 60dB and a CMMR of 80dB. Find the percentage error in the output voltage and the error voltage.
 - What do you mean by voltage follower circuit? Explain in brief.
 - How MOSFET works as a switch and amplifier.
 - Explain the difference between DMOSFET & EMOSFET.
 - A BJT having $\beta = 100$ is biased at a dc collector current of 1 mA. Find the value of g_m and r_e .
 - Find out the relationship between α , β and γ .
 - Draw the current mirror circuit and write its output current equation.
 - What are the advantages of using an active load in differential amplifier circuit?
 - Explain the Barkhausen criterion for oscillator.
 - What are the advantages and disadvantages of negative feedback.

SECTION B

- 2. Attempt any three of the following: 10 x 3 = 30**
- What are the characteristics of the ideal Op-Amp? Explain the concept of virtual ground. Design a noninverting amplifier with a gain of 2 at the maximum output voltage of 10V the current in the voltage driver is to be 10 μA .
 - A MOSFET is to operate at $I_D = 0.1 \text{ mA}$ and is to have $g_m = 1 \text{ mA/V}$. If $K'_n = 50 \mu\text{A/V}^2$. Find the required W/L ratio and the overdrive voltage.
 - Write the steps through which small signal equivalent circuit model can be used in the analysis of transistor amplifier.
 - Design and explain the working of a differential amplifier using active load circuit in detail.
 - Explain the working of a Phase Shift oscillator. Derive an expression for the frequency of oscillations. What are the merits and demerits of such oscillator?

SECTION C

- 3. Attempt any one parts of the following: 10 x 1 = 10**
- (i) Draw the schematic diagram of an instrumentation using op amp and explain its working.
(ii) What do you mean by Integrator? Derive the expression for output voltage.
 - (i) For the circuit shown in figure-1, obtain the transfer function.

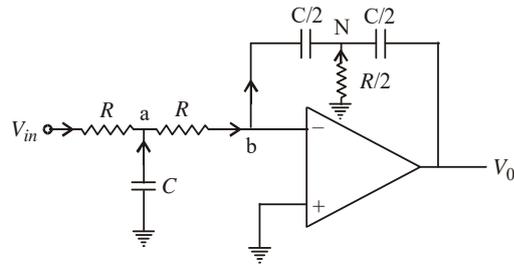


Figure 1

(ii) Derive the formula for negative feedback amplifier gain in terms of A_f , A & β

4. Attempt any one parts of the following: 10 x 1 = 10

- a) Draw and explain depletion type N-MOSFET with its characteristics
- b) Draw the circuit diagram of biasing the MOSFET using a constant-current source and calculate the expression for I in terms of I_{REF} .

5. Attempt any one parts of the following: 10 x 1 = 10

- a) Find the collector current and collector-emitter voltage for the circuit shown in figure-2.

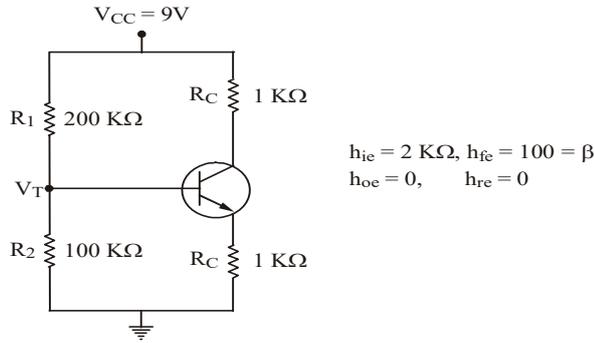


Figure 2

- b) Draw the circuit diagram of single stage CE amplifier, implement hybrid- π model for it and calculate expressions for gain, input/output impedance, i_e , g_m and i_b .

6. Attempt any one parts of the following: 10 x 1 = 10

- a) Find the Q-point, V_c and I_B for the differential amplifier shown in Figure-3.

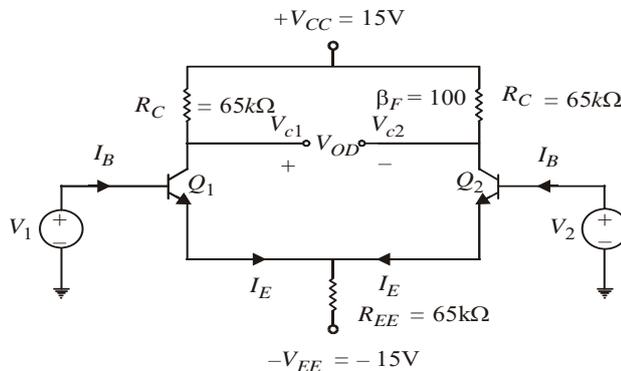


Figure 3

- b) Do the small signal analysis of MOS differential pair to determine differential and common mode gain.

7. Attempt any one parts of the following:**10 x 1 = 10**

- a) Distinguish current feedback and voltage feedback with appropriate circuit /block diagram.
- b) (i) Draw the circuit diagram of a Wien-bridge oscillator and derive an expression for the frequency of oscillations.
(ii) In colpitts oscillator using FET, the frequency of oscillations is observed to be 2.5MHz oscillator uses: $L=10\mu\text{H}$, $C_1=.02\mu\text{f}$. Find (i) value of C_2 (ii) If L is doubled, the new value of freq. of oscillations.