

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0323

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. IV) EVEN THEORY EXAMINATION 2012-13

**ELECTRONIC INSTRUMENTATION AND
MEASUREMENTS**

Time : 3 Hours

Total Marks : 100

Note :- (i) Attempt ALL questions.

(ii) Assume the missing data if any.

(iii) Marks are indicated at the end of each Section.

1. Attempt any four parts of the following : (5×4=20)

(a) What are the desirable characteristics of transducer element in respect of sensing any physical variable ?

(b) Mean Torque of an electro dynamometer type of Wattmeter may be written as $T \propto M^p E^q Z^t$.

$M \rightarrow$ Mutual inductance between fixed and moving coil, E is applied voltage, z is impedance of load circuit. Determine the value of p, q, t from the dimensions of the quantities.

(c) Explain the limiting error. A 4 dial decade resistance box has its accuracy specified as follows :

(i) $X_1 \times 1000 \Omega \pm 0.1\%$

(ii) $X_2 \times 100 \Omega \pm 0.1\%$

(iii) $X_3 \times 10 \Omega \pm 0.5\%$

(iv) $X_4 \times 1 \Omega \pm 1\%$

If R across the terminal of Decade Resistance Box is 4739Ω , then determine the relative limiting error involved in this measurement ?

(d) How the limiting error is calculated when :

(i) Two or more variables are added

(ii) Product of two or more variable

(iii) Composite factor.

The value of an unknown R is calculated in terms of current drawn by it and the power it dissipates. If the limiting error involved in the measurement of power and current are 1.5% and 1% respectively. The relative limiting error in the measurement of R is ?

(e) An 820Ω resistance with an accuracy of $\pm 10\%$ carries a current of 10 mA. The current was measured by an analog ammeter on a 25 mA range. With an accuracy of $\pm 2\%$ of full scale. Calculate the power dissipated in the resistor and determine the accuracy of the result.

2. Attempt any two parts of the following : (10×2=20)

(a) Describe the multimeter probes which can extend the range of measurement and sense the physical variables. What is the difference between the decibel (dB) and decibel-milliwatt (dBm) measurement ?

(b) The half wave restifier electronic Voltmeter circuit in the following fig, uses a meter with a FSD current of 1 mA. The meter coil resistance is $1.2 \text{ k}\Omega$. Calculate the value of R_3 that will give meter full scale pointer deflection when ac input voltage is 100 mV (rms). Also determine the meter deflection when the input is 50 mV.

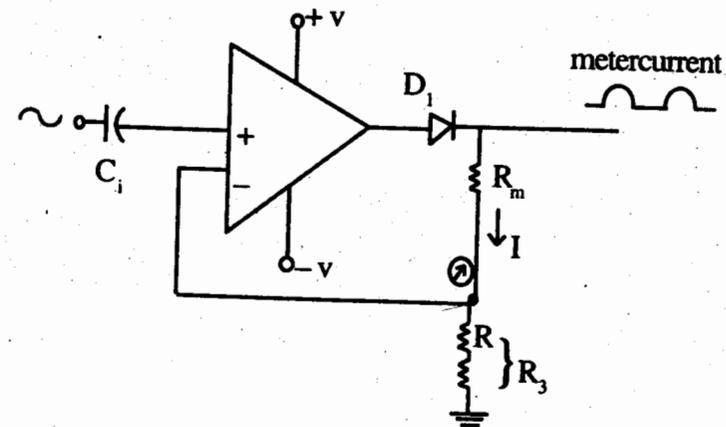


fig. 1

(c) An opamp meter shown in fig. is required to measure maximum input of 20 mV. The opamp input current is

0.2 μA and the meter circuit has $I_m = 100 \mu\text{A}$ FSD and $R_m = 10 \text{ k}\Omega$. Determine suitable resistance value for R_3 and R_4 .

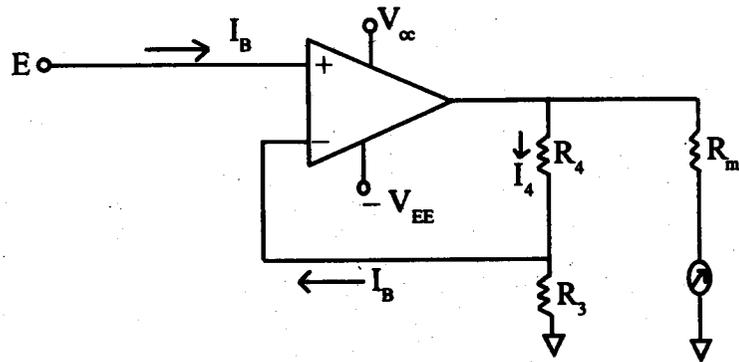


fig. 2

3. Attempt any four parts of the following : (5×4=20)

- Explain the working, principle and phasor diagram of Maxwell's capacitance Bridge.
- Explain the Budge method to measure the low resistance. What will we have to do to minimize the effect of lead resistance ?
- How the capacitance value is measured with the help of De-Sauty's Bridge ? This Bridge is used for which type of capacitor ?

(d) The 3 impedances of AC Bridge are $z_1 = 200 \Omega \angle 60^\circ$, $z_2 = 400 \Omega \angle 90^\circ$, $z_3 = 300 \Omega \angle 0^\circ$, $z_4 = ?$ When Bridge is Balanced ?

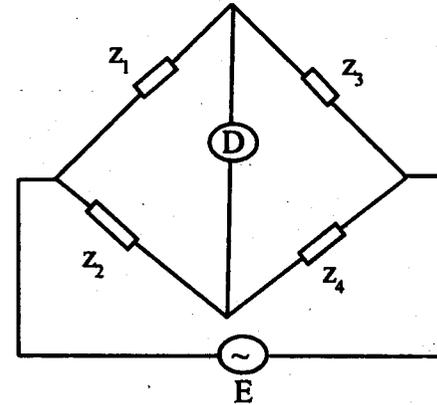


fig. 3

- How the voltmeter ammeter is used in measurement of medium Resistance and low Resistance ?
 - How the sources and detectors are determined according to f range used in AC Bridge ? Write Balance condition for AC Bridge.
4. Attempt any two parts of the following : (10×2=20)
- Determine the minimum time/division sensitivity for an oscilloscope that is to be used investigate 50 MHz waveform. Assume that the time base magnifier expands the horizontal display by a factor of 5.

- (b) A IV signal with a source resistance of $R_S = 600 \Omega$ is connected to an oscilloscope which has an input impedance of $R_i = 1 \text{ M}\Omega$ in parallel with $C_i = 30 \text{ pF}$. The coaxial cable has a capacitance of $C_{cc} = 100 \text{ pF}$. Calculate the oscilloscope terminal voltage (V_i) when $s/g f$ is 100 Hz. Also determine the f at which V_i is 3 dB below V_s .
- (c) Sketch the Block diagram of CRO and explain the working of it : What is the utility of input attenuator ? How is the loss of leading line occurred ?

5. Attempt any two parts of the following : (10×2=20)

- (a) For the 10 and 50 readings in the calibration chart in figure below. Determine the instrument accuracy as a percentage of the reading and as a percentage of full scale.

Scale reading	Precise Voltage	Correction
100	103	+3
90	93	+3
80	82.5	+2.5
70	72.5	+2.5
60	62	+2
50	51.7	+1.7
40	41.5	+1.5
30	31	+1
20	19.7	-0.3
10	9.5	-0.5
0	0	0

- (b) Sketch the circuit for calibration of wattmeter and explain the calibration procedure.
- (c) Determine the displayed rise time when a pulse waveform with a rise time of 21 ns is applied to an oscilloscope that has an upper cut off frequency of :
- 20 MHz and
 - 50 MHz.