

B. TECH

FIFTH SEMESTER EXAMINATION, 2002-2003

ANALOG INTEGRATED CIRCUITS

Time : 3 Hours.

Total Marks : 100

Note : (1) Attempt **ALL** questions.

(2) Make suitable assumptions wherever required and justify.

1. Answer any **TWO** of the following :— (10×2=20)

(a) (i) Define Common Mode Rejection Ratio and explain its significance with respect to differential amplifier.

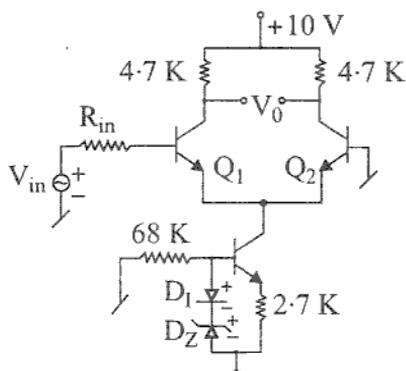
(ii) For the circuit as shown in Fig. 1, $\beta_{ac} = \beta_{dc} = 100$, $V_{BE} = V_{D1} = 0.715$ V, $V_Z = 6.2$ V, $I_{Zt} = 41$ mA, calculate :
(a) voltage gain of differential amplifier,
(b) input resistance,
(c) operating point values I_{CQ} and V_{CEQ} .

Fig. 1 -10 V

- (b) (i) Why are current mirrors used in biasing?
- (ii) In Fig. 2, a transistor array CA3086 is used and $\beta_{dc} = \beta_{ac} = 100$ and $V_{BE} = 0.715V$, find collector current of each transistor.

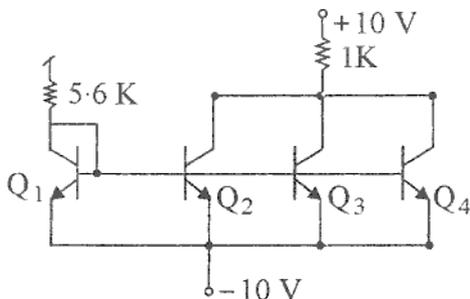


Fig. 2

- (c) Explain the working of op-amp 741 schematic diagram with a neat sketch.
2. Answer any TWO of the following :— (10×2=20)

- (a) Find $\frac{V_{01}}{V_{in}}$, $\frac{V_{02}}{V_{in}}$ and $\frac{V_{03}}{V_{in}}$ for Fig. 3 in terms of circuit parameters. Also explain, what these transfer functions represent. Assume all operational amplifiers to be ideal.

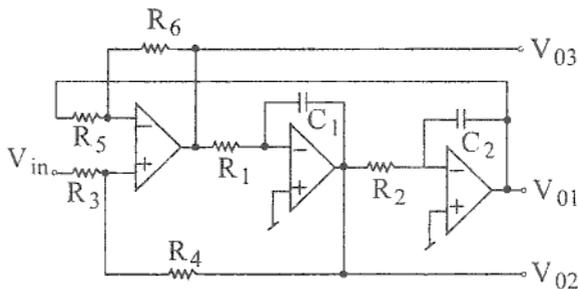


Fig. 3

- (b) (i) Explain the working of the following with neat diagrams :—
- (1) Non-inverting VCVS
 - (2) CCVS
- (ii) Design a second order Butterworth active low pass filter for a cut-off frequency of 1.0 kHz.
- (c) Consider Fig. 4 and ideal op-amp.
- (i) Compute condition of oscillation.
 - (ii) Find the frequency of oscillation.

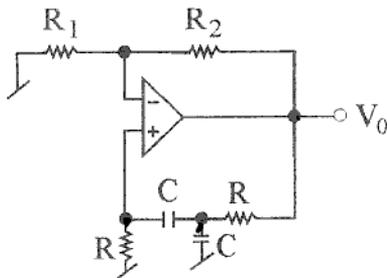


Fig. 4

3. Answer any FOUR of the following :— (5×4=20)
- (a) Derive the output expression of Log-amplifier using op-amp as active device.
 - (b) Draw Sample and Hold circuit using op-amp and explain its working.
 - (c) Explain how a Schmitt trigger works with a neat diagram.
 - (d) Draw and explain the circuit of square and triangle wave generator using op-amp and also draw the waveforms at various nodes of the circuit diagram.

- (e) Draw and explain the working of Monostable Multivibrator using op-amp.
- (f) Draw the circuit of a precision rectifier and explain its working.

4. Answer any FOUR of the following :— (5×4=20)

- (a) What is the function of a voltage regulator ? Draw the op-amp voltage regulator circuit and explain its working.
- (b) Explain with neat sketch, the current limiting features of 723 voltage regulator.
- (c) Draw the block diagram of SMPS and explain its working.
- (d) Explain the current fold back characteristics with respect to 723.
- (e) List the characteristics of an Operational Transconductance Amplifier (OTA). Draw the inverting and non-inverting amplifiers using OTA.
- (f) Find the input impedance of circuit as shown in Fig. 5.

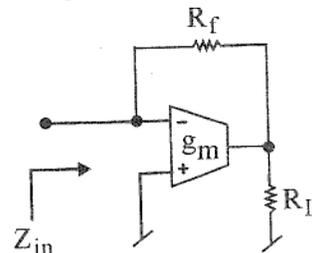


Fig. 5

5. Answer any TWO of the following :— (10×2=20)

- (a) Explain the block diagram of 555. Derive the expression for time delay of a monostable multivibrator using 555.

EC

- (b) (i) Explain Lock-in Range, Capture Range and Pull-in-time of a PLL.
- (ii) Draw the block diagram of a PLL and explain its working.
- (iii) List the applications of PLL.
- (c) (i) Write note on Programmable Gain Amplifier.
- (ii) Enlist the applications of Analog Switches. Select one application and explain its working with a neat sketch of the circuit.

