

02166

Printed Pages—3

EC—502

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 3005**

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.Tech.**

FIFTH SEMESTER EXAMINATION, 2005-2006

**ANALOG INTEGRATED CIRCUITS**


Time : 3 Hours

Total Marks : 100

FIFTH

- Note :** (i) Answer **ALL** questions.  
(ii) All questions carry equal marks.  
(iii) Make suitable assumptions wherever required and justify.  
(iv) Be precise in your answer.

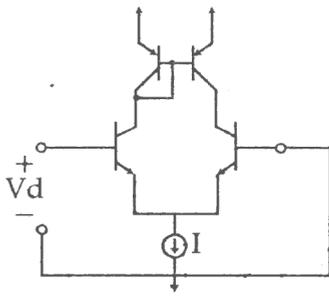1. Attempt **any two** of the following questions : (10x2=20)
- (a) (i) Discuss the operation and significance of a multiple output transistor current mirror.
- (ii) Discuss the operation of an active load in Differential Amplifier. What is primary advantage of using an active load ?
- (b) For an active loaded differential amplifier of figure shown below when biased with a current  $I = 0.2\text{mA}$ , and if the BJTs have  $\beta = 200$  and  $V_A = 100\text{V}$ , find the values of  $R_i$ ,  $R_o$ , the differential mode voltage gain, common-mode voltage gain.



- (c) Describe the operation and characteristics of a BJT complementary push pull output stage. What are the advantages of this circuit ?
2. Attempt *any two* of the following questions : (10x2=20)
- (a) Design an inverting Op-amp circuit with a voltage gain of  $A_v = v_o/v_i = -8$ . When the input voltage is  $V_i = -1V$ , the maximum current in  $R_1$  and  $R_2$  must be no larger than  $15\mu A$ . Determine the minimum values of  $R_1$  and  $R_2$ .
- (b) Describe the operation and characteristics of an Instrumentation Amplifier with neat sketch. Why do we call this as instrumentation amplifier ?
- (c) Design a second order low-pass filter at a cutoff frequency of 2KHz using op-amp.
3. Attempt *any two* of the following questions : (10x2=20)
- (a) Sketch the circuit and characteristics of basic Schmitt trigger. What are the advantages of a Schmitt trigger circuit in analog electronics ? Explain its working.

- (b) Draw and explain the operation of a triangular wave generator. How square wave can be obtained using this triangle wave ?
- (c) Draw the circuit of a log amplifier using op amps and explain its operation. Enlist the possible applications of this circuit.

4. Attempt *any two* of the following questions : (10x2=20)

- (a) Draw and explain the circuit of Electronically tunable "resistor" using OTAs.
- (b) (i) How is current boosting achieved in 723 IC ?  
(ii) Explain current fold back characteristics in voltage regulators.
- (c) Explain with circuit which gives square and square root of the given analog signal.

5. Attempt *any two* of the following questions : (10x2=20)

- (a) Design a 555 timer as an astable multivibrator with an output signal frequency of 800Hz and 60 percent duty cycle.
- (b) Draw the circuit of a PLL AM detector and explain its operation.
- (c) Draw and explain the circuit of Programmable Gain Amplifiers using Analog switch.

- o O o -