

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2115

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. V) ODD SEMESTER THEORY EXAMINATION
2010-11

ANALOG INTEGRATED ELECTRONICS.


Time : 3 Hours

Total Marks : 100

Note : Attempt all questions.

1. Attempt any **four** of the following : **(5×4=20)**
- (a) Draw the high frequency model of an Op-Amp with double break frequency. Explain the principle of this circuit.
 - (b) Explain dc and ac amplifier.
 - (c) The parameters for the differential Amplifier are given as $R_C = 1 \text{ K-ohm}$, $R_S = 1 \text{ K-ohm}$, $h_{fe} = 1 \text{ K ohm}$ and $R_e = 2 \text{ M ohm}$. Neglecting h_{oe} , calculate the difference mode gain and common mode gain. Hence calculate CMRR in dB. The amplifier is in dual input balanced output configuration.
 - (d) What do you mean by differential amplifier ? Explain the operation of a basic differential amplifier. Give the four differential amplifier configurations.

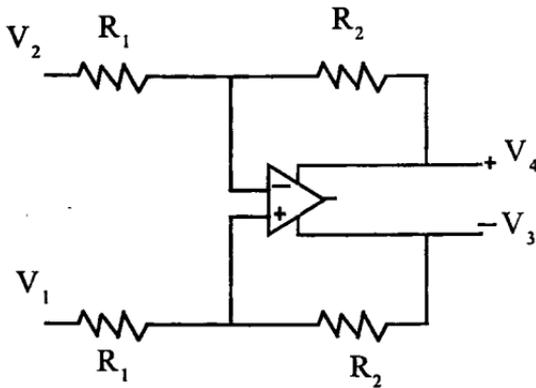- (e) Show that $V_0 = R_2/R_1 (V_1 - V_2)$ where $V_0 = V_4 - V_3$ for a differential amplifier with double ended output whose circuit is given below :



- (f) What would be the maximum Frequency of the input Voltage connected to an Op-Amp having maximum slew rate of $1/\mu\text{s}$ if the magnitude of the input voltage is 1V.

2. Attempt any **two** of the following : (10×2=20)
- (a) Draw and explain the commonly used three Op-Amp instrumentation amplifier ckt. Derive expressions for its gain.
- (b) Explain the working of Practical differentiator. Also derives its frequency response.
- (c) Design the instrumentation amplifier to have a variable differential gain in the range 5-200. Use a 50 Kohm potentiometer.

3. Attempt any **two** of the following : **(10×2=20)**
- (a) What are the advantages of active filter over passive filter ?
 - (b) Explain the working of a voltage to frequency converter with neat sketch.
 - (c) Define in case of ADC :
 - (i) Resolution
 - (ii) Quantization error
 - (iii) Conversion time.
4. Attempt any **two** of the following : **(10×2=20)**
- (a) What are precision rectifiers ? Explain full wave precision rectifier with circuit diagram waveforms.
 - (b) Explain the types of switching regulators and enlist their characteristics. Why do switching regulator have better efficiency than the series regulator ?
 - (c) Write short notes on :
 - (i) Schmitt Triggers
 - (ii) Analog switches
 - (iii) Analog multipliers
 - (iv) Voltage comparators.

5. Attempt any two of the following : (10×2=20)

- (a) What do you mean by antilog amplifier ? How log amplifier can be turned around to provide antilog function ? Explain.
- (b) List the characteristics of an operational Trans-conductance amplifier (OTA). Draw the inverting and non-inverting amplifier using OTA.
- (c) Explain the basic principles of a PLL and mention its applications. If a wave form has a positive peak of magnitude V_2 , draw a circuit using two peak detectors whose output is equal to the peak to peak value V_1-V_2 .