



Printed Pages : 2

TEC507

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3000

Roll No.

--	--	--	--	--	--	--	--	--	--

## B.Tech

(SEM V) ODD SEMESTER THEORY EXAMINATION 2009-10  
ANALOG INTEGRATED ELECTRONICS

Time : 3 Hours]

[Total Marks : 100

- Note :
- (1) Attempt all questions.
  - (2) All questions carry equal marks.

1 Attempt any **two** parts of the following :

- (a) The parameters for the differential amplifier are given as :  $R_C = 1 \text{ k}\Omega$ ,  $R_S = 1 \text{ k}\Omega$ ,  $h_{fe} = 1 \text{ k}\Omega$  and  $R_E = 2 \text{ M}\Omega$ . Neglecting  $h_{oe}$ , calculate the difference mode gain and common mode gain. Hence calculate CMRR in dB. The amplifier is in dual input, balanced output configuration.
- (b) What do you mean by differential amplifier ? Explain the operation of a basic differential amplifier. Give the four differential amplifier configuration.
- (c) Explain the Miller effect compensation method used for internally compensated op-amp. Which are the two commonly used compensating networks ?

2 Attempt any **two** parts of the following :

- (a) Design the instrumentation amplifier to have a variable differential gain in the range 5-200. Use a 50 k $\Omega$  potentiometer.



- (b) Explain the working of practical differentiator. Also derive its frequency response.
- (c) Draw and explain the commonly used three op-amp instrumentation amplifier circuit. Derive expression for its gain.

3 Attempt any **two** parts of the following :

- (a) What is an all pass-filter? Explain its operation and application areas.
- (b) Design a multiple feedback narrow band pass filter with  $f_c=1$  kHz,  $Q = 3$  and  $A = 10$ .
- (c) Explain the operation of a 4-bit R-2R type DAC and derive the expression for the output voltage.

4 Attempt any **two** parts of the following :

- (a) Using op-amp design triangular wave generator and square wave generator.
- (b) State the frequency of oscillation and minimum gain of op-amp required in Wien bridge Oscillator.
- (c) Draw and explain the working of op-amp based staircase and pulse generator circuit.

5 Attempt any **two** parts of the following :

- (a) Explain working of PLL using appropriate block diagram and explain any one application of the same.
- (b) What is a voltage controlled oscillator? Explain the working of voltage controlled oscillator.
- (c) What do you mean by Antilog amplifier? How log amplifier can be turned around to provide antilog function? Explain.

