

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3004

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

FIFTH SEMESTER EXAMINATION, 2005-2006

DIGITAL INTEGRATED CIRCUITS


Time : 3 Hours

Total Marks : 100

- Note :** (i) Attempt **ALL** questions.
(ii) All questions carry equal marks.
(iii) Be precise in your answer.

1. Attempt **any four** parts of the following : (5x4=20)

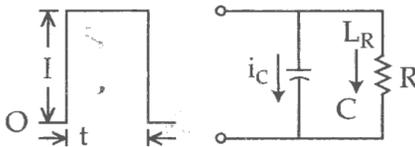
- (a) A current pulse of amplitude I is applied to a parallel RC circuit as shown in figure below, plot to scale (approximately) wave forms of currents i_C for the cases (i) $t < RC$ (ii) $t = RC$ and (iii) $t > RC$




- (b) A symmetrical square wave of peak-to-peak amplitude V and frequency f is applied to a high pass RC circuit. Show that percentage tilt is given by

$$P = \frac{1 - e^{-1/2/RC}}{1 + e^{-1/2/RC}} \times 200\%$$

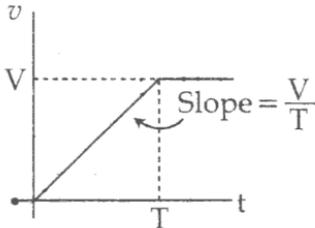- (c) A ramp as shown in figure is applied to a RC differentiates. Draw the output waveform for the cases :



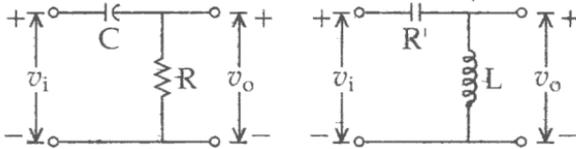- (i) $T = RC$
 (ii) $T = 0.2 RC$
 (iii) $T = 5RC$
- (d) Prove that for same input and with circuits at rest, the output from both differentiating circuits will be same if $RC = L/R'$.




- (e) Why integrators are preferred over differentiates in analog computer applications.
- (f) Why compensation is required in attenuator at all ? Draw step responses of over compensated and under compensated attenuators and explain.

2. Attempt *any four* parts of following : 5x4=20

- (a) Compare the relative merits of N MOS, C MOS, TTL and ECL logic families.
- (b) Draw the circuit diagram of a TTL NAND gate and explain its operation.

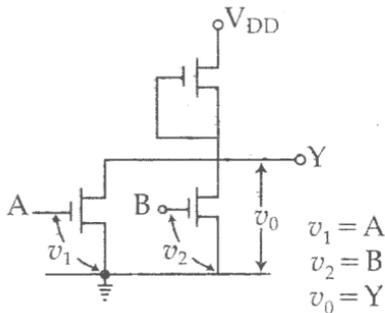- (c) Draw the circuit diagram of a CMOS NOR gate, explain its operation and enumerate five desirable properties of CMOS gates.
- (d) Draw the circuit diagram of a ECL OR/NOR gate, explain its operation and discuss the significance of reference voltage.
- (e) For the circuit shown below, find output boolean expression for Y and hence deduce the truth table.




- (f) List and discuss four advantages and four disadvantages of a the ECL gate.

3. Attempt *any two* parts of following : 10x2=20

- (a) What do you mean by universal shift register ? Draw the circuit diagram of a universal shift resistor and explain its working with timing diagram.
- (b) What is the difference between serial and parallel transfer ? Explain how to convert serial date to parallel and parallel data to serial. What type of register is needed.

The content of a 4 bit register is initially 1101. The register is shifted to six times to the right with serial input being 101101. Tabulate the content of each register after each shift.

- (c) For the figure shown below, derive the flip-flop input equations for J and K in terms of L, C and I. Explain the working of circuit.

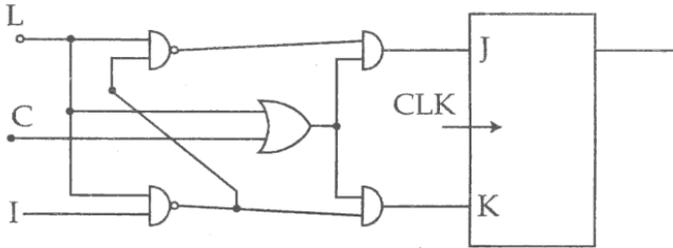

4. Attempt *any two* parts of following :

- (a) Differentiate between DRAM and SRAM. Draw the logic diagram of a memory cell (RAM) and explain its working with read and write timing diagram.
- (b) Draw the wiring diagram of 256K byte ROM bank using $32K \times 8$ ROM chip and mention (i) Number of address lines (ii) Specify decoder.
- (c) Draw the circuit diagram of Schmitt trigger circuit using 555 explain its operation with suitable waveforms. Enumerate the application of this circuit.

5. Write short notes on *any three* of following :

20

- (a) Multiplexer and Demultiplexer
- (b) PLA and PAL
- (c) SPLD and CPLD
- (d) As table and mono stable multivibrator
- (e) BiCMOS digital circuit.

** *** **