



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B. TECH**  
**(SEM V) THEORY EXAMINATION 2021-22**  
**INDUSTRIAL ELECTRONICS**

*Time: 3 Hours**Total Marks: 100***Note:** 1. Attempt all Sections. If require any missing data; then choose suitably.

**SECTION A**

1. **Attempt *all* questions in brief.** **2 x 10 = 20**
- a. Define regenerative feedback?
  - b. Define Latching Current.
  - c. Explain Holding Current.
  - d. What is FACLF?
  - e. Explain di/dt protection.
  - f. How dv/dt protection is done?
  - g. What is the use of Freewheeling diode?
  - h. Define Duty Cycle of a chopper.
  - i. Define Soft Switching.
  - j. Explain Transducer.

**SECTION B**

2. **Attempt any *three* of the following:** **10 x 3 = 30**
- a. Describe different modes of operation of thyristor with the help of its static V-I Characteristics. Also explain Gate Characteristics of SCR.
  - b. Draw R and RC firing circuits for SCR and discuss the function of various components used. Also draw the voltage waveforms.
  - c. Explain the working of UPS with the help of block diagram.
  - d. Explain Opto-SCR.
  - e. Write brief note on Industrial Robots.

**SECTION C**

3. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain the operation and working of TRIAC.
  - (b) Explain the operation and working of IGBT.
4. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain series and parallel operations of SCR.
  - (b) Explain the working of SCR using two transistor model.
5. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain single phase bridge inverter with the help of load voltage and load current waveforms.
  - (b) Explain SMPS through block diagram.



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

6. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain Variable Frequency Drives.
- (b) Explain Programmable Timers and their industrial applications.
7. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain slip power Recovery Scheme for the speed control of AC drive.
- (b) The speed of separately excited dc motor is controlled through 1-phase half wave-controlled converter from 230V mains. The motor armature resistance is  $0.5 \Omega$  and motor constant is  $K=0.4V\text{-s/rad}$ . For load torque of 20 Nm at 1500 rpm and for constant armature current, calculate
- (i) Firing angle of converter
- (ii) Rms value of thyristor current