

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2117Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. V) THEORY EXAMINATION 2011-12

INTEGRATED CIRCUITS

Time : 3 Hours

Total Marks : 100

Note :- Attempt all questions. All questions carry equal marks.

Assume missing data suitably if any.

1. Attempt any **two** parts of the following : **(10×2=20)**
- (a) (i) What are desirable characteristics of current mirror circuits? Draw the simple BJT current mirror circuit and reduce the expression for current transfer ratio using matched transistors.
- (ii) What are the advantages of Widlar current source? For the circuit shown in figure 1, assuming high β of transistors and $V_{BE} = 0.7$ V at 1 mA. Find the value of R that will result in $I_o = 10 \mu\text{A}$.


 



Figure 1

- (b) Explain the role of negative feedback capacitance of $C_c = 30\text{pF}$ at second stage of OPAMP 741. Find corresponding pole frequency of IInd stage gain = 515, output resistance of input stage is $67\text{M}\Omega$ and input resistance of IInd stage is $4\text{M}\Omega$.
- (c) Figure 2 shows output stage OPAMP 741. Find output voltage swing. Also explain the role of short circuit protection circuit.

 

2. Attempt any two parts of the following : (10×2=20)

 - (a) For the circuit shown in figure 4, find $\frac{V_o}{V_i}$.



Design a single stage amplifier to have $R_i = 1 \text{ M}\Omega$ and voltage gain hundred. N_o Resistance should have value greater than $50 \text{ M}\Omega$.

- (b) Draw the circuit diagram of an inductance simulation circuit and find the expression for equivalent inductance.
- (c) Draw the circuit diagram of state variable filter and find the transfer function of Low pass, High pass and Band pass filter.

3. Attempt any **two** parts of the following : **(2×10=20)**

- (a) Find truth table and CMOS realization of following gates :
 - (i) AND-OR-INVERT (AOI) $\Rightarrow F = \overline{AB + CD}$
 - (ii) OR-AND-INVERT (OAI) $\Rightarrow F = \overline{(A + B)(C + D)}$
- (b) Give two different CMOS realization of the exclusive-OR function $Y = A\bar{B} + \bar{A}B$ in which the PDN and PUN are dual networks.
- (c) Give CMOS implementation of a clocked SR flip-flop and explain its working.

4. Answer any **two** parts of the following : **(2×10=20)**

- (a) Draw the circuit diagram of triangular waveform generator using OPAMP and also find the expression for frequency of the Triangular waveform.
- (b) Draw the circuit diagram of Anti-log amplifier and find the expression for output voltage.

- (c) Draw the circuit diagram of Astable multivibrator using OPAMP and find the expression for its time period. Show

$$\text{that } f_0 = \frac{1}{2 RC} \text{ if } R_1 = 1.16 R_2.$$

5. Attempt any **two** parts of the following : (2×10=20)

- (a) Define Lock-in-Range, Capture Range and Pull-in-Time as related to PLL. Draw the circuit diagram of Frequency multiplier using PLL and explain its working.
- (b) Draw the functional block diagram of IC 555 and explain its working. Draw the circuit diagram of a monostable multivibrator using 555 and find expression for quasi state period.
- (c) Write short note on analog to digital converter.