

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B. TECH.
(SEM-V) THEORY EXAMINATION 2019-20
INTEGRATED CIRCUITS

Time: 3 Hours

Total Marks: 100

Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A**1. Attempt all questions in brief.****2 x 10 = 20**

- (i) What do you mean by Current Mirror circuit?
- (ii) Give small signal model of transistor.
- (iii) What do you mean by DC analysis of a circuit?
- (iv) For Widlar current source assume $I_{ref} = 1 \text{ mA}$ and $R_2 = 5 \text{ K}\Omega$, neglect base current, find I_{C2} .
- (v) Give two application of analog multiplier.
- (vi) Define a Filter circuit.
- (vii) Differentiate between Comparator and Schmitt trigger.
- (viii) Describe the need of voltage limiter circuits.
- (ix) The basic step of an 8-bit DAC is 20mV. If 00000000 represents 0V, what is represented by the input 10110111.
- (x) Which is the fastest ADC and why.

SECTION B**2. Attempt any three of the following:****10x3=30**

- (a) Describe the operation and characteristics of a BJT complementary push-pull output stage.
- (b) Draw the circuit of state variable filter and find the transfer function of Low pass, High pass and Band pass filters.
- (c) Describe temperature compensated Log amplifier using two op-amp & explain its operation.
- (d) What do you mean by the quadrant operation of multiplier. Draw and explain a GILBERT analog multiplier.
- (e) Draw the block diagram of a PLL and explain its operation. Explain lock-in-range, capture range and pull-in time of a PLL. List the application of PLL.

SECTION C**3. Attempt any one part of the following:****10x1=10**

- a) Explain the circuit of Wilson MOS current mirror. Also discuss how it can be improved.
- b) The parameter of the three transistor CM are $V_{CC} = 9\text{V}$, $V_{EE} = 0$, $R_1 = 12\text{K}\Omega$, $V_{BE(\text{on})} = 0.7\text{V}$, $\beta = 75$, $V_A = \infty$. Calculate the value of current, I_{ref} , I_o , I_{C1} , I_{B1} , I_{B2} , I_{B3} , I_{E3} .

4. Attempt any one part of the following:**10x1=10**

- a) Draw the V-I converter and derive its output equation for grounded load.
- b) Derive the output expression for RC Phase Shift Oscillator.

5. Attempt any one part of the following:**10x1=10**

- a) Give CMOS implementation of a SR flip-flop and explain its working.
- b) Discuss the features of CMOS circuit. Realize one AND-OR-INVERT (AOI) and one OR-AND-INVERT (OAI) function using CMOS logic circuit.

6. Attempt any one part of the following:**10x1=10**

- a) Draw & explain the working of monostable multivibrator using op-amp.
- b) Describe the working of single op-amp based full wave precision rectifier.

7. Attempt any one part of the following:**10x1=10**

- a) Draw and Explain the block diagram of IC 555.
- b) Explain the operation of dual slope ADC giving its neat diagram.