

c) Write a short note on the following

- i. Transconductance cells
- ii. Ladder design

—x—

Printed Pages : 4



\*1316\*

351

EEC-011

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 131651**

Roll No.

**B.Tech.**

**(SEM VI) THEORY EXAMINATION, 2015-16**

**ANALOG SIGNAL PROCESSING**

*Time : 2 Hours]*


*[Total Marks : 50*

*Note- Attempt All Questions. All Questions carry equal marks:-*

**1. Attempt any Two of the following questions:**

- (a) Describe in detail account on Integrator and Differentiator with suitable equations. Also define CMRR and Slew rate with its significance.

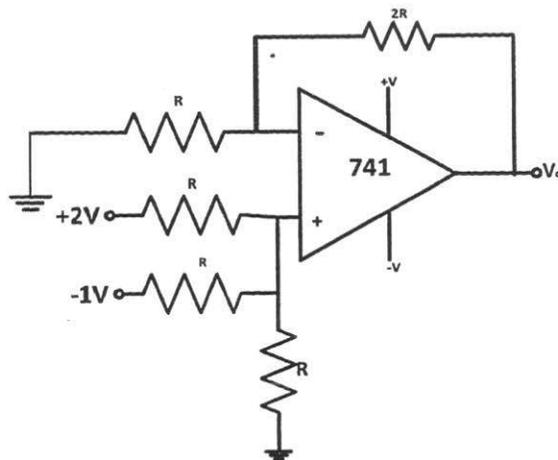- (b) Calculate the output voltage  $V_o$  of the given circuit in fig.



- (c) Sketch a three input inverting summing circuit and derive an expression for the output voltage. Design a Non- Inverting amplifier capable of providing a voltage gain of 15. Assume ideal Op-Amp and Resistances used should not be exceeding 30K $\Omega$ .

2. **Attempt any TWO of the following questions:**

- a) Name the circuit that is used to detect the peak value of the non- sinusoidal waveforms. Explain the operation with neat circuit diagram.

- b) Draw and explain the most commonly used three op-amp instrumentation amplifiers. Also derive the expression for its voltage gain.
- c) Draw the circuit of an inverting negative half wave rectifier and its transfer characteristics. Explain its working.

3. **Attempt any TWO of the following questions:**

- a) Draw and explain the anti-log amplifier. How temperature compensation is achieved in anti-log amplifier?
- b) Draw the circuit of a generalized impedance converter (GIC). Realize a grounded impedance using GIC and find its value.
- c) Draw the block diagram of Tow Thomas biquad. Derive the circuit diagram of the biquad. Find the transfer function of high pass and low pass functions.

4. **Attempt any TWO of the following questions:**

- a) Draw the KHN biquad filter and derive the transfer function of BPF and LPF from that.
- b) Discuss first order gyrators and sallen key circuits.