

Printed Pages:02

Paper Id:

1	3	1	6	0	4
---	---	---	---	---	---

Sub Code:EEC-604

Roll No.

--	--	--	--	--	--	--	--	--	--

B TECH
(SEM-VI) THEORY EXAMINATION 2017-18
INTRODUCTION TO ELECTRIC DRIVES

Time: 3 Hours**Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A**

- 1. Attempt all questions in brief. 2 x 10 = 20**
- a. Write the differences between Transistor and Thyristor.
 - b. Explain the basic principle of Thyristor.
 - c. Listed the various performance factors of line commutated converters.
 - d. What do you mean by dual converter? Explain.
 - e. Enlist the advantages & applications of cyclo-converter.
 - f. Explain the term: Chopper.
 - g. Define DC motor speed control.
 - h. Enlist the different methods for braking of a dc motor
 - i. Discuss about the significance of rotor resistance control.
 - j. Write the differences between AC drives and DC drives.

SECTION B

- 2. Attempt any three of the following: 10 x 3 = 30**
- a. (i) Explain the gate protection of SCR against over voltage and currents.
(ii) Draw and explain the V-I characteristics of a thyristor.
 - b. Draw and explain the circuit for single phase half wave controlled converter with RLE load. Also explain its output waveforms.
 - c. Explain the principle of chopper operation. Also Explain the working of step-up chopper.
 - d. Explain the operation of separately excited dc motor driven using a semi-converter.
 - e. (i) Explain the construction and working of three phase induction motor.
(ii) Discuss about anyone method for speed control of induction motor.

SECTION C

- 3. Attempt any one part of the following: 10 x 1 = 10**
- (a) With a neat diagram explain the working of the gate trigger circuit thyristor.
 - (b) (i) Write a note on resistance capacitance firing circuit.
(ii) The voltage and current rating in a particular circuit are 3KV and 750A respectively. SCRs with a rating of 800V and 175A are available. Minimum derating factor is 15%. Determine the number of series and parallel units required.

4. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Explain the operation of fully controlled bridge circuit having inductive load and find the expression for output voltage.
 - (b) What do you mean by the three phase inverter? Explain its working with its output waveforms.
5. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) Describe the waveform for single phase to single phase circuit step-down cyclo converter for discontinuous load current.
 - (b) What do you mean by Jones copper? Explain the design considerations of Jones copper.
6. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) (i) Describe the regenerative braking of a chopper-fed separately excited dc motor. Illustrate answer with circuit diagram and relevant waveforms.
(ii) Explain in brief anyone method of braking of a dc motor.
 - (b) Explain the speed control of DC series motor using single phase full converter.
7. **Attempt any *one* part of the following:** **10 x 1 = 10**
- (a) (i) Draw a suitable diagram & explain working of slip power recovery system using commutator-less Kramer drive.
(ii) Enumerate the variable frequency control of an induction motor.
 - (b) A 3-phase squirrel cage induction motor running at 1440 rpm at 50Hz develops torque of 2000N-m. If motor frequency is now increased to 80 Hz using constant power mode. Calculate the new value of torque developed by motor at constant slip.