

- (b) Describe the stick layout design style for CMOS circuit design.
- (c) Draw CMOS inverter circuit and explain its transfer characteristics. If the change over between logic levels is symmetrical, show that the width to length ratio of the p-device is approximately three times that of the n-device.

Attempt any *two* parts of the following : (2×6=12)

- (a) What is VLSI design rule ? Why is it required ? Describe the Lambda based design rules for CMOS circuit design. Explain with suitable diagram.
- (b) Construct a colour coded stick diagram to represent the design of a CMOS circuit that implements the following function :

$$F = \overline{A} \cdot (\overline{B} + \overline{C}).$$

- (c) Discuss a combined voltage and dimension scaling model. Compare the scaling factors for the following device parameters :

Gate area, Gate capacitance, channel resistance, current density and power dissipation for the different scaling models.

4. Attempt any *two* parts of the following : (2×7=14)

- (a) Describe the standard cell based design. Enlist the various standard cell library. What are the parameters of good VLSI design ?
- (b) Design an n-MOS switch based logic implementation of a four-way multiplexer layout.
- (c) Draw and discuss the general format of Built-in-Self-Test (BIST) structure.