



Printed Pages : 4

TEC-042

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0392

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.**(SEM. VIII) EXAMINATION, 2007-08****VLSI DESIGN***Time : 3 Hours]**[Total Marks : 100*

- Note :**
- (1) *Attempt all questions.*
 - (2) *Be precise in your answers.*
 - (3) *All questions carry equal marks.*

1 Attempt any four parts of the following : 5×4=20

- (a) Discuss different steps involved in a typical n-well process.
- (b) In how many ways tubs can be formed in a substrate ? Discuss the advantages associated with twin tub structure.
- (c) What is the role of LOCOS technique in the development of VLSI circuits ?
- (d) How does the non-uniform doping control the threshold voltage of MOS transistor ? Which other parameter can affect the threshold voltage effectively ?
- (e) Obtain the transconductance (g_m) of an MOS transistor in terms of its circuit parameters.



- (f) List the parameters that affect the switching speed of an MOS transistor. How does the figure of merit is related to the transconductance of an MOS transistor ?

2 Attempt any **four** parts of the following : **5×4=20**

- (a) How does a β - ratio shifts a VTC curve of an MOS based inverter circuit ? Give suitable reasons in support of your answer.
- (b) Discuss the important features of Lambda based design rules.
- (c) Determine the value of pull-up to pull-down ratio (Z_{pu}/Z_{pd}) for an N-MOS inverter driven by another N-MOS inverter.
- (d) If the pull-up to pull-down ratio is 4:1 in the above case and delay is $\tau = 0.3 n$ sec across the first inverter determine the overall delay for the above pair.
- (e) If a CMOS inverter charges and discharges through a capacitive load (C_L), obtain the expression for rise-time (t_r). (Assume $V_{tp} = 0.2 V_{DD}$, where V_{DD} is the supply voltage). In order to achieve symmetrical operation of a CMOS inverter what design parameters are required ?



- (f) If approximate value of R_S (ohms per square) of an n-channel transistor is $10^4 \Omega/\text{square}$, calculate the channel resistance for the Fig. 1 given below

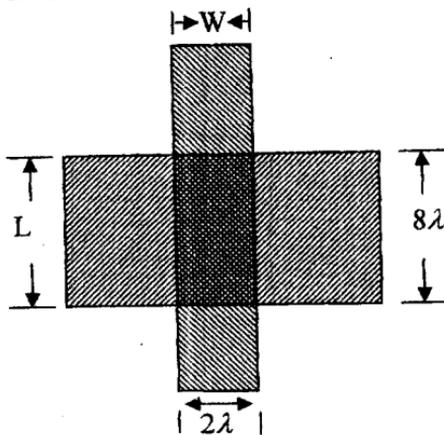


Fig. 1

3 Attempt any two parts of the following : $2 \times 10 = 20$

- (a) Discuss the scaling effect on MOS structures and limitation of scaling on the following on the following :

- (1) Substrate doping
- (2) Depletion width
- (3) Limits of miniaturization

- (b) Draw the color coded stick diagrams of two input n-MOS, CMOS, NAND and NOR gates.

- (c) Consider a CMOS inverter circuit with the following parameters : $V_{DD} = 3.3 \text{ V}$,

$$k_n = 200 \mu\text{A}/\text{V}^2, \quad k_p = 80 \mu\text{A}/\text{V}^2$$



$$V_{T_{0,n}} = 0.6 V, \quad V_{T_{0,p}} = -0.7 V \quad \text{and}$$

$k_R = 2.5$. Calculate the output voltage

V_{out} and critical voltages

$(V_{OL}, V_{OH}, V_{IL} \text{ and } V_{IH})$ in the VTC and determine the noise margins of the circuit.

4 Attempt any **two** parts of the following : $2 \times 10 = 20$

- (a) What is FPGA ? Discuss the design flow of an FPGA chip. Mention certain advantages of it.
- (b) With the help of a block diagram explain the sequence of steps to design an ASIC. Explain the term semi-custom and full-custom ASICs.
- (c) Give the names of various ASIC design methodologies. Discuss in brief the LCA approach.

5 Write short notes on any **two** of the following : $2 \times 10 = 20$

- (a) Fault types of Models
- (b) Controllability and Observability
- (c) Built-in-self test (BIST) techniques
- (d) Packaging technology

