

Printed pages:  
Paper ID: 2008

Sub Code: EE-303

Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.TECH**

**(SEM III) THEORY EXAMINATION 2017-18  
ANALOG AND DIGITAL ELECTRONICS**

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

**SECTION A**

1. Attempt all questions in brief.

2 x 10 = 20


- Draw the characteristic of a diode.
- What do you mean by doping in diodes?
- Why we use feedback in amplifier.
- What is the effect of coupling capacitor in low frequency response?
- What is Barkhausen condition for oscillation?
- What are the applications of oscillator?
- What is the difference between encoder and decoder?
- Draw the pin diagram of IC555 timer.
- Draw the block diagram of a sequential circuit.
- What is a basic memory cell explain.

**SECTION B**

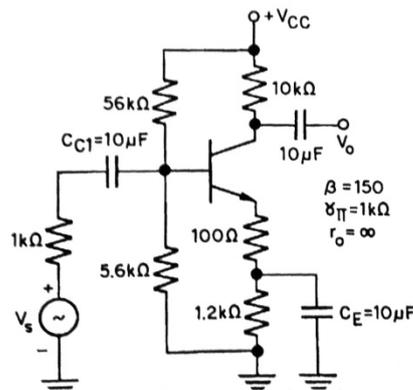2. Attempt any three of the following:

10 x 3 = 30

- Explain tunnel diode and schottky diode draw their characteristic and diagram
- For the BJT amplifier circuit shown in figure determine:
  - The lower half frequency due to coupling capacitor (i)  $C_{c1}$  (ii)  $C_E$
  - the overall lower cut off frequency of the amplifier circuit



- Derive the relation for oscillation frequency and oscillation condition for Wien Bridge and Colpitts oscillator.
- What is shift registers? Explain any two types of shift registers with their wave diagram, table and applications.
- Explain and derive the relations for DAC. What is a R-2R ladder network, explain in detail.

**SECTION C**

3. Attempt any one part of the following:

10 x 1 = 10

- Explain varactor diode ,its characteristics and applications
- What is a photodiode? Explain its characteristic and applications. Explain how a photodiode works as photo resistor.

4. Attempt any one part of the following:


10 x 1 = 10

- Explain voltage series and voltage shunt feedback with the help of circuit and block diagram and derive the relation for gain and input/output impedance with and without feedback.

- (b) Explain properties of negative feedback. A power amplifier with a gain of  $100 \angle 0^\circ$  has an output of 12V at 1.5 kHz along with a second harmonic content of 25%. A negative feedback is to be provided to reduce the harmonic content of the output to 2.5%. What should be the gain of the feedback path and the level of signal input to the overall system?

**5. Attempt any two parts of the following: 5 x 2 = 10**

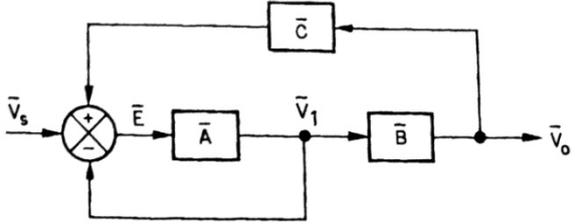
- (a) Explain the working of Hartley Oscillator with suitable diagram. Give its expression for frequency of oscillation.
- (b) For the block diagram given  $\bar{A} = 60 \angle 90^\circ$ , and  $\bar{B} = 30 \angle 90^\circ$  at a certain frequency. Find the value of C for the system to be oscillatory.



- (c) Explain phase shift oscillator and derive the relation for the frequency of oscillation.

**6. Attempt any two parts of the following: 5 x 2 = 10**

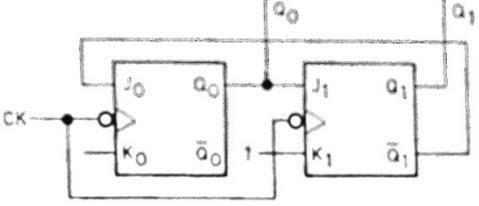- (a) Realize a JK flip flop using AND and NOR gate only.
- (b) Design a mod- 9 counter by cascading two mod-3 counter of given figure. Give the table showing the sequence of state.



- (c) Explain multiplexer and demultiplexer with their block diagram, logic diagram and truth table.

**7. Attempt any two parts of the following: 5 x 2 = 10**

- (a) Explain ROM with the help of block diagram. Also show the array of diodes.
- (b) Explain monostable multivibrator and derive the relation for pulse width and restoration time and output characteristic.
- (c) Write a short note on Switch Mode power Supply (SMPS).