



Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM III) THEORY EXAMINATION 2021-22**  
**NETWORK ANALYSIS AND SYNTHESIS**

**Time: 3 Hours**



**Total Marks: 70**

**Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.

**SECTION A**

**1. Attempt all questions in brief.**



**2 x 7 = 14**
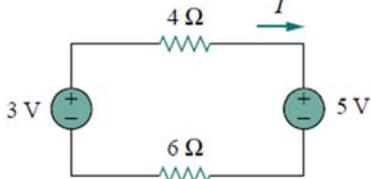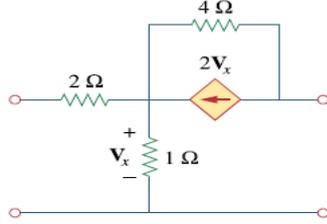
<b>a.</b>	Find the current $I$ in the circuit shown in the Figure 1.
	
Figure 1	
<b>b.</b>	Find out $h_{11}$ and $h_{21}$ in terms of Y parameters.
<b>c.</b>	Find Z-parameter for the given network in Figure 2:
	
Figure 2	
<b>d.</b>	What is maximum power transfer theorem?
<b>e.</b>	Write two properties of Complete Incidence matrix.
<b>f.</b>	Perform test on given polynomial to check whether it is Hurwitz or Not. $F(s) = s^7 + 3s^6 + s^5 + 4s^4 + 4s^3 + 2s^2 + 10s + 10$
<b>g.</b>	Write the properties of R-C driving point functions.

**SECTION B**

**2. Attempt any three of the following:**

**7 x 3 = 21**

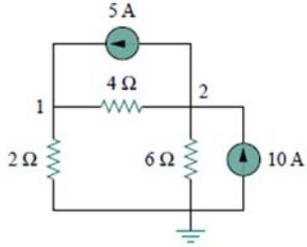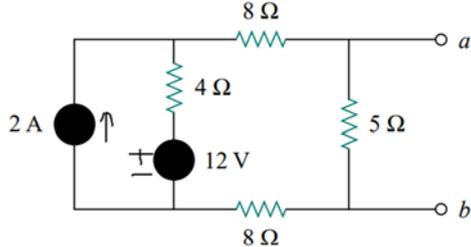
<b>a.</b>	Identify the node voltages in the circuit shown in Figure 3.
	
Figure 3	
<b>b.</b>	Find the Norton equivalent circuit of the circuit in Figure 4.
	



Roll No: 


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM III) THEORY EXAMINATION 2021-22**  
**NETWORK ANALYSIS AND SYNTHESIS**

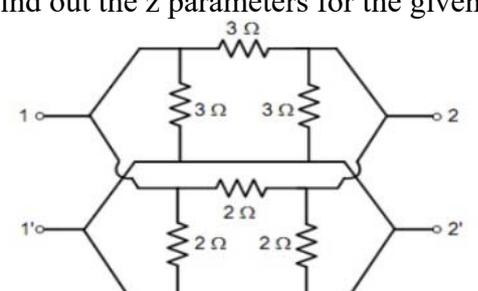
	Figure 4
c.	Check the stability of the polynomial by applying Routh-Hurwitz criterion in: $F(s) = s^6 + 3s^5 + 8s^4 + 15s^3 + 17s^2 + 12s + 4$
d.	Find out the z parameters for the given two port networks in figure 5: 
e.	Find the first Foster form and second Cauer form after synthesizing the impedance function given by, $Z(s) = 2(s+1)(s+3)/(s+2)(s+6)$

**SECTION C**

3. Attempt any one part of the following: 7 x 1 = 7

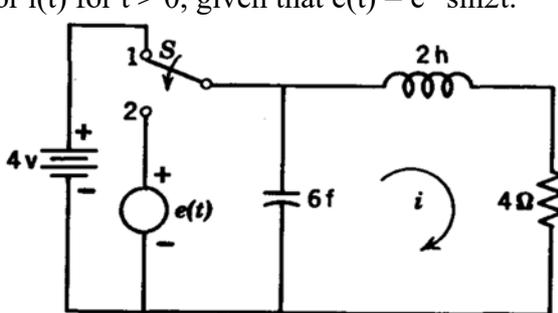(a)	Explain the term resonance. Also determine the condition of resonance in serial RLC circuit.
(b)	As shown in the Figure 6 the switch S is moved from position 1 to 2 at $t = 0$ , having been in position 1 for a long time before $t = 0$ . Find particular solution for $i(t)$ for $t > 0$ , given that $e(t) = e^{-t} \sin 2t$ . 

4. Attempt any one part of the following: 7 x 1 = 7

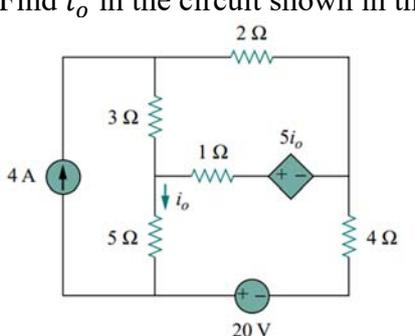(a)	Find $i_o$ in the circuit shown in the figure using superposition. 
-----	---



Roll No: 

--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM III) THEORY EXAMINATION 2021-22**  
**NETWORK ANALYSIS AND SYNTHESIS**

(b) Find the Thevenin equivalent circuit of the circuit shown in Figure 8, to the left of the terminals *a-b*.

Figure 8

5. Attempt any one part of the following: 7 x 1 = 7

- (a) Explain following terms with reference to network topology:  
 (i) Tree  
 (ii) Co-tree  
 (iii) Incidence matrix  
 (iv) Oriented graph  
 (v) Twig and link
- (b) Explain Complete Incidence Matrix, Tie Set Matrix and Cut set matrix for a graph with the help of proper example.

6. Attempt any one part of the following: 7 x 1 = 7

(a) Find  $Y$  parameters for the given network in figure 9:

Figure 9

(b) Obtain  $h$  and  $g$  parameters for the network shown below in figure 10:

Figure 10

7. Attempt any one part of the following: 7 x 1 = 7

- (a) Identify the Given impedance function and then Find out first and second Cauer form for the same impedance function given below:  
 $(s^2+4)/2(s^2+1)(s^2+9)$
- (b) Find the Foster I form, Foster II form, Cauer I form & Cauer II form for the given function:  
 $F(s) = 2(s^2+1)(s^2+9) / s(s^2+4)$