

Printed Pages—5

TEE—303

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID: 2044

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

THIRD SEMESTER EXAMINATION, 2006-07

NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours

Total Marks : 100

- Note : (i) Attempt ALL questions.
(ii) All questions carry equal marks.
(iii) In case of numerical problems assume data wherever not provided and state assumption made.
(iv) Be precise in your answer.

1. Attempt *any four* parts of the following : (5×4=20)

(a) Differentiate with suitable example :

- (i) Cut-set and Tie-set.
(ii) Directed graph and connected graph.

(b) A reduced incidence matrix of a graph is given by

$$[A] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

obtain the number of possible trees.

04995

TEE—303

1

[Turn Over

- (c) Draw a graph of resistive network shown in fig 1 (b). Select a suitable tree and obtain the tie-set matrix.

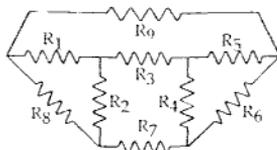


Fig.1(b)

- (d) Derive relation between Branch voltage matrix, Twing Voltage matrix and Mode Voltage matrix of a network.
 (e) Find Norton's current I_N for the network shown in fig. 1 (d) using graph theory.

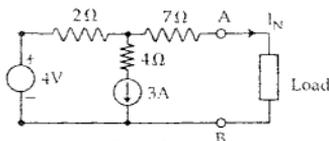


Fig.1(d)

- (f) Develop the Tie-set matrix of the circuit given in fig. 1 (e).

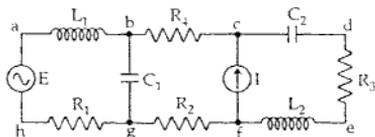


Fig.1(e)

2. Attempt *any two* parts of the following : (10x2=20)

- (a) Define and explain Thevenin's theorem. In the network shown in fig. 2 (a), find Thevenin's equivalent network across A-B terminals.

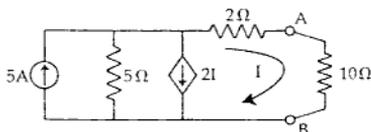


Fig.2(a)

- (b) (i) Find Norton's equivalent circuit across 1-1' of ac network shown in fig 2 (b).

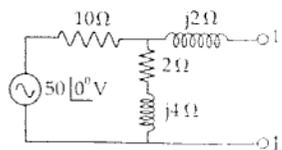


Fig.2(b)

- (ii) Illustrate Tellegen's theorem for the network shown in fig 2 (c).

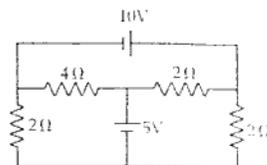


Fig.2(C)

- (c) Find the current through the capacitor and voltage across 4Ω resistance of the ac network shown in fig 2 (d) by using superposition theorem.

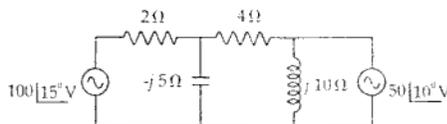


Fig.2(d)

3. Attempt *any two* parts of the following : (10x2=20)

- (a) Enlist the necessary conditions for transfer function. Find the transfer function $\left(\frac{V_2}{V_1} \right)$ of the network given in fig. 3 (a). Also sketch pole - zero configuration.

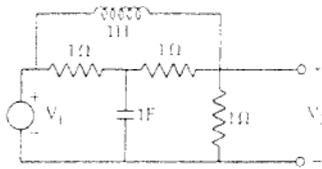


Fig. 3(a)

(b) The transform current $I(s)$ in a network is given

$$I(s) = \frac{3S(S+2)}{(S+1)(S+4)}$$

Plot the poles and zeros in the s -plane and hence obtain the time domain response.

(c) Discuss difference between driving point function and transfer function. Determine driving point impedance function of the network shown in figure 3 (b).

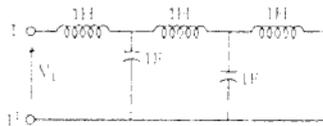


Fig. 3(b)

4. Attempt *any two* parts of the following : (10x2=20)

(a) Determine the h parameters of the network given in fig. 4 (a).



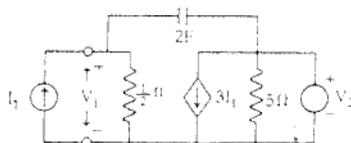


Fig 4(a)

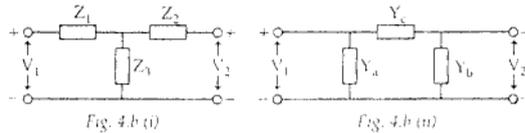- (b) For the T-network given in fig 4 (b) (i), obtain z-parameters and for π -network of fig. 4 (b) (ii). Obtain Y-parameters. If these networks have identical behaviour at the ports relate the elements of the two networks.



- (c) Determine transmission parameters of a network given in fig. 4 (c), considering sections as shown are connected in cascade manner.

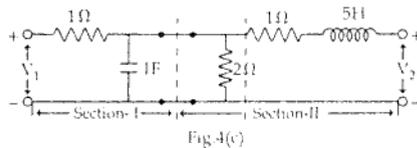

5. Attempt *any two* parts of the following : (10x2=20)
- (a) Diagnose whether the following impedance function represents a RL or RC network and find its first cauer form.

$$Z(S) = \frac{(S+4)(S+6)}{(S+3)(S+5)}$$

- (b) Realise the function $Z(S) = \frac{S(S^2+4)}{2(S^2+1)(S^2+9)}$ in

both foster forms of LC network.

- (c) Design a T-section constant K - high pass filter having cutoff frequency of 10 KHz and design impedance of 600 Ω . Find its characteristic impedance and phase constant at 25 KHz.

- o O o -