

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2044

Roll No.

--	--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. III) ODD SEMESTER THEORY EXAMINATION
2010-11

NETWORKS ANALYSIS AND SYNTHESIS

Time : 3 Hours

Total Marks : 100

Note : Attempt **all** the questions.

1. Attempt any **three** of the following :

(a) Define the following : 6

- (i) Connected graph
- (ii) Path
- (iii) Tree
- (iv) Links.

(b) For the network shown write the tie-set Matrix and determine the loop current and the branch currents. 6

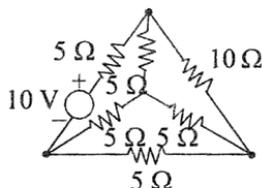


Figure 1

(c) For the graph shown in figure 2, find the cut-set schedule. 6

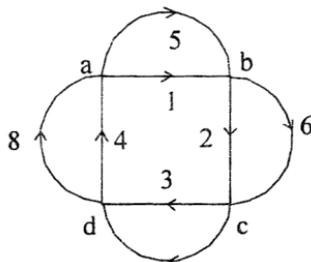


Figure 2

(ii) Show that the graph shown in figure 3 is isomorphic. 6

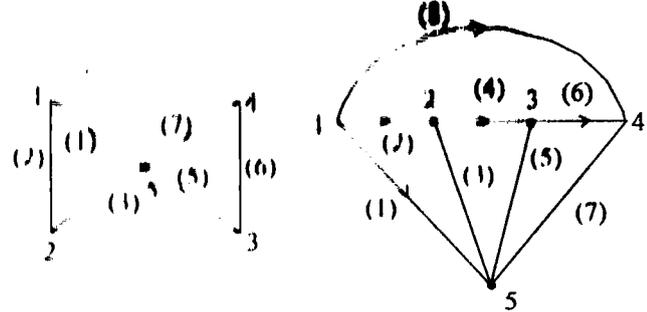


Figure 3

2. Attempt any **three** parts of the following :
- (a) (i) Write the super position theorem.
 - (ii) For the network shown determine Thevenin's equivalent source and the series impedance.

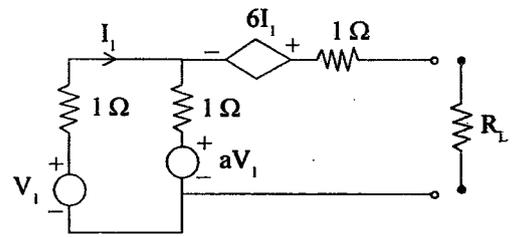


Figure 4

- (b) Verify Tellegen theorem for the pair of networks shown. Select suitable values in the two circuits. 7

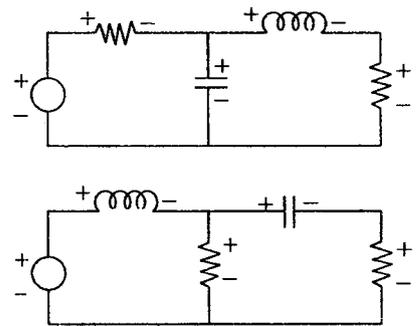


Figure 5

- (c) Write the statement of maximum power transfer theorem and also prove that maximum power can be transferred if load is complex conjugate of internal impedance. 7
- (d) Determine X_1 and X_2 in terms of R_1 and R_2 to give maximum power dissipation in R_2 . 7

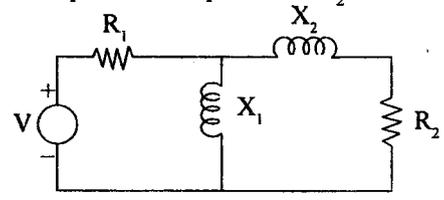


Figure 6

3. Attempt any **two** parts of the following :

- (a) Construct the Bode plot for the following transfer functions :

$$G(s) = \frac{10(s+10)}{s(s+5)(s+2)} \quad 10$$

- (b) Test whether the system represented by following characteristic equation is stable or not :

$$2s^4 + s^3 + 3s^2 + 5s + 10 = 0. \quad 10$$

- (c) For the given L-C network find the transform impedance $Z(s)$. 10

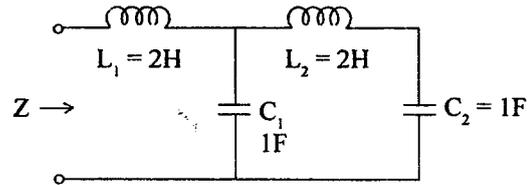


Figure 7

4. Attempt any **two** parts of the following :

- (a) Derive the condition for reciprocity and symmetry in case of (a) h-parameters, (b) Y-parameters. 10

- (b) Find the $Z_{11}(s)$ and $Z_{22}(s)$ parameters for the given bridged-T R-C network. 10

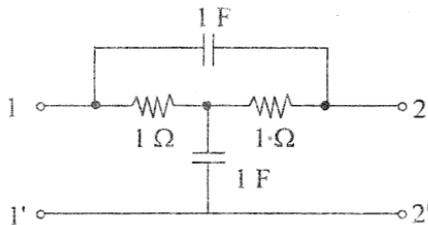


Figure 8

- (c) Obtain the transmission parameters in term of Z-parameters and Y-parameters. 10

5. Attempt any **two** parts of the following :

- (a) An impedance function is given by :

$$Z(s) = \frac{(s+1)(s+5)}{s(s+3)(s+7)}$$

find the R-C representation of foster-I and II forms. 10½

- (b) For the constant-k, low pass filter, derive/find out the two cutoff frequencies.
- (c) Find the driving point impedance as a quotient of polynomials for the given network. 10½

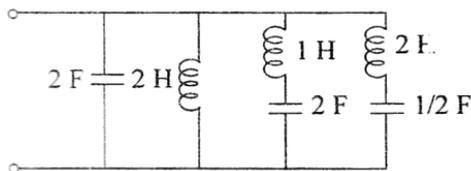


Figure 9